

75 cents

hcr


focus
on
communications
technology . . .

ham radio

magazine

JANUARY 1971


THE MAINLINE ST-6 RTTY DEMODULATOR

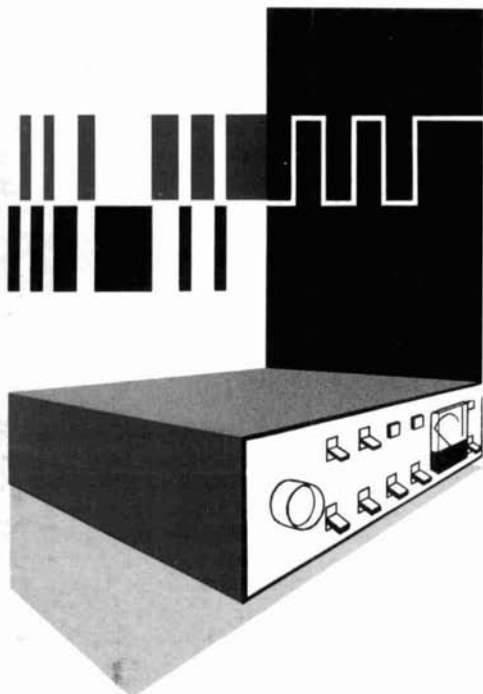

this month

- intermittent voice operation of power tubes 24
- 8873 zero-bias triode 32
- frequency meter 40
- 220-MHz linear 44

The *ALPHA SEVENTY*

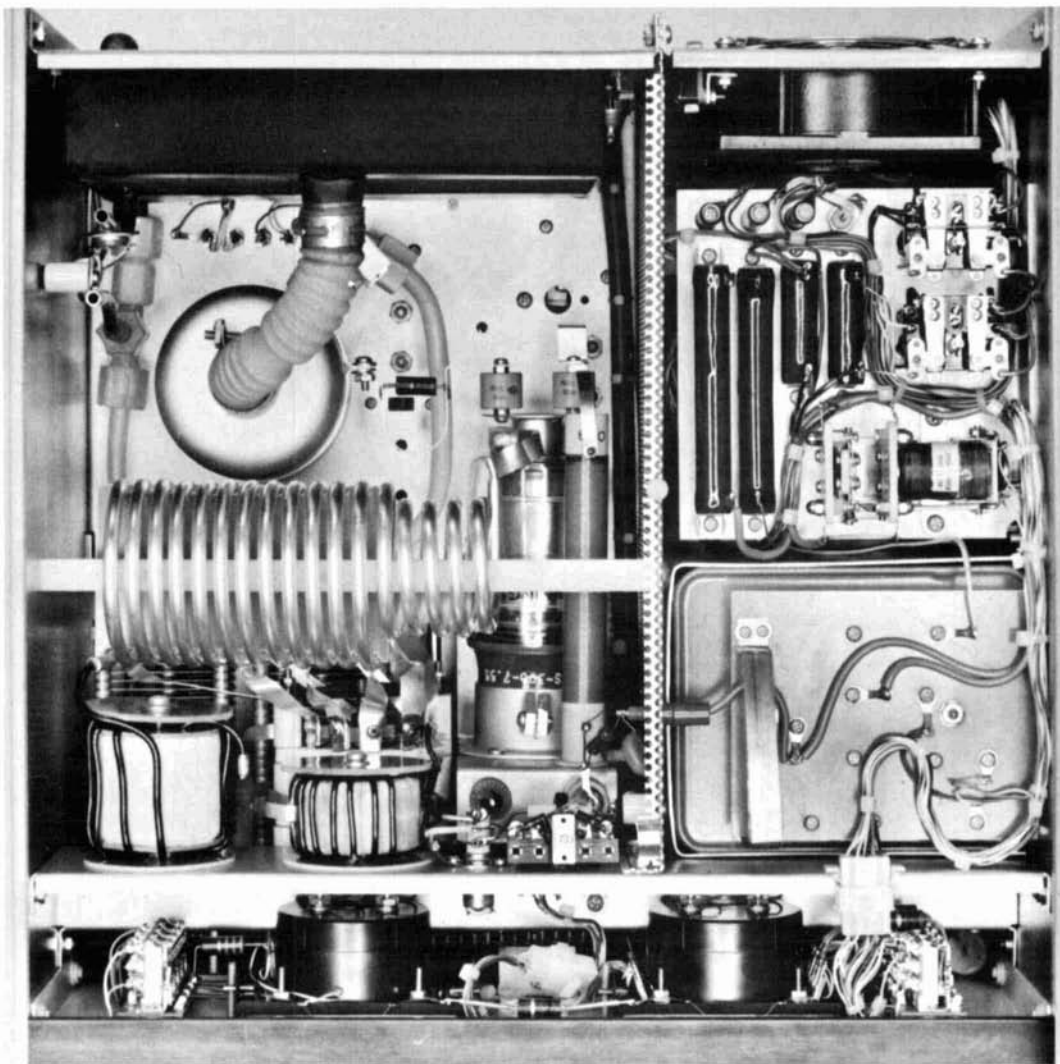

BEAUTY IS MORE THAN SKIN DEEP

The *ALPHA SEVENTY* is handsome *on the outside* . . . but to a performance lover - a connoisseur of superb quality - the real *functional beauty* is *inside*.

The *ALPHA SEVENTY* speaks *performance* . . . continuous high power capability - cool, quiet operation - versatility and convenience.

The *ALPHA SEVENTY* is *seventy pounds of Silectron® powered, vapor-cooled muscle* . . . free of excess bulk, weight, and noise. Write for details of *THE ULTIMATE* in linear amplifiers. Or see your dealer. \$1595.




EHRHORN TECHNOLOGICAL OPERATIONS, INC.

BROOKVILLE, FLORIDA 33512

(904) 796-8400

**IF YOU'VE
EVER
USED
A
REPEATER,**

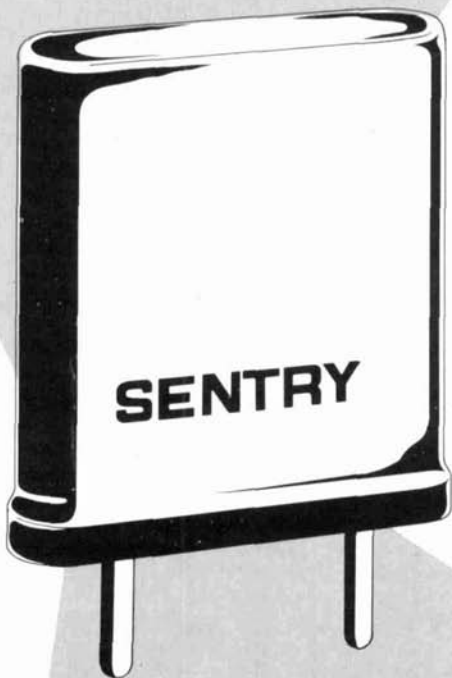

**YOU'VE USED A
SENTRY CRYSTAL**

If you haven't
already received
a copy of our **NEW**
1970 Catalog of Precision
Quartz Crystals & Electronics
for the Communications Industry,
SEND FOR YOUR COPY TODAY!

Somewhere along the line, in virtually every ham repeater in the world, you'll find a couple of Sentry crystals.

Repeater owners and FM "old-timers" don't take chances with frequency—they can't afford to. A lot of repeater users depend on a receiver to be on frequency, rock stable...in the dead of winter or the middle of July. The repeater crowd took a tip from the commercial "pros" a long time ago—and went the Sentry Route.

That's one of the reasons you can depend on your local repeater to be there (precisely there) when you're ready to use it. FM'ers use the repeater output as a frequency standard. And for accuracy, crystals by Sentry are THE standard.

**IF YOU WANT THE BEST,
SPECIFY SENTRY CRYSTALS.**

*"Ask the Hams and Pros
Who Build Repeaters!"*



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780

TWX-910-830-6425

The only difference between the new Heathkit® Frequency Counter and those costing \$400

...is the price **\$199⁹⁵***



Compare performance & features of the IB-101 to counters selling for twice the price! Counts from 1 Hz to over 15 MHz; advanced IC design eliminates blinking readout and divider chain adjustment.

8-digit capability. Set the range switch to kHz and read to the nearest kHz... push the range switch to Hz and read down to the last Hz. Overrange & Hz/kHz indicators light up to give correct range at all times; do an 8-digit measurement with 5-digit readout.

Exclusive Heath-designed input circuit. Dual gate, diode-protected MOSFET design provides proper triggering without adjustment from less than 100 mV to over 200 V. Input Z is 1 megohm shunted by less than 20 pF to minimize circuit loading & error.

Other features include sockets for all 26 IC's and 5 display tubes... double-sided, plated-thru fiberglass circuit board... 120/240 VAC operation...

convenient handle/tilt-stand. Compare the new Heathkit IB-101 to the \$400 models... and discover that \$199.95 buys more counter.

Kit IB-101, 7 lbs. \$199.95*

IB-101 SPECIFICATIONS: Frequency Range: 1 Hz to greater than 15 MHz. Accuracy: ± 1 count \pm time base stability. Gate Times: 1 millisecond or 1 second with automatic reset. INPUT CHARACTERISTICS—Sensitivity: 1 Hz to 1 MHz, less than 100 mV rms. 1 MHz to 15 MHz, less than 250 mV rms, after 30 minutes warmup. Trigger Level: Automatic. Impedance: 1 Megohm shunted by less than 20 pF. Maximum Input: 200 V rms, DC—1 kHz. Derate at 48 V per frequency decade. TIME BASE: Frequency: 1 MHz, crystal controlled. Aging Rate: Less than 1 PPM/month after 30 days. Temperature: Less than ± 2 parts in 10^7 /degree C. 20 to 35 degrees C after 30 minutes warmup. $\pm .002\%$ over 0 to 40 degrees C. GENERAL: Readout: 5 digits plus overrange. Ambient Temperature Range: Storage: -55 to 80 degrees C. Operating: 0 to 40 degrees C. Power Requirements: 105-125 or 210-250 VAC, 50/60 Hz, 8 watts. Cabinet Dimensions: 8 $\frac{1}{2}$ " W x 3 $\frac{1}{2}$ " H x 9" D not including handle. Net Weight: 4 $\frac{1}{2}$ lbs.



FREE '71 CATALOG

Describes these and over 300 other Heathkits. Save up to 50% by building them yourself. Use coupon and send for your FREE copy!

HEATH COMPANY, Dept. 122-1
Benton Harbor, Michigan 49022



a Schlumberger company

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Name _____
(Please Print)

Address _____

City _____ State _____ Zip _____

Prices & specifications subject to change without notice.

*Mail order prices; F.O.B. factory.

TE-237

January, 1971
volume 4, number 1

staff

James R. Fisk, W1DTY
editor

Nicholas D. Skeer, K1PSR
vhf editor

J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Jean Frey
art director

Wayne T. Pierce, K3SUK
cover

T. H. Tenney, Jr. W1NLB
publisher

John B. Morgan, K1RA
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology Inc.
Greenville, New Hampshire 03048

Subscription rates, world wide:
one year, \$6.00, three years, \$12.00.
Second class postage
paid at Greenville, N. H. 03048
and at additional mailing offices

Foreign subscription agents:
United Kingdom:
Radio Society of Great Britain,
35 Doughty Street, London WC1, England.

All European countries:
Eskil Persson, SM5CJP, Frotunagrand 1,
19400 Upplands Vasby, Sweden.

African continent:
Holland Radio, 143 Greenway,
Greenside, Johannesburg,
Republic of South Africa

Copyright 1970 by
Communications Technology, Inc.
Title registered at U. S. Patent Office.
Printed by Wellesley Press, Inc.
Wellesley, Massachusetts 02181, U.S.A.


ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind,
221 Rock Hill Road, Bala Cynwyd,
Pennsylvania 19440.
Microfilm copies of current
and back issues are available
from University Microfilms,
Ann Arbor, Michigan 48103.

Postmaster: Please send form 3579 to
ham radio magazine, Greenville,
New Hampshire
03048



contents

- 6 mainline ST-6 RTTY demodulator
Irvin M. Hoff, W6FFC
- 24 intermittent voice operation
of power tubes
William I. Orr, W6SAI
- 32 using the 8873 zero-bias triode
Robert I. Sutherland, W6UOV
- 40 two-meter fm frequency meter
C. A. Baldwin, W4JAZ
- 44 220-MHz power amplifier
M. O. Beck, WB6DJV
- 50 swr indicator
J. A. Houser, WB2GQY
- 54 fire protection in the ham shack
Jack Darr
- 62 mosfet converter for receiver
instrumentation
Robert A. Schiers, Jr., WA9ZMT
- 65 simple cw monitor
James L. Wiesmueller, WA9OHR
- 4 a second look 66 ham notebook
- 94 advertisers index 70 new products
- 83 flea market 94 reader service

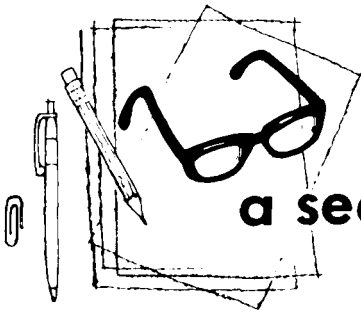

a second look

by Jim
fisk

Although the number of manned Apollo missions to the moon has been drastically cut back by NASA, the amateur group working on Moonray still hopes to have their uhf lunar repeater carried to the moon on one of the remaining flights. The primary objective of Moonray, proposed in 1960 by W6OLO, is to provide a free-access uhf repeater for world-wide communication on the 432-MHz band.

The Moonray package will contain a sensitive low-noise receiver, tuned to 439.9 MHz, a signal processor, an identifier, six to eight channels of telemetry, and transmitter output on 430.1 MHz, as well as a laser receiver. Power will be provided by a nuclear thermoelectric generator with a half life of 87 years. The system is expected to be continuously operational for a year or longer on a 24-hour-per-day basis, with one-minute interruptions at the end of each 10-minute period.

The antenna, pointing system and thermal controls are all self contained in a louvered metal cylinder about 6 inches in diameter and 10 inches long. Three legs will be used for supporting the package on the lunar surface, as well as leveling; a special pointing mechanism is provided so the astronaut who sets up the unit will be able to accurately align the Moonray antenna to earth.

The 10-KHz passband on both the 430.1- and 439.9- MHz links will accept all modes of transmission, including cw, fsk, modulated cw, afsk, narrow-band fm,

ssb and a-m (in that order of preference). Moonray's callsign will be the identifier SS, transmitted every ten minutes along with a telemetry sequence.

Amateurs who want to use the Moonray repeater should be equipped with a high-gain antenna (15-dB minimum gain) capable of tracking the moon, as well as a low-noise (3-dB maximum) crystal-controlled converter on 430.1 MHz, and a stable 439.9-MHz transmitter. For cw operation, transmitter power output should be approximately 50 watts. More power will be required for other modes, progressing from about 100 watts for fsk to 1000 watts for slow-scan television.

The design, development and test of an operational prototype is now in progress, and final construction of a flight model is planned for the near future. There are many ways you can help with this ambitious project including technical help to the group, providing publicity, promoting additional 432-MHz activity, or by making financial contributions to help obtain special items and defray postage and printing costs (contributions are fully tax deductible).

To obtain more technical information on Moonray, or to offer help, write to Nassau College Amateur Satellite Tracking, Astronomy and Radio, Post Office Box T, Syosset, New York 11791. Your help will be appreciated.

Jim Fisk, W1DTY
editor

Henry Radio's **KENWOOD**



Never before has there been an amateur receiver and transmitter like the KENWOOD R-599 solid state receiver and T-599 hybrid transmitter. The wait is over . . . the promise of the transistor has been fulfilled. KENWOOD promises to be the new pacesetter in the field of short wave radio equipment . . . setting new standards of performance, reliability, flexibility, high styling, and value. Deliveries start in November. Order yours today. Become the proud owner of the world's most technologically advanced amateur Receiver/Exciter combination.

The R-599 Receiver \$298.00
The T-599 Transmitter \$345.00


Henry Radio's **TEMPO "ONE"**



The Tempo "ONE" SSB transceiver represents the culminating achievement of many years of experience in the amateur radio field. Modern design, superb performance, sturdy construction, outstanding reliability . . . at a surprisingly low price makes the Tempo "ONE" the best buy in transceivers today. Please come in or write for complete specifications.

The Tempo "ONE" \$298.00
AC/one, 110-220 volt 50/60 cycle power supply . . . \$99.00
DC/one, 12 volt DC power supply . . . \$107.00

Henry Radio's **2K-4**

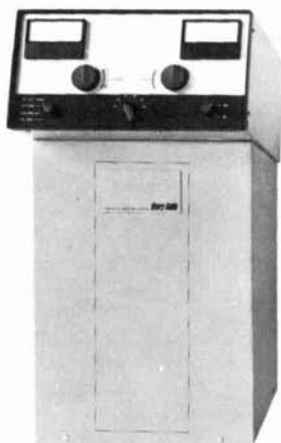

The 24-K linear amplifier embodies all of the famous features of the 2K-3 . . . rugged construction, reliable performance and heavy duty components, plus unique modern styling. The tilted RF deck faces up for easy visibility and convenient operation. If you are one of the more than 3000 happy 2K

owners, trade up to the new 2K-4. If you are not one of the group, now is the time to join.
The 2K-4 (console or desk model) . . . \$795.00

Now, meet Henry Radio . . .



Walt Henry
W6ZN
ANAHEIM



Ted Henry
W6UOU
LOS ANGELES



Bob Henry
WØARA
BUTLER


Plus a large staff of highly qualified sales and service personnel pledged to serve you. Henry Radio carries large stocks of all major brands. We take trade-ins, sell used equipment and offer better terms because we carry our own financing. Our reconditioned equipment carries a 15 day trial, 90 day warranty and may be traded back within 90 days for full credit toward the purchase of new equipment. Export inquiries solicited. Also, military, commercial, industrial, and scientific users . . . please write for information on our custom line of high power linear amplifiers and RF power generators.

Henry Radio

11240 W. Olympic Blvd., Los Angeles,
Calif. 90064
931 N. Euclid, Anaheim, Calif. 92801
Butler, Missouri 64730
New York area: John Richardt W2W1Y
Houston area: Jan Carman W5SBX

213/477-6701
714/772-9200
816/679-3127
201/637-4107
713/464-0419

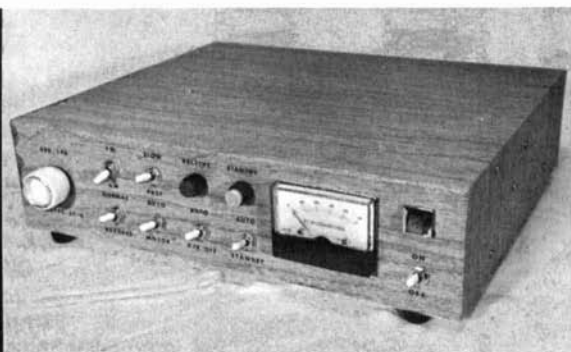"World's Largest Distributor of Amateur Radio Equipment"



the Mainline ST-6 RTTY demodulator

Here's an ultra-modern
RTTY tuning unit
that features
the latest in
electronic circuitry
and design

An RTTY demodulator (often called a terminal unit, TU or converter) is used between the radio receiver and the Teletype machine to change the audio output of the receiver into on-off dc pulses to operate the printer.

Most RTTY demodulators work on the fm principle — they have a limiter followed by a discriminator that selects the mark or space tone, a detector to convert this audio into the dc keying rate, perhaps a low-pass filter to clean up the signal, a trigger stage that decides when mark has changed to space and vice versa, and finally, a keyer stage that drives the Teletype machine. Two power supplies are normally used, one to drive the demodulator and one to drive the Teletype machine, called the loop supply.

Some demodulators work on the a-m principle. This is often called two-tone, or limiterless operation. In this case, no limiter is used although some modest amplification might be incorporated. A threshold corrector is required to provide

Irvin M. Hoff, W6FFC, Los Altos Hills, California 94022

the proper symmetry to the slicer. This type of demodulator can copy mark-only or space-only type signals also. It works quite well in some circumstances, especially at full automatic machine speed, sometimes called "tape speed." To realize the advantages of a-m reception, high-performance channel filters should be used, but rarely are — a simple linear discriminator providing little advantage over fm in a majority of cases. If automatic printer control (auto-start) has been added, it must be disabled for a-m copy since the steady reference level used for the squelch system is no longer a stable voltage.

A good demodulator should have provisions for both fm and a-m operation, as the circuitry used for a-m is beneficial even when using normal fm reception.

the mainline rtty demodulators

The original Mainline RTTY converter was published in 1963.¹ The Mainline TT/L was introduced in late 1964² and had features that soon set the standard for

published, as the GE PA-238 operational amplifier became available about the same time. The ST-2 (autostart but no motor delay) and the ST-3 (autostart with motor delay) were published in 1968.⁴ The ST-4 was the same as the ST-3, but designed exclusively for narrow-shift (170 Hz) reception for autostart. The ST-5⁵ used two 709C operational amplifiers and was as simple a unit as a person could hope to get for normal reception of RTTY signals. The Mainline ST-6 presented here is an advanced solid-state demodulator offering all the practical advantages known to be beneficial for RTTY reception.

features of the ST-6

1. Optional bandpass input filters of 3-pole Butterworth design.
2. Use of seven 709C operational amplifiers; nine if both 170 and 850 shifts are added.
3. A limiter having over 90-dB gain.
4. Well-designed linear discriminators for various shifts.
5. Full-wave detection.
6. Active low-pass minimum bandwidth 3-pole Butterworth filter using two operational amplifiers.
7. Threshold corrector for a-m reception.
8. High-gain operational amplifier for a slicer that allows reception on shifts as low as 1 Hz.
9. 300-volt keying transistor stage for minimum distortion.
10. Floating-loop supply giving optimum plus-minus voltages for best FSK (transmitter) provisions.
11. Narrow-shift cw identification provisions.
12. Regulated plus-minus 12-volt supply.
13. *Anti-space* system that quickly puts the printer to mark-hold if the signal goes to steady space.
14. Automatic printer control (auto-start) that ignores voice or cw signals but responds to RTTY, turning on the printer motor automatically.
15. Motor delay control to keep the motor from turning on and off exces-



Rear-panel layout of the ST-6 RTTY demodulator.

serious RTTY enthusiasts. The Mainline TT/L-2³ was an up-graded TT/L with a heftier power and loop supply, plus a few minor circuit improvements.

Then I turned to solid-state — all units just mentioned used vacuum tubes. The first in the new series was the ST-1, using an RCA integrated circuit. It was never

sively during weak signal reception or compulsory cw identification.

16. Optional a-m or fm reception.

17. Simplified switching for versatility.

18. Low-cost but effective tuning indicator.

19. Very simple alignment and adjustment procedures.

circuit description

The bandpass input filters These are 3-pole Butterworth design, based on modern

The discriminator When using inductors of the same value for both mark and space, great attention must be given by the designer in order to achieve similar bandwidths, similar voltages, good zero-axis crossover, good noise balance, etc. It becomes even more difficult to design discriminators for both 170 and 850 which can be interchanged in the same overall circuit. Attention to these details has been given to all the Mainline demodulators and the ST-6 is based on the



Front-panel layout of the ST-6 RTTY demodulator.

filter synthesis networks. The one for 850 shift uses normal 88-mH toroids wired in series for 88 mH. It is about 1 kHz wide at the ± 3 dB points. The filter for 170 shift uses 88-mH toroids wired in parallel for 22 mH. (The two outer wires together and the two pigtailed together.) This keeps the impedance of the two units similar. The 170-shift input filter is about 275 Hz wide.

The limiter This is a 709C operational amplifier running "open loop" for maximum gain. It has been frequency compensated only lightly. For a-m reception the gain is reduced so that the unit becomes a linear amplifier at normal input levels, but reverts to a controlled limiter if the input exceeds the normal level.

experience learned from the other units.

The detector Full-wave detection is used, a unique feature of the Mainline ST-series demodulators. This offers optimum detection for easiest filtering of the remaining ripple component. An additional "plus-plus" detector is incorporated for a tuning display and to drive the automatic printer control system.

The lowpass filter The optimum lowpass filter of minimum bandwidth will do more to improve the performance of a demodulator than any other single thing, assuming a high-voltage loop supply is already being used. Vic Poor⁶ pointed out in his outstanding article on RTTY filters that this filter should cut off at

27.3 Hz for 60 speed (45.45) Baud operation, and set up the criteria for testing such filters. The active lowpass filter in the TT/L was built with these features in mind. Fig. 1 shows the curve obtained with the ST-6. The observed "eye pattern" was ideal, indicating optimum cutoff for 60 wpm. The active filter is one that uses feedback circuits with amplification rather than passive components (inductors, etc.). This gives consistent uniformity from one unit to

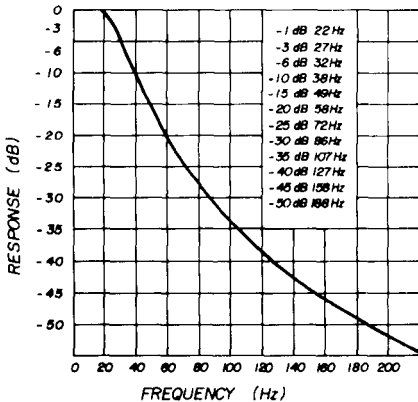


fig. 1. Bandpass curve for the low-pass active filter used in the ST-6.

another, small size, modern design, light weight, low-cost components and freedom from magnetic fields and hum.

The atc threshold corrector This section provides the automatic symmetry needed for the slicer to minimize distortion when using limiterless a-m reception. It also enables mark-only or space-only reception. It is beneficial even with the limiter in use as it offers a form of diversity reception, capitalizing on the redundancy of the mark and space signals. As a good minimum-bandwidth lowpass filter changes square-wave inputs to sine-wave outputs, such a threshold corrector is practically a requirement for proper zero-axis crossover at the slicer.

The slicer This is another 709C operational amplifier running in "open loop"

for maximum gain. It is heavily frequency compensated since the signals handled are at nearly dc. The output of the lowpass filter is so clean and the gain of this stage so high that signals as low as 1 Hz shift will adequately swing the output from full mark to full space. No hysteresis was either necessary or desired.

The control section The output of the slicer is followed by a simple control section that allows a mark-hold voltage to be placed on the keyer stage when there is no authentic RTTY signal, putting it in mark-hold. This same control section allows simple use of the Sel-Cal⁷ unit some enthusiasts have built for autostart purposes. It responds only to their own call letters. The control section is part of the manual standby system.

The loop supply This is a 180-volt supply that gives virtually distortion-free keying of the Teleprinter. A voltage-absorbing network is used on the collector of the keying transistor to protect it against excessive back-emf of the printer magnets which could otherwise occur if two or three printers were used on the same loop supply. The loop also puts out plus-minus voltages at the FSK output for best transmitter keying. It also adapts instantly (with no changes) to the Mainline AK-1 AFSK Keyer⁸ for ssb units. It also offers narrow-shift cw identification.

Normal loop current is approximately 60 mA. This means the selector magnets of the printer and/or reperf should be in parallel. This keeps the inductance in the circuit at 25% the value it would be were the selector magnets in series. If a reperf and printer are to be in the same circuit at the same time, they would then go in series with each other, both having their own selector magnets in parallel. For solid-state keyers the lower the inductance the better due to "spikes" generated by the back-emf of the inductors in a collapsing field.

The power supply This plus-minus 12-volt supply is transistor and zener-regulated for good stability. It is heavily fused to

prevent any damage during long periods of unattended operation and is bypassed for rf.


The anti-space circuit A "blank" key has the longest continuous amount of space time of any RTTY character, about 132 milli-seconds. Any space signal longer than this cannot be RTTY. The anti-space system samples the mark-space output of the slicer. If the signal goes to space more than 132 ms the system says "tilt" and locks the printer to mark-hold, at the same time turning the automatic printer control off and starting the countdown on motor delay cutoff. Thus, if a person is checking his shift at the other end, your printer does not sit there running "open." This also gives greatly improved protection from a non-RTTY signal in the space channel from activating the automatic printer control and turning the motor on. This system works just as effectively with the limiter on or off, with the autostart on or off and with straddle tuning of any shift. No provisions for disabling it were provided. If this were needed, a switch to short the base of Q7 to ground would be suitable.

Tuning meter Although labeled as optional this is a most worthwhile device. Many amateurs prefer a scope for tuning, but this type of meter gives satisfactory results. It is better than most scope displays for straddle tuning where the incoming signal is not very accurately adjusted for correct shift, i.e. the operator might be using 600 shift, thinking it was in reality 850. The tuning meter is also helpful in adjusting the ST-6, although any voltmeter can be used for alignment.

Automatic printer control This system is normally called autostart. It is a unique squelch system that responds only to authentic RTTY, or to a steady mark carrier. A steady space carrier will not affect it due to the anti-space system. It samples both the mark and space channels for a signal having a duty time in excess of about 75%. Since most cw has a duty time of less than 50%, and most voice signals a duty time of perhaps under

30%, this system responds almost exclusively to RTTY signals.

To get the 75% duty time requirement an analog charging circuit is used. Since this is based on fm squelch principles, the use of limiterless a-m is not compatible with this system and is disabled if the limiter is turned off. Since momentary static crashes, deep fades and other temporary interference could cause the system to decide there was no longer any RTTY present, a one-second delay is incorporated into the shut-off feature. This in turn requires about a 3 to 4 second turn-on delay to obtain 75% recognition. Other ratios are shown in **table 1** for those who may wish to experiment.

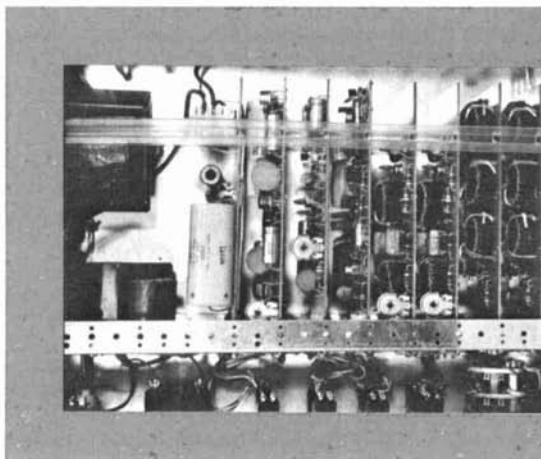

Internal construction of the ST-6 built by the author. A total of eight printed-circuit boards are used.

The higher ratios (like 8:1) will only respond to the very best RTTY signals and will not try to copy those signals that would normally produce garble, but would lock up if the signal deteriorated momentarily. Perhaps their biggest disadvantage is the long turn-on time: 6 to 7 seconds. This is the equivalent of about a half-line of RTTY.

The system used for automatic printer

table 1. Autostart ratios which may be used for protection from printing garble from marginal signals.

ratio	duty time	R61	R59	R60	time to on	time to off
2:1	67%	5.1k	390	4.7k	1.80	.88
3:1	75%	3.6k	2.4k	4.7k	2.48	.84
3.3:1	77%	3.6k	2.7k	5.1k	2.74	.86
4:1	80%	3.3k	3.9k	6.8k	3.53	.87
5:1	83%	3.0k	5.1k	6.8k	4.16	.84
6:1	86%	3.0k	6.8k	8.2k	5.25	.88
7:1	88%	3.0k	9.1k	9.1k	6.38	.90
8:1	89%	3.0k	10k	11k	7.35	.93

control in the Mainline series is unique in that it requires no special call-up or turn-off characters. As a result, it is extremely useful for normal RTTY QSOs where autostart itself would not be considered by the operator. In this case automatic printer control is a more vivid and realistic description of the system than autostart.

Motor delay This feature allows the automatic printer control to place the printer in mark-hold without turning the motor off. During poor conditions, it is a nuisance to have the motor turning on and off. During fast break operation the motor could turn off if it took more than approximately one second for the other station to respond. Also, the FCC requires cw identification between transmissions, and this would normally cause the motor to turn off if no delay system were used. The motor delay in the ST-6 keeps the motor running for 20 to 30 seconds after the autostart system thinks there is no further RTTY present.

Loop supply cutoff A feature is incorporated in the ST-6 that opens the loop supply to space whenever the motor relay turns the motor off. Otherwise there is some 10 watts of heat in the cabinet from the 2750-ohm, 20-watt loop-current regulating resistor. This is not detrimental, but serves no useful purpose, and consumes an additional 10 watts of unnecessary power when the printer is not running.

Fuses The ST-6 probably has more fuses in it than any other item in your entire station. They aren't all *necessary*, but for unattended operation good fusing is worthwhile. Receivers, transmitters and other electronic items have been known to develop partial shorts in the high-voltage secondary systems, destroy components which may occasionally catch on fire, ruin transformers and *still not blow the fuse* in the primary! This is often because the secondary has several windings. By merely fusing the primary, it is hard to select a fuse that will quickly blow if the secondary pulls excessive current in *one* of the windings.

Thus the ST-6 fuses each secondary winding as well as the combined primaries. The jack for the motor is not fused (and should not go through the on-off switch) since the printers have their own protective fuses. The relay handles the motor current.

On the printed-circuit boards from Halle,* the indicator lamps also run through the fuses. In the event you add those lamps, you may find it necessary to increase the size of the fuses somewhat.


Rf protection The operational amplifiers have such fantastic gain that precautions should be taken to prevent amplification of nearby rf signals, because their usefulness is destroyed while that rf is present. The ST-6 bypasses the 120 Vac input line, the power supply output, and isolates the plus-minus voltages to each op amp to prevent any instability or oscilla-

tion. Thus, no adverse affects have been noted from nearby kilowatt transmitters.

Scope connections Provisions have been included for connecting an oscilloscope, the 1 megohm isolating resistors provide adequate protection against the low-impedance scope inputs from affecting discriminator balance. If you incorporate a scope it should be an external unit that plugs into the rear of the ST-6. This allows the scope to be used for other demodulators, to be larger than the 1" or 2" display the ST-6 cabinet might allow,

ables the autostart (turns the motor on and keeps it on). There is also a jack for an external remote standby switch, Fig. 2 shows how this can be used. Switches S10 and S11 would be placed at or on the printer itself; S10 as a standby switch and S11 as the transmit control switch. This not only automatically turns the transmitter on, it mutes the ST-6 so incoming signals for the tuning meter or scope do not affect the transmitted signal – without this provision acoustical feedback could cause incorrect signals to be transmitted. By placing these two switches

fig. 3. Simple lamp circuit to indicate standby and receive. Resistors marked with asterisk are selected for normal lamp current.

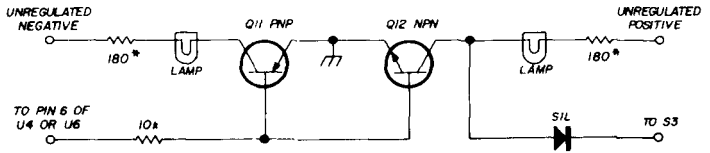

and allows the operator to run the ST-6 twenty-four hours a day for autostart.

the switches

S1 is a dual-purpose switch to change the unit from fm to a-m reception. When in a-m limiterless, it also disables the autostart system, putting the motor automatically to *on*.

S2 is the normal-reverse switch. It is not necessary, but there are rare occasions when a newcomer is "upside-down" and you may want to see who it is. Many people will leave this switch completely off their unit.

S3 is the local standby switch. This places the printer in mark-hold and dis-

ables the autostart (turns the motor on and keeps it on). This offers maximum versatility plus simple fast-break operation.

S4 is the fast-slow autostart; it also turns the motor on when in *fast* and keeps it on. The *fast* system uses the same ratio of turn-on to turn-off times, but speeds them both up. This makes it convenient to use automatic printer control for fast break, but gives inadequate protection against momentary signal loss during unattended operation.

S5 merely turns the automatic printer control off, allowing manual operation via the standby switch S3 or S10. (S10 is not shown on the schematic, it is shown on fig. 2.)

S6 is the manual motor *on* switch. It keeps the motor running regardless of any other switch position except the power off switch, S7.

S7 turns the 120 Vac power on and off, and opens the FSK line when in off, to prevent any hum loops from the FSK keyer in the transmitter. This could be annoying when using voice or normal cw if the ST-6 were in the off position. This is normally no problem, but the switch is

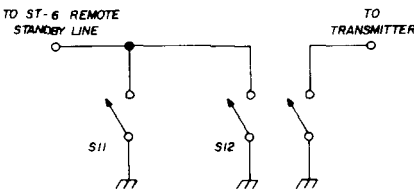


fig. 2. Station switching. S11 and S12 normally located near printer. Standby switch S11 keeps machine from printing; station control switch S12 puts the transmitter on the air and mutes the ST-6 for local copy.

available for this purpose if you want to use it.

standby-receive lamps

Fig. 3. shows how lamps may be added to indicate standby and receive. When the manual or remote standby switch is activated the standby lamp turns on, whether the receive lamp is on or not. The receive lamp works only from the output of the automatic printer control system.

Thus it is possible to have both lamps on at the same time. This tells the operator he has selected manual standby. As a result he is informed that he is not in automatic reception mode at all, and before leaving the room he must turn off the standby switch (S3 or S10) if he expects to get automatic copy. It makes an excellent fail-safe reminder.

If you prefer an indicator for mark and space signals, attach the 10k resistor in fig. 3 to pin 6 of U4. In this case the diode on the collector of Q12 is removed.

850-170 switch

If incorporating both 850 and 170 shifts, duplicate the front end up to but not including the first 16k resistor on U3. Then a multipole two-position switch would be used to switch the audio input,

*Printed-circuit boards and complete parts kits for the ST-6 are available from several sources, including Hal Devices, Post Office Box 365, Urbana, Illinois 61801. This firm offers various options and has a brochure available on request. The printed-circuit boards are designed for the 14-pin dual-inline op amps. Hal Devices also have a unique power transformer available that has windings for both the loop voltages and plus and minus dc supplies.

For Canadian builders, arrangements have been made with Space Circuits Ltd. to provide printed-circuit boards for Canadian amateurs. Write to Hugh Watt, VE3HY, President, Space Circuits Ltd., 156 Roger Street, Waterloo, Ontario, Canada.

the output of the two U2 stages, the output of the U1 limiter for the limiter-less a-m mode, and the two 47k resistors on the inputs to the U1 stages. The scope display for mark and space probably should be switched as well as the output to the meter and autostart at point 2. Other poles can be used to ground the audio input of the unused limiter off. I used a two-section (6 poles per section) two-position ceramic switch.

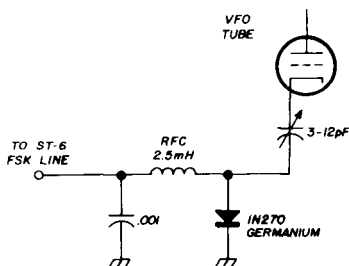


fig. 4. Circuit for adding frequency-shift keying to your transmitter. If your signal is "upside down," turn the diode around.

construction

The unit shown in the pictures uses printed-circuit boards. There are six different boards. For both 170 and 850 shift the first two are duplicated, making a total of eight.* The boards are laid out by function as follows:

1. Bandpass input and limiter U1.
2. Discriminator and U2.
3. Lowpass filter, slicer, keyer and anti-space.
4. Autostart, standby, meter, delay system.
5. $\pm 12V$ volt regulated power supply, lamp drivers, meter driver Q10.
6. Loop supply (and room for motor relay).

Room for all parts is included on the boards except for the control switches, meter and the two transformers. The boards are approximately $2\frac{3}{4}$ inches high by about 6 inches long and plug into 12-pin connectors such as the Amphenol 143-012-01. This is not only neat appearing, it allows the boards to be removed easily for other shifts or to try various


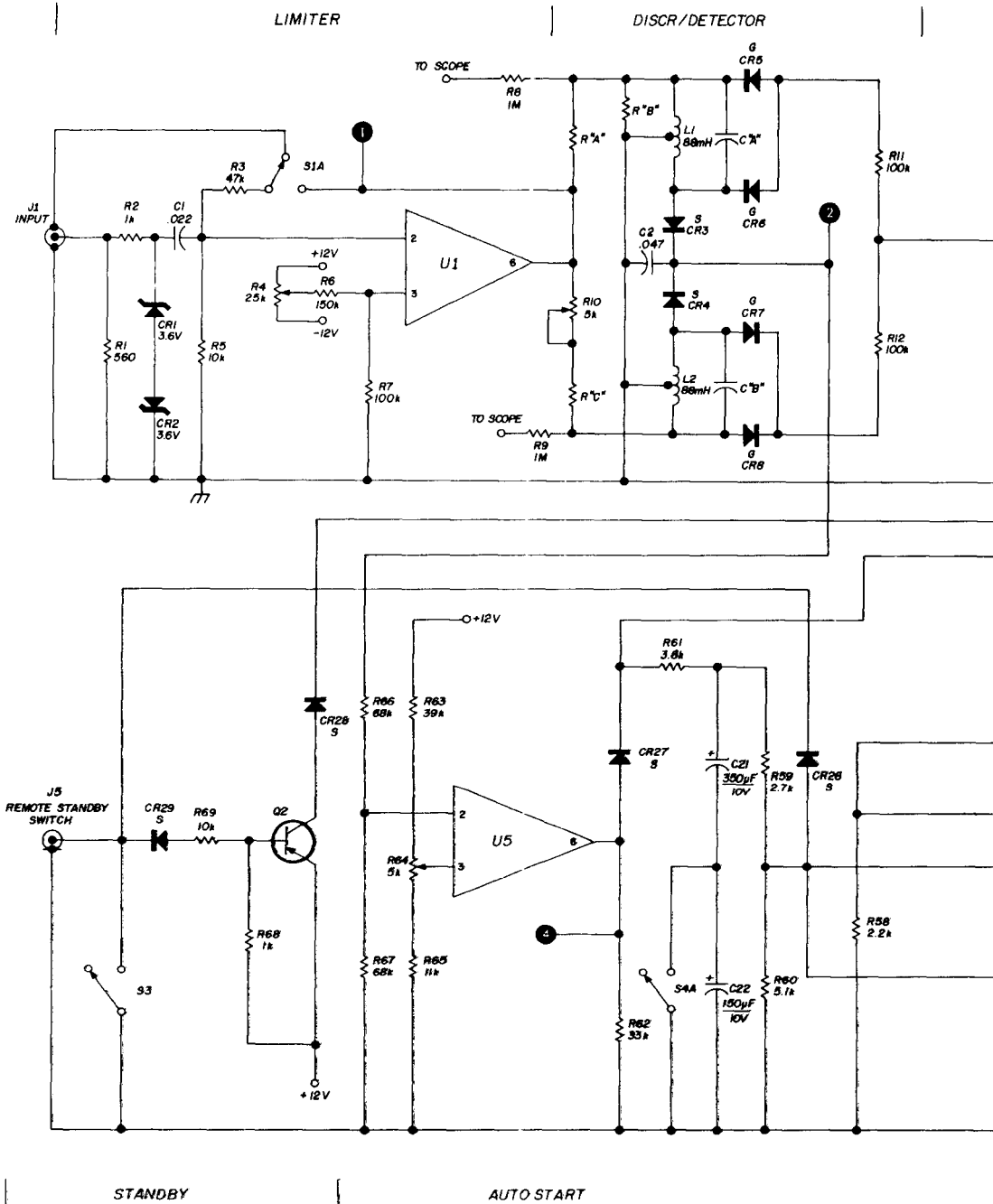
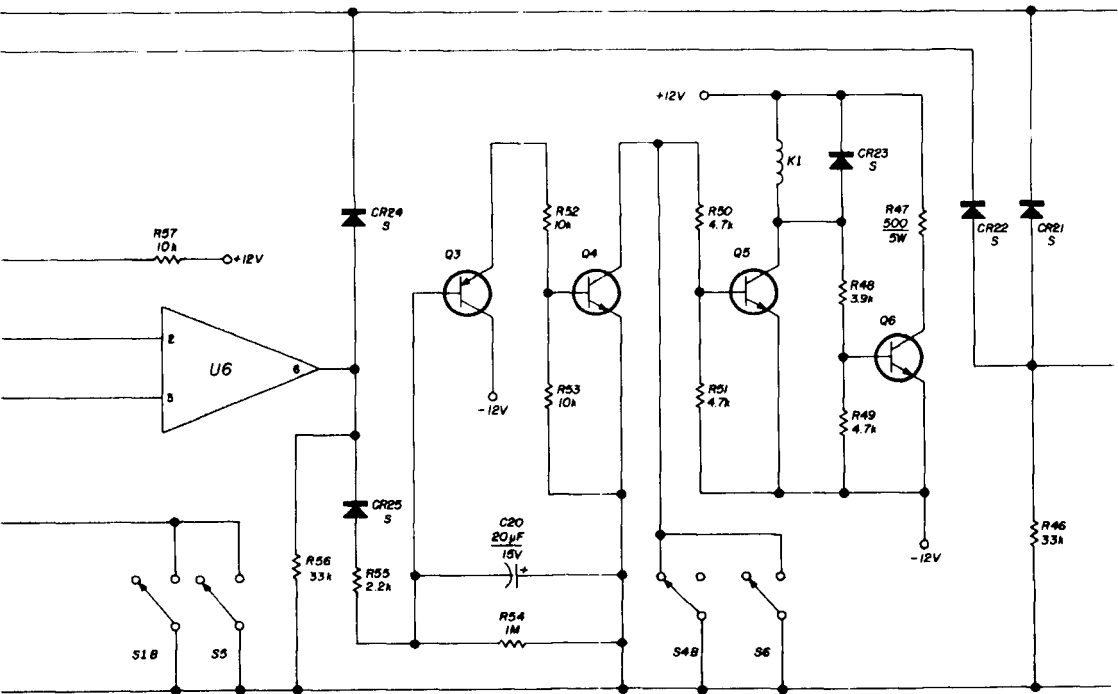


fig. 5. Schematic diagram for the Mainline ST-6 RTTY terminal unit. Contacts on relay K1B open the loop when the motor is off.

LOW-PASS FILTER

ATC

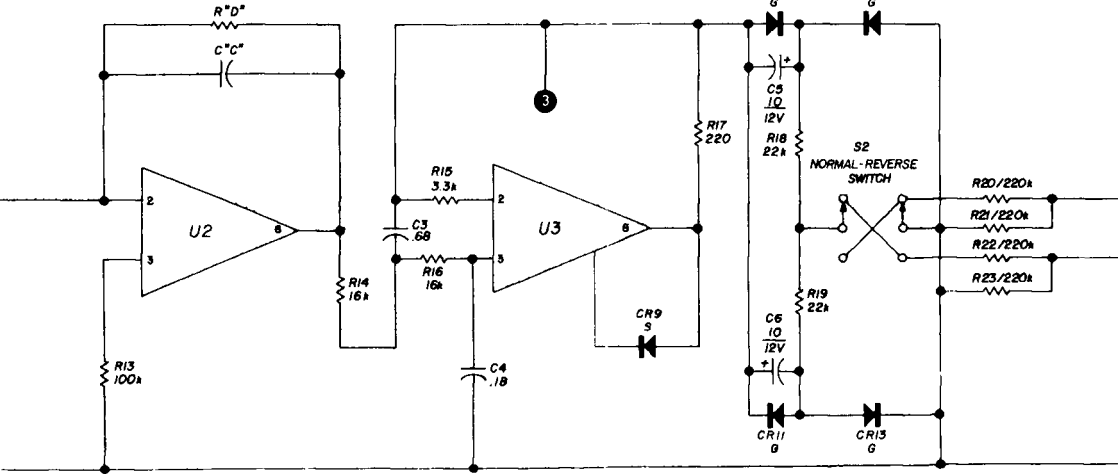


AUTOSTART

SLICER

KEYER


LOOP

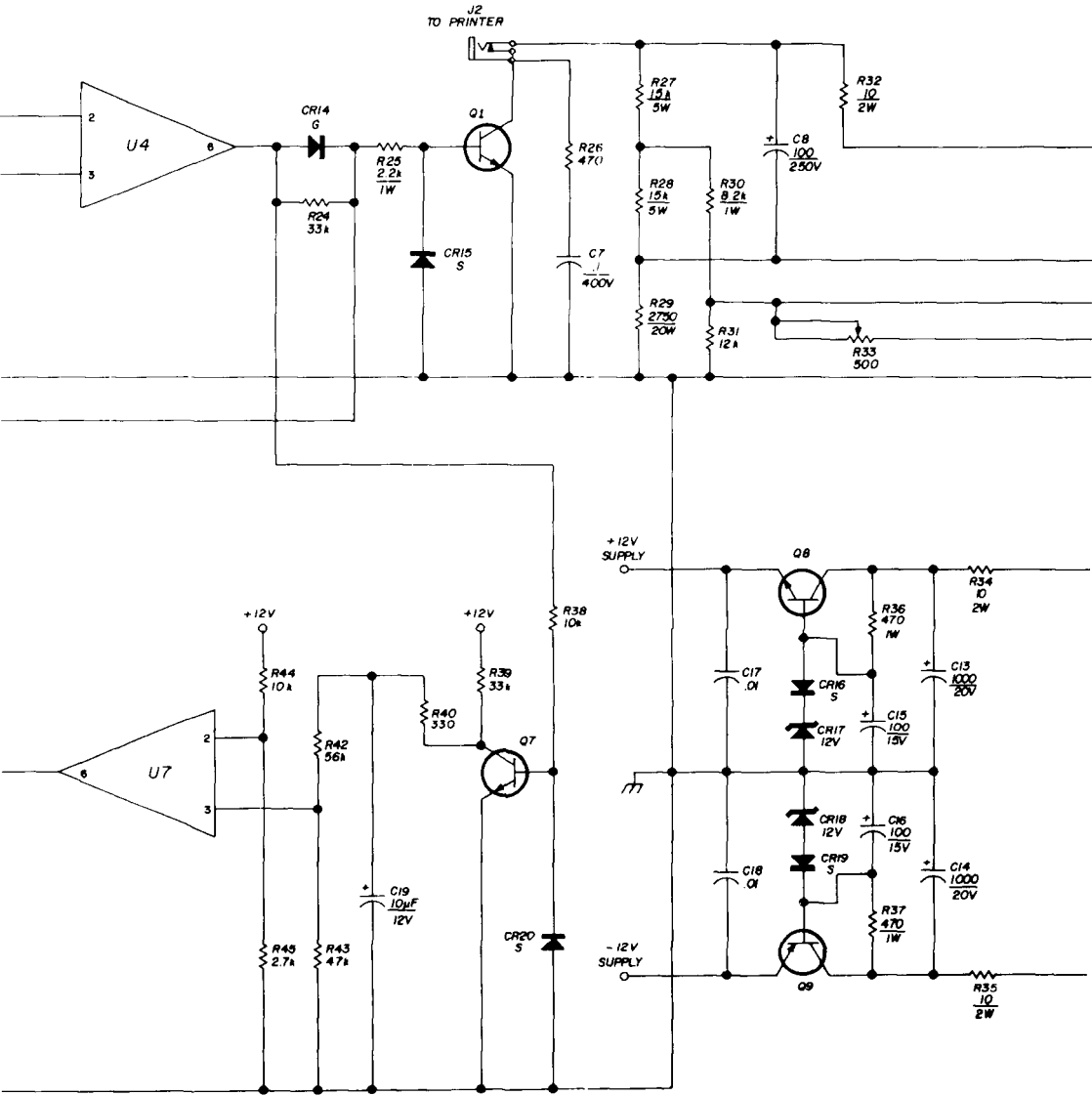

ANTI-SPACE

POWER

SLICER

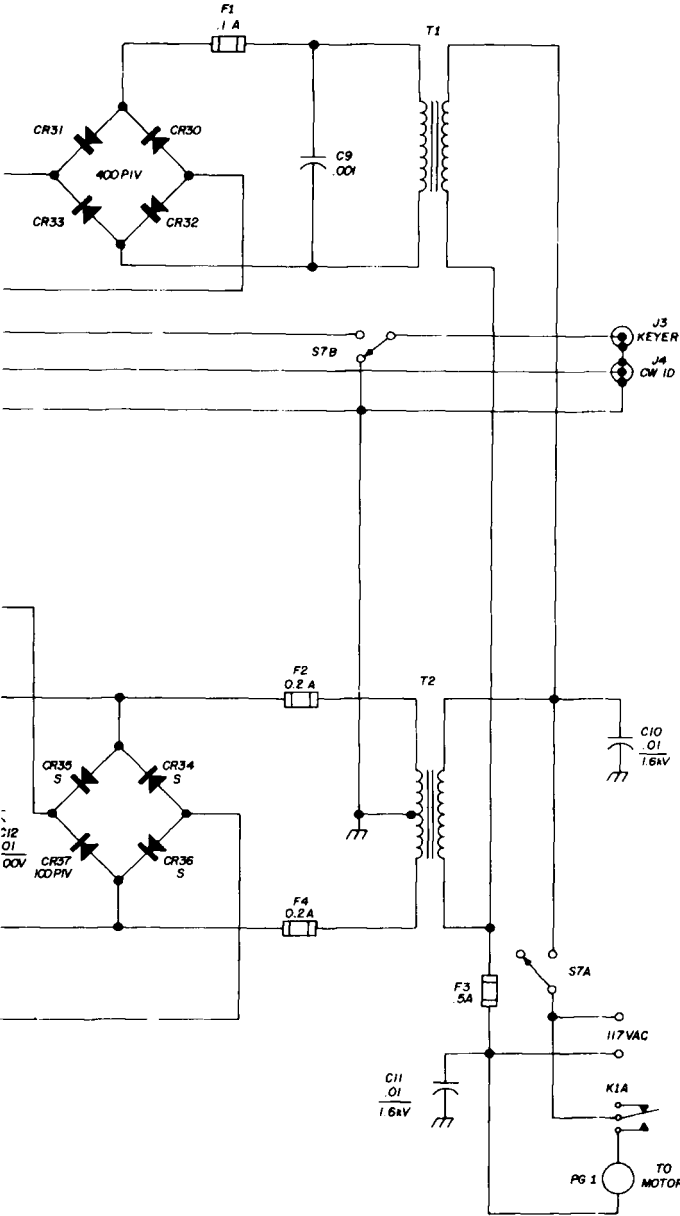

SUPPLY

- S1 limiter on-off, also disables autostart
 - S2 normal-reverse switch, keep wiring short
 - S3 standby, also turns motor on
 - S4 fast-slow autostart, fast keeps motor on
 - S5 autostart off, keeps motor on
 - S6 manual motor on
 - S7 power on-off, also ground fsk line when off
- T1 isolation transformer, 115 Vac, 0.3 A (Triad N-51X)
- T2 filament transformer, 28.6 Vac, 1 A (Triad F-40X)
- Diodes marked "G" are 1N270 germanium.
- Diodes marked "S" are silicon, 50 piv unless otherwise noted

discriminator values

	170	850
R'A'	6800	4700
R'B'	100k	33k
R'C'	6800	6800
R'D'	270k	180k
C'A'	.068	.068
C'B'	.056	.033
C'C'	.02	.03

Large schematics are available directly from the author for easy-to-follow construction. \$1 in USA or Canada, \$2 US for airmail elsewhere.

circuit changes the operator may wish to experiment with.

The unit shown in the photos was built into a 10 x 12 x 3 inch chassis, and covered with shelf paper from the local dime store. This makes an attractive way to cover the aluminum chassis and provides an excellent base for rub-on labels.

No shielded lines were used except to the external scope jack. The normal-reverse switch should be as close as possible to board 3 to keep the leads short. The connectors and switches were all wired before placing them in the chassis.

are S1, S4, the receive lamp, the standby lamp, the tuning meter and the power-on indicator. The latter is superfluous if you have either the meter or the indicator lamps. On the bottom row are S2, S6, S5 and S3, and in the bottom right-hand corner, S7.

On the rear from left-to-right are the remote standby jack, remote scope jack (2-way type), audio input (600 ohms), printer motor, FSK output, fuse, and 120 Vac input.

No cw identification jack was provided as I normally hook that into the fsk line

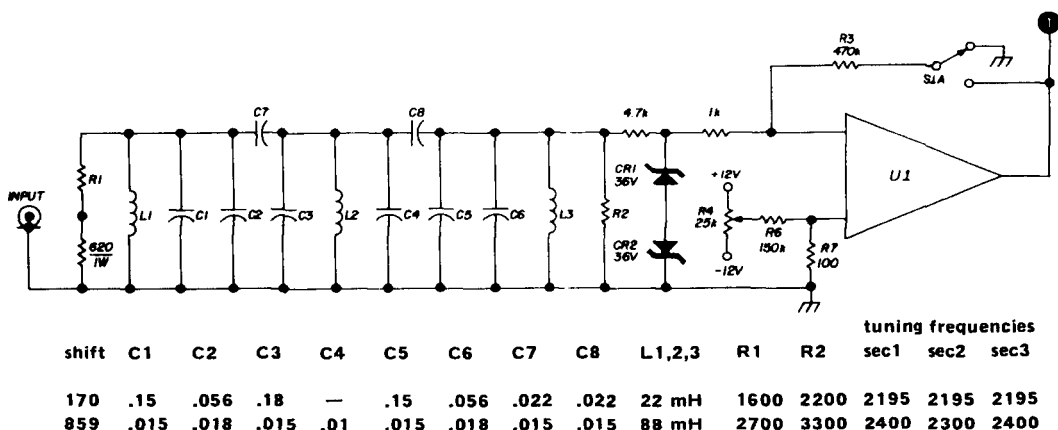


fig. 6. Optional bandpass input filter.

Adequate spacing is 1" between boards, with board 6 (loop supply) facing the open air with its 2750 ohm, 20 W resistor. This board would be somewhat more than 1" wide when all the parts are mounted.

The printed-circuit boards sold by Halle have transistor connections for Motorola transistors. The Q1, Q8 and Q9 transistors have connections that differ from the others. If you use RCA or GE transistors, be careful to install them properly. About 0.4 watt will be dissipated through Q8 and Q9.

panel layouts

In case you cannot read the printing on the photos, the 170-850 switch is at the far left. Next to it on the upper level

externally, but another jack could be provided as suggested in the schematic.

tuneup

The ST-6 is very simple to align, and once done, should not require any further attention. No pots are located on the front or rear panels. Complete alignment is as follows:

1. Unhook the audio input. Place a dc voltmeter at test point 1 on pin 6 of U1. Adjust the 25k pot on pin 3 of U1 so the meter reads zero. This is a very touchy adjustment due to the high gain of the 709C op amp, so get it as close to zero as is convenient and leave it - this adjusts the offset input balance which allows the op amp to run at its maximum gain level.

2. Either move the dc meter to test point 2 on the discriminator or observe the tuning meter on the front panel. Connect audio to the ST-6 and tune between mark and space signals, adjusting the 5k pot on pin 6 of U1 for equal readings on the meter. This balances the discriminator.

3. If using the tuning meter, with maximum mark indication, adjust the meter sensitivity pot on the emitter of Q10 so the meter reads 70% full scale. Hopefully it will have markings each 0.1 of full scale. Now detune the input frequency to the point where the meter reads 60% of full scale. Place the voltmeter on test point 4 on pin 6 of U5. Adjust the 5k pot on pin 3 of U5 so the voltmeter cannot decide to stay positive or go negative. This sets the autostart sensitivity to approximately ± 3 dB bandwidth — about ± 45 Hz for 170 shift and about ± 100 Hz for 850 shift. If both discriminator boards have been included, set this adjustment in the 170 shift position and take what you get for 850 (850 is much less critical than 170 shift).

If a tuning meter was not incorporated on the front panel, use a voltmeter at test point 2. Tune for maximum mark and note the meter reading. Multiply this by 85%, and retune the input frequency for this new meter reading. Then proceed to adjust the pot on U5 so the voltage at test point 4 cannot decide if it should stay positive or go negative.

tuning the filters

Access to a digital counter makes this job very simple. The Mainline TT/O semi-counter⁹ also makes the job very easy. That unit is low cost and hooks to an existing oscilloscope but is quite accurate when compared to anything but a true digital counter. The values of the capacitors in parallel with the toroids in the bandpass input filters and discriminators are only approximate. With toroids that can vary 2 to 3% and capacitors that

are $\pm 10\%$, you can miss the desired frequency by as much as 150 Hz.

When tuning the bandpass input filters, a review of my filter article might be of interest.¹⁰ Basically the procedure is as follows:

1. Disconnect the input and output lines.
2. Disconnect the resistors at input and output of the filter.
3. Short out the center toroid with a piece of wire.
4. Tune the first section.
5. Tune the third section.
6. Remove the shorting wire from the center section and short the first and third toroids to ground.
7. Tune the center section.
8. Remove all shorts.
9. Connect the resistors.
10. Connect the input and output lines.

Room has been provided on the circuit boards for as many as three tuning capacitors for each toroid. This should allow easy, precise tuning without adding or removing turns of wire from the toroid.

The coupling capacitors on the bandpass input filters (C7 and C8) should not be changed from those indicated.

A good method for final checking of discriminator tuning is to put a meter at test point 2 and tune for maximum. Then tune off on the high side to a slightly lower meter reading, note that frequency; tune for the same reading on the other side of center and note that frequency. Average the two to get the best center frequency and change as needed to get the frequency you want.

low tones

This is a subject that is difficult to discuss as part of a demodulator article. Mark tone is customarily 2125; space tone is customarily 2295 for 170 shift or 2975 for 850 shift. Years ago, when these tones were selected good mathematical reasons were used. They are an excellent compromise between channel separation for harmonic suppression and adaptability to communications receivers.

table 2. Components for low-tone discriminators.

	170 1275/1445	850 1275/2125
R'A' (R1)	2.7k	1.5k
R'B' (R2)	27k	8.2k
R'C' (R3)	2.7k	2.2k
R'D' (R4)	240k	160k
C'A' (C1)	.18 μ F	.18 μ F
C'B' (C2)	.12 + .018 μ F	.068 μ F
C'C' (C3)	.022 μ F	.033 μ F

Many ssb receivers use 2100 Hz audio filters in the *i-f* and are limited to the range of 300-2400 Hz. Thus, many operators complain that they cannot receive the 2975 tone and assume there must be more appropriate audio tones. Many operators feel that 1275 and 2125 would be suitable. These tones *can* be used and for several years I used them on my 75S-1 receiver and Electrocom demodulator.

However, they are not recommended, particularly if a linear discriminator is used in the demodulator to separate mark and space tones after the limiter.

It is very simple with most receivers to change the bfo frequency with a new crystal so that an audio range of 1400-3500 Hz is obtained instead of 300-2400 Hz. The Collins S-line, the Heathkit SB-line and many others require only a new bfo crystal about 1 kHz lower than that normally used for ssb reception.

The Collins 75A4 and most Drake receivers have passband tuning which automatically allows reception of tones in excess of 3 kHz.

Component values for discriminators for 1275-1445 shift and 1275-2125 shift are shown in table 2 for those who wouldn't build the ST-6 otherwise. No bandpass input filters have been designed for these shifts nor are any contemplated.

relay circuit

Just a word about an unusual feature - Q6 has a 500-ohm resistor in its collector circuit. Q6's only purpose is to afford a similar current drain on the power supply when the relay is not being used, hence voltage regulation is materially aided. This can be omitted if you are not a purist.

The 47k resistor on U1 was picked for limiterless operation, *without* the bandpass input filter. If using the filter, you will want to change this resistor to a 470k (or whatever value gives adequate meter indication) when running limiterless and using normal audio level on the receiver.

controlled limiting

In limiterless operation if the audio input is more than is needed to reach

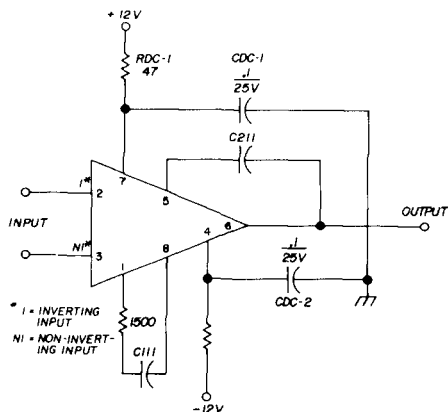


fig. 7. All operational amplifiers used in the ST-6 must be compensated and decoupled as shown here. For U1, C111 is 47 pF and C211 is 3 pF. For integrated circuits U2 through U7, C111 is .005 μ F and C211 is 200 pF.

normal meter reading, then the unit goes into modest limiting, sometimes called controlled limiting. This is no longer linear a-m, nor is it hard limiting for fm, but somewhere in between. Some people feel this gives excellent results, but of course you need sharper filters than a linear discriminator offers to take full advantage of any limiterless mode.

cost

The approximate cost using all new parts is \$100 for one shift, using vector boards and no PC boards. With both 170 and 850 shift, using the drilled PC boards with connectors, the new-item cost should be around \$150.

parts suggestions

Meters may be obtained for as low as

\$2.98 from Radio Shack. That is the meter shown on the ST-5. It did a nice job. The one shown on the ST-6 is an imported *Micronta* movement.

The op amps are the 709C types, and Motorola, Fairchild, Texas Instruments, National Semiconductor, and Signetics all make them. The PC boards were made for the round TO-5 type that has eight leads. Prices are dropping constantly. They were \$12 each when I first started using them, but at the time this article is being written they are \$1 each in small quantities.

The pots used for the PC boards are the 39¢ Mallory MTC-L1 type for vertical

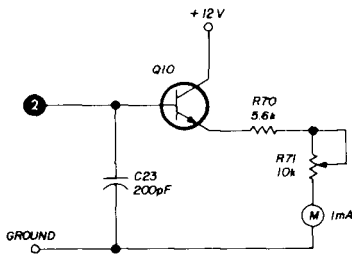


fig. 8. Optional tuning meter for the ST-6.

mounting. IRC type X-201 at 39¢ are similar.

Any 24 Vdc dpdt relay should be adequate. The resistor on the collector of Q6 would be chosen to have the same value as the dc resistance of the relay, such as the Potter and Brumfield KA11DG at \$3.90.

The small 0.1 μ F 25V capacitors used on each op amp can be the 21¢ Sprague HY-550. Both Centralab and Sprague make 1.6 kV ceramic capacitors used for bypassing the 120 Vac line. The other small value capacitors can be Sprague *Orange Drop* Mylar types, 75 V where obtainable, to keep the size small. Typical price 18¢. The 10-, 20-, 150-, and 350- μ F capacitors can be Sprague type 30D. The large 100- and 1000- μ F types can be Sprague TVA.

Diodes marked *G* are 1N270 germanium; those marked *S* are silicon with 50 volts PIV except in the loop supply where

400 PIV minimum are needed. The zener diodes can be 400 mW or more, preferably 1 W in the power supply.

Transistors are not critical except in a few places. Q1 should be rated for at least 300 volts; the Motorola MJE-340 is recommended (\$1.06). The MJE-340 can also be used in the power supply for Q8. An MJE-370 can be used for Q9 as well as many other types handling 5 W or more — these two being 25 W types. The other transistors can be literally any that are rated for at least 15 volts or more. Those for Q5 and Q6 should be rated at 30 volts or more.

Recommended low-cost transistors for Q2, Q3, Q4, pnp, MPS-3703 (39¢); Q5, Q6, npn, MPS-6565 (52¢); Q1, Q8, npn, MJE-340 (\$1.06); Q9, pnp, MJE-370 (\$1.07); Q7, Q10, npn, MPS-3394 (27¢); Q11, pnp, MPS-6518 (67¢); and Q12, npn, MPS-3395 (45¢).

The Stancor PA-8421 makes an excellent loop transformer. Other 24 Vct, 0.5 A units should be suitable for the power supply.

The lamps should be low current types, hopefully under 50 mA. Those shown are the Sylvania 925 cartridge indicator lamps using 15 to 20 mA. If you use lamps that pull 80 mA each, change the 10k resistor to the bases of Q11 and Q12 to 4.7k.

The Muralite L-28/40 indicator is ideal for the ST-6. This lamp is rated at 10,000 hours life and may be used with voltages from 12 (25 mA) to 28 (40 mA). They are 39¢ each from: Western Radio, 1415 India Street, San Diego, California 92101; Attn: Gary Pierce Amateur Store Manager.

They are available in violet, red, white, green, blue and amber. Gary suggests you specify "violet leads" as this apparently identifies the L-28/40 bulb, not the color of the lens. These lamps are complete and are normally distributed through the Mura Corp. 355 Great Neck Road, Great Neck, New York 11021. The Sylvania lamps will run around \$2.25 each by the time you get the cartridge lamp, lens and holder.

The 709C op amps are now only \$1.00

each from Texas Instruments distributors in the 14-pin dual-inline style, and \$1.25 for the round 8-pin TO-5 style. By the time this article appears in print it is possible prices could be even lower; as of now the other brands cost about \$2.60 each. Texas Instruments uses their own designations for the 709C op amp: SN72709N for the 14-pin dual-inline package and SN72709L for the TO-5 can.

performance

The ST-6 outcopies any other demodulator I have tried. It does not run away from the TT/L-2, but the ST-6 seems to do better *most* of the time. Other operators who have built the ST-6 report similar experiences, and one enthusiast sold both his TT/L-2s and has replaced them with ST-6s. The unit only pulls 5 to 7 watts in standby when the motor is off, so it can run 24 hours a day without affecting the monthly electricity bill. The convenient switching system makes it very simple to use.

The ST-6 is designed for 600-ohm input. Most receivers have such an output available somewhere (on the Collins S-line it is the anti-vox jack). In some receivers, such as the Drake, there is no 600-ohm output. You will throw away about 30-dB potential limiting in the ST-6 if you use the 3.2-ohm speaker line, but small 3.2-ohm to 600-ohm transformers are available for under \$1 from most distributors.

other op amps

Some people have asked why I did not use newer, more exotic op amps. Most of the newer devices are internally frequency compensated (such as the 741, for example), and not at all suited for audio use. They have other excellent qualities and could be used in the ST-6 at places other than U1 and U2. Their cost is such that even with external compensation, the 709C is still cheaper. The 709C already has so much inherent potential performance it would be similar to running the TT/L-2 with perhaps 7500 volts on the plate of each tube.

100 speed

For those needing 100 speed, change the two 16k resistors at the input of U2 to 10K, and change the capacitor between pins 2 and 6 of U2 to 60% of its usual value. That is, for normal 60 speed with the 850 shift discriminator for 2125-2975, the normal 0.03- μ F capacitor would be changed to 0.018 μ F.

The unit would then receive 60, 75 and 100 speed. Do not attempt to switch these items around, just leave it for 100 speed.

conclusion

The ST-6 offers the RTTY enthusiast a high-performance solid-state demodulator. It has features similar to those in the Mainline TT/L-2 but with greater inherent capabilities. It has automatic printer control which is useful for unattended autostart operation as well as for normal QSOs. Printed-circuit boards are available which simplify the construction and make it possible for the home enthusiast to make a commercial-looking unit with only simple tools.

references

1. Irvin M. Hoff, K8DKC, "Getting Started on Radioteletype," *RTTY*, January, 1963, p. 3.
2. Irvin M. Hoff, K8DKC, Keith B. Petersen, W8SDZ, "The Mainline TT/L FSK Demodulator," *QST*, August, 1965, p. 27 (also *RTTY*, November, 1964).
3. Keith B. Petersen, W8SDZ, "The Mainline TT/L-2 FSK Demodulator," *QST*, May, 1969, p. 28 and June, 1969, p. 24 (also *RTTY Journal*, September, 1967).
4. Irvin M. Hoff, W6FFC, "The Mainline ST-3 RTTY Demodulator," *QST*, April, 1970, p. 11.
5. Irvin M. Hoff, W6FFC, "The Mainline ST-5 RTTY Demodulator," *ham radio*, September, 1970, p. 14 (also *RTTY Journal*, May, 1970).
6. Victor D. Poor, "Filters for RTTY," *RTTY*, May, 1964, p.2.
7. W. Mallock, WA8PCK, and T. Lamb, K8ERV, "The Selcal - An RTTY Character Recognizer," *73*, May, 1968, p. 58.
8. Irvin M. Hoff, W6FFC, "AFSK for RTTY," *QST*, February, 1969, p. 11.
9. Irvin M. Hoff, K8DKC, "Checking RTTY Shifts," *QST*, May, 1966, p. 35.
10. Irvin M. Hoff, K8DKC, "High-performance RTTY Filters," *QST*, September, 1966, p. 34.

ham radio

NCX-1000

THE 1000 WATT TRANSCEIVER of the 70'S



Pleasure value.....\$1,000,000

- 5 BANDS
- 4 MODES
- SOLID STATE DESIGN

NOW AVAILABLE FROM THE
NEW NRCI AT A
NEW LOW PRICE **\$839.95**

37 WASHINGTON STREET, MELROSE, MASSACHUSETTS 02176
TEL: 617-662-7700 TWX: 617-665-5032



Write for Specifications!

Excellence in Communications Since 1914

NATIONAL RADIO CO., INC.

intermittent voice operation of power tubes

The power capability of a transmitting tube is often the subject of long and heated discussions among amateurs (and even among equipment design and tube engineers). In the past, amazing things have been done to power tubes by daring amateurs who seemingly had an inexhaustible supply of replacement tubes at hand.¹ The tube manufacturer looks upon such goings-on with mixed emotions; he's proud his products can take such a beating, but he shudders at the gross overload he knows is taking place, and he has nightmares when he imagines that such tactics are being done by users who may be ignorant of the basic limitations of vacuum tubes. Sometimes that manufacturer may be his own worst enemy. When he speaks of the ruggedness, long life and reliability of his product, he may unintentionally be inviting some eager-beaver to prove the utter conservatism of his remarks.

Up to now, tube ratings have been based upon an absolute system providing "maximum" ratings and "typical" operating conditions for various classes of service, for use below a certain specified frequency. These ratings are designated as *Continuous Commercial Service* (CCS) and *Intermittent Commercial and Amateur Service* (ICAS). The CCS rating may be defined as, "that type of service in which long tube life and reliability of performance under continuous operating

conditions are the prime consideration."² The ICAS rating is defined to include the many applications where the "transmitter design factors of minimum size, light weight, and maximum power output are more important than long tube life." The term "intermittent" is used to identify operating conditions in which no operating or "on" period exceeds five minutes and every "on" period is followed by an "off" or standby period of at least the same or greater duration.

These ratings are of cold comfort to today's radio amateur. The first rating applies to high-reliability service (broadcast, military, etc.) wherein off-the-air time is critical or costly; and the second rating, by its very definition, excludes amateur operation in meaningful terms. Neither classification, moreover, applies to ssb or cw operation. Ssb and cw are more properly expressed in terms of peak-to-average power ratio rather than in terms of "on" and "off" periods.

Before new and meaningful ratings are proposed for today's operational modes, it would be prudent to look for a moment at transmitting tube ratings now in use and examine their validity. Contrary to often expressed belief, maximum ratings and typical operating conditions are not arbitrary figures dreamed up by the manufacturer to avoid answering legitimate questions posed by users. On the contrary, they are the result of careful analysis of tube geometry and of prolonged life tests run on typical production tubes with some guaranteed or expected life in mind. Properly understood, the maximum ratings and typical operating conditions can be employed by

William I. Orr, W6SAI, EIMAC Division of Varian, San Carlos, California 94070

the tube user to decided advantage.

transmitting tube ratings

Maximum ratings (or absolute maximum ratings) are those limits within which all tubes of a given type should give satisfactory service and long useful life. Why they are necessary at all and how they are determined are discussed in this article.

The *data sheet* (often suspected of being written by the wise to impress the humble) informs the user of the capabilities and limitations of the tube, both of which are based upon the maximum temperature the elements of the tube can safely withstand for an expected life. Heat, then, is the enemy of unlimited tube life, but heat is the unfortunate consequence of making the tube work. Once the maximum tube capability is determined *a compromise of some kind must be made to establish useful life without exceeding the heat limitations, yet allowing some safety factor for "cockpit troubles."*

maximum plate dissipation

Plate dissipation is limited by the maximum safe temperature of the plate and plate-to-glass (or ceramic) seals of the tube. Generally speaking, the plate will withstand several times its maximum rated dissipation level for a short period of time. Other parts of the tube (glass envelopes, mainly) are greatly affected by the excessive heat radiated by the plate. High level of plate temperature may cause the grid, filament or envelope to become overheated. The grid structure may warp, the filament temperature may rise to an excessively high degree, or the tube envelope may be destroyed. These effects, however, are not instantaneous, and short periods of plate overload do not usually overheat the adjoining tube structure to a damaging extent. However, the user has no way of telling to what degree he can safely exceed the plate dissipation limit, or over what period of time this abuse can take place. The obvious conclusion is that the maximum plate dissipation rating should not be exceeded in

continuous operation if long tube life is desired.

maximum plate voltage

The maximum plate voltage point is set at a value above which the internal or external insulators of the tube may arc over, or above which the envelope of a glass tube may be damaged from dielectric losses. Finally, a plate voltage ceiling tends to set a limit to the maximum rf charging current flowing in the plate and screen leads, or plate and grid leads in grounded-grid service. The charging current is a function of the rf plate voltage which, in turn, is a function of the dc plate voltage. Setting a limit on the dc voltage sets a limit on charging current without the difficult task of determining the current directly. This effect depends on frequency and is the reason for the upper frequency limit for maximum ratings.

average dc plate current

The fundamental limit on plate current is the available supply of electrons emitted by the filament or cathode of the tube. The maximum plate-current figure is intended to set a value which may be easily realized throughout the expected life of the tube. If operating conditions are chosen which require that the maximum plate-current limitation to be exceeded at the start of tube life, it may become increasingly difficult to maintain the desired value of plate current as the tube ages. There is a definite relationship between the *maximum instantaneous value* of plate and grid current and the *average dc* (meter reading) *plate current* which differs for each class of tube operation. In linear-amplifier service, for example, most transmitting tubes are run class AB₁, AB₂ (loosely termed class B).* In these cases, the peak plate current is about three times the indicated (average)

*Most class-B linear amplifiers are operated in class AB₂. Class-B operation is defined as cutoff operation with an 180° operating angle of plate current flow. Class AB₂ operation signifies less-than-cutoff condition with more than 180° operating angle.

dc plate current. For long life, the cathode emission should be great enough to provide two or three times the required peak value of plate, plus grid, plus screen current.

The user can quickly determine the allowable average dc plate current in linear service for thoriated tungsten filament-type tubes by merely multiplying the filament watts by a factor of about 5.5. This is a rule-of-thumb number that — over the years — has proven to give a conservative balance between allowable plate current and good tube life. For the 3-500Z, therefore, the filament power is 5 (volts) x 14.5 (amperes) = 72.5 watts. Therefore, allowable maximum average dc plate current for linear amplifier service is $72.5 \times 5.5 = 400$ milliamperes.

In the case of an indirectly heated cathode the rule-of-thumb is different. Emission from an indirectly heated cathode depends upon the emissive material and the active cathode area, assuming cathode temperature is the proper value. The rule-of-thumb in this case for oxide cathodes is that maximum average dc plate current is approximately 125 milliamperes for each square centimeter of cathode area. For example, the 4X150A tetrode has an active cathode area a little over 2.0 square centimeters and the average dc plate current rating is 250 milliamperes.

long pulse service

In pulse service where the "on" time is small compared to the "off" time, many transmitting tubes can be run to much higher peak power limits than are permissible in continuous service. In continuous service, the maximum voltage and current limitations are set with a safety factor in mind to consider average power dissipated on the tube electrodes. In pulse service, when the tube "rests" for an appreciable time, it is possible to set new guidelines on peak electrode dissipation and maximum ratings, provided the *average* electrode dissipation and maximum temperature ratings are not exceeded.

In pulse service (less than 0.1 second)

a thoriated tungsten power tube may have an anode instantaneous peak dissipation capability as high as 100 times the average power capability, and the available filament emission may be as high as 80 milliamperes per watt of filament power. In some cases, the filament voltage has been boosted above normal to obtain emission levels as high as 150 milliamperes per watt with the penalty of greatly reduced tube life.

In the case of the oxide-coated cathode, the peak pulse current is not as clearly defined or as easily generalized as in the case of the thoriated filament tube. A figure of 500 milliamperes peak plate current per watt of heater power is often used for very short pulse service (less than 3 microseconds), and other numbers are available giving pulse plate current in terms of active cathode area.

In *long* pulse service (more than 0.1 second), the rise in temperature of the electrodes rather than the average power during the pulse often becomes the basic tube limitation, and the maximum capability of the power tube is progressively derated as the pulse length increases. For a radiation cooled tube, a pulse length of 2.5 seconds is often considered equivalent to a continuous duty operation. In the case of an oxide-coated cathode, life tests indicate that a peak-to-average dc plate current ratio of 2.0 for long pulse (0.5 second) is *not unrealistic*. This corresponds to a duty factor of 0.5.

voice and cw operation

A shadow world exists between continuous duty (CCS) operation, and ICAS operation on the one hand and pulse operation. Amateur voice and cw operations seem to fall into this shadow area. Cw operation may be compared to a form of pulse operation as it defines an "on" and "off" duty cycle wherein the two times are approximately equal. This would represent a duty cycle of fifty percent (0.5) and the pulse (cw) waveform would be nearly square.*

*Note quite true; waveshaping is necessary to some extent to reduce key clicks.

Voice operation, on the other hand, is a different and more complex problem. The voice waveform is not a square pulse; it has a large peak-to-average power ratio with irregular waveform. Normal speech, unclipped, uncompressed or otherwise altered, seems to have a peak-to-average ratio of about 14 dB.³ Various compression and clipping techniques can reduce this ratio to 3 to 5 dB before severe distortion becomes apparent.⁴ Thus, heavily clipped or compressed speech waveforms tend to resemble the cw duty cycle as far as the peak-to-average power ratio is concerned.

It is prudent to expect, therefore, that the power capability of a tube can be safely increased for *Intermittent Voice and CW Service* (IVS service) over the CCS rating provided the maximum element temperature of the electrodes is not exceeded and the cathode (or filament) emission is sufficient to satisfy plate and grid current peaks. In addition, the tube in question should not have an intolerable level of intermodulation distortion when operated in linear service under these enhanced conditions.

This type of intermittent operation is done everyday with the popular sweep tubes used in ssb equipment designed for amateur service. Small soft-glass envelope tubes (i. e., the 6LQ6) are run up to 250 or 300 watts PEP input with no apparent harm *provided* the maximum level of plate dissipation is held within reason, even though the average, long-term dissipation rating in tv service is only 30 watts or so. The user is taking advantage of the intermittent nature of amateur voice operation and the high peak-to-average ratio of the human voice to get more watts per dollar of tube investment. Many amateurs have found, to their regret, an overworked sweep tube tends to overheat and shows extremely short life when a voice clipper/compressor unit is used to bring up the average power of the equipment, or if extended cw operation is used. A moment's reflection upon the heating process in the tube will show the reason for this problem. The tube is being pushed so far that any margin of safety

has vanished. Unfortunately, no one has yet been able to miniaturize the watt!

Thus, there's a limit beyond which pushing the transmitting tube becomes uneconomical. It may be well to push an inexpensive sweep tube to 300 watts PEP input, since a tuning error, or other maladjustment won't bankrupt the unlucky user. The owner of a more expensive transmitting tube, however, may well have second thoughts before he blasts his pet power tube. Obviously, some middle ground is called for where the peak-to-average power ratio of ssb and cw operation can afford new and conservative tube ratings more in line with today's usage.

intermittent voice service

In single sideband service, the two plate current values of significance are the single-tone plate current and the two-tone plate current. The ratio of single-tone to two-tone plate current may vary from 1.1/1 to 1.57/1, depending upon the class of operation. Two-tone plate current is useful as the magnitude of intermodulation distortion products may be specified as the reduction in decibels of one product from one tone of a two-equal-tone signal. Precedence exists, therefore, for providing typical operating data for linear amplifier service specifying the dc plate current under two-tone conditions of average plate current and plate current at the peak of the modulation envelope. Such data for the 8122 is shown in **table 1**.²

Based upon such data, extensive life tests have been run at the Eimac Division of Varian to determine if more meaningful operating conditions could be specified for either ssb or cw operating modes. As far as amateur operation is concerned, the limiting mode is cw, where the duty factor is about 0.5. The duty factor for single sideband transmissions with unprocessed speech runs about 0.05 for a 13-dB peak-to-average signal and could rise as high as 0.5 for high levels of speech compression or clipping. A duty factor of 0.5 (peak-to-average ratio of 2.0) for Intermittent Voice Service rating would therefore cover both

table 2. Preliminary operating data for 8873 family of ceramic/metal, zero-bias power triodes.

Cathode: Oxide coated, unipotential	
Warm-up time	60 sec
Heater voltage	6.3 V
Heater current	3.2 A
Direct interelectrode capacitances, grounded-grid connection	
Input	19.5 pF
Output	7.00 pF
Feedback	0.04 pF
Maximum frequency ratings	450 MHz
Operating temperature, maximum, ceramic seals and anode core	
	250 ° C
Base	11-pin Special (JEDEC E11-81)
Radio-frequency linear amplifier, cathode driven, class AB₂	
Absolute maximum ratings, to 450 MHz	
Plate voltage	2200 Vdc
Plate current, continuous	250 mA
Plate dissipation	see note 1
Grid dissipation	5 W
Typical operation, Intermittent Voice Service²	
frequencies to 30 MHz	
Peak envelope or modulation crest conditions	
Peak voltage	2000 Vdc
Cathode voltage ³	8.2 Vdc
Zero-signal plate current	22 mA
Single-tone IVS plate current	500 mA
Two-tone plate current (approximate)	312 mA
Average plate current	250 mA
Single-tone grid current	30 mA
Two-tone grid current	12 mA
Peak rf grid-cathode voltage	67 V
Peak driving power	26 W
Peak power input	1000 W
Single-tone IVS useful output power	587 W
Resonant load impedance	2140 ohms
Intermodulation distortion products:	
3rd Order	-35 dB
5th Order	-36 dB

notes. 1. 8873 is conduction cooled, and plate dissipation depends upon heat-sink cooling. 8874 plate dissipation is 400 watts, and tube has an axial-flow, forced-air cooled anode. 8875 plate dissipation is 300 watts, and tube has a transverse-flow, forced-air cooled anode.

2. Intermittent voice and cw ratings are based upon the maximum voltage and current ratings given for a signal having a peak-to-average power ratio of 2.0 or more. During short periods of adjustment (less than 30 seconds), the average plate current may be as high as the IVS value.

3. Cathode bias is obtained from a zener diode.

the cw and ssb speech-with-processing situations.

The derivation of a different rating from an existing rating may only take place after extensive life tests have been completed to make sure that tube life is not being shortened and that maximum temperature and dissipation limits are not

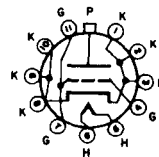


fig. 2. Tube base diagram for the 8873, 8874, 8875 family of zero-bias triodes. Multiple cathode leads keep cathode inductance to a minimum.

being exceeded. Any tube may be limited by grid or screen dissipation level and some may be limited by a plate voltage ceiling, or by available cathode emission. *Each tube type is an individual case, and to jump to conclusions or to interpret data from one type to another is risky and unfounded to say the least.* In all cases the total average current load on the oxide cathode will remain about the same for the new rating as for the average situation.

The *Intermittent Voice and CW (IVS)* rating may be defined as:

That maximum voltage and current rating given for a signal having a maximum peak to average power ratio of 2.0 or more. During short periods of adjustment (less than 30 seconds), the average plate current may be as high as the IVS value.

In all cases, the IVS rating and "short period of adjustment" are limited by the maximum allowable temperature of the tube anode and seals.

using the ivs rating

The IVS rating is especially attractive to amateur operators as it outlines typical operating parameters for cw and ssb. How are the new ratings used? The following is an example of how an amateur operator can safely and properly tune up for an IVS operating condition with the aid of an inexpensive oscilloscope.

The oscilloscope is necessary for ssb adjustment at first since meter response to a voice waveform may vary from meter to meter and is, in any case, highly irregular and difficult to interpret.

1. The first step to achieve an IVS condition for either ssb or cw is to tune and load the linear amplifier with carrier (single tone) to an IVS rated value of dc plate current (as read on the plate meter), observing maximum "on" time. The amplifier is now ready for IVS CW operation. This could be called the "long-dash" tuning method. An electronic key is handy for this operation.

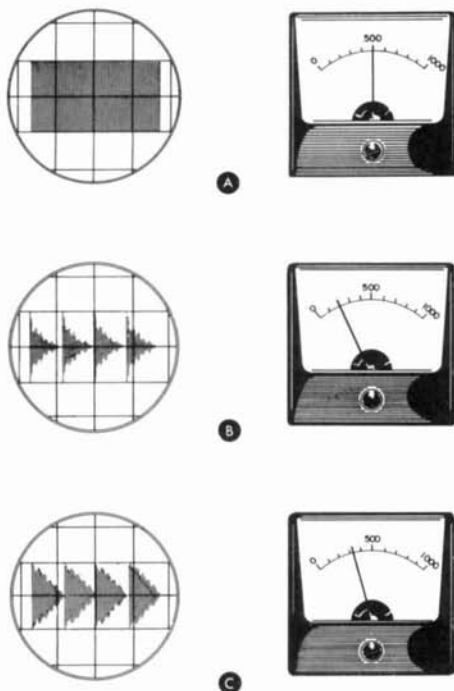


fig. 1. Typical meter readings for IVS operation.

A. With single tone (carrier), the linear amplifier is loaded to maximum IVS plate current (500 mA in this example). Oscilloscope shows carrier pattern. Pattern height is noted as 2 units. Observe short tuneup time.

B. Carrier is removed and voice modulation applied and gradually increased until voice peaks reach carrier height of 2 units as noted in pattern A. Plate meter kicks up to about 200 mA on voice peaks. No speech processing used.

C. Adding speech processing (clipping or compression). Note that plate meter now kicks up under voice peaks to about 325 mA, but that voice peaks on oscilloscope rise no higher than the single-tone limit of 2 units. However, area under the peaks is greatly enhanced, indicating greater average-to-peak ratio of voice signal. If oscilloscope peaks are greater than 2 units height, with or without voice processing, amplifier is being overdriven, with accompanying splatter and distortion.

2. For ssb observe the rf output pattern on the oscilloscope and note the amplitude for reference.
3. Remove the carrier. Insert audio and slowly increase audio gain so that the instantaneous rf peaks observed on the oscilloscope reach the same maxi-

table 1. Type 8122, linear rf power amplifier service (AB₁). Typical CCS operation at 30 MHz with two-tone modulation.

Plate voltage	2000 Vdc
Grid no. 2 voltage	400 Vdc
Grid no. 1 voltage	-35 Vdc
Zero-signal plate current	100 mA
Plate current	
Peak of envelope	335 mA
Average	250 mA
Grid no. 2 current	
Peak of envelope	10 mA
Average	7 mA
Average grid no. 1 current	0.05 mA
Effective rf load resistance	3050 ohms

mum level as obtained in *step 2* under carrier insertion. The amplifier is now working at the correct IVS level of peak input.

4. Observe the average current peaks on the plate meter for future reference.

In summary, the amplifier is tuned up to IVS condition with single-tone excitation to set the peak signal level. The single tone is removed, and audio is applied so the instantaneous signal peaks reach the same peak level as before, but the peak-to-average level of the intelligence may vary widely, depending upon voice characteristics, degree of speech processing, etc. This is summed up in **fig. 1**.

ivs ratings for the 8873 family of triodes

The new 8873 family of zero-bias triodes is the first to carry the new IVS rating. These ratings are based upon the original design concept of the tube, plus extended life tests where electrode temperatures, cathode emission and power output were carefully monitored. For example, the continuous plate current rating is 250 milliamperes. The cathode area of the 8873 is over 2 square centimeters; this corresponds quite closely to the 125 milliamperes per square centimeter rule-of-thumb stated earlier for an oxide-coated cathode. The life tests showed that a peak dc plate current rating of 500 milliamperes is reasonable at a duty cycle of 0.5 (peak-to-average

power ratio of 2.0), corresponding to the IVS philosophy (**table 2**). The various input levels at a given plate voltage may now be established. At 2000 volts, for example, the average plate input is 2000 (volts) x 250 (milliamperes) = 500 watts. This corresponds to key-down service, such as RTTY. The two-tone rating (as in a short two-tone test) is 2000 (volts) x 312 (milliamperes) = 624 watts, average power. The IVS rating for ssb voice or cw is 2000 (volts) x 500 (milliamperes) = 1000 watts peak envelope power. In the case of voice and cw, the average current "load" on the cathode is the same.

Thus, today's power tube may be rated in two different and useful ways. Commonly, it bears the continuous duty (CCS) rating, and occasionally it bears the semi-obsolete ICAS rating. It is hoped that the new IVS rating will find favor in the future as it permits greater operating economy to be achieved in the use of all power-grid tubes.

what about . . .

The immediate question arises, "If this is so, what about the IVS ratings for the 3-500Z or the 8122 or the 4X150A, or whatever?" The present answer to this query is that *each tube type must be examined on its merits* and the outer limits established for any new rating, whether it be pulse, ICAS, or IVS. This is a continual process with most tube manufacturers, and more relevant data of this type will probably be forthcoming over the months.

Thanks to William McAulay, W6KM; Jack Quinn, W6MJG; and Robert Sutherland, W6UOV, for their help in the preparation of this article.

references

1. Perrine, "Thirty-Three Watts per Dollar from a type '52," *QST*, September, 1932.
2. RCA Electron Tube Handbook, HB-3, Volume 1, "Tube Ratings," RCA, Harrison, New Jersey 07029.
3. Magnuski and Firestone, "Comparison of SSB and FM for VHF Mobile Service," *Proceedings of the IRE*, December, 1956.
4. Collins, "Ordinary and Processed Speech in SSB Application," *QST*, January, 1969.

ham radio



**MXX-1 Transistor
RF Mixer \$3.50**

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range.

Lo Kit 3 to 20 MHz
Hi Kit 20 to 170 MHz
(Specify when ordering)



**SAX-1 Transistor
RF Amplifier \$3.50**

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output.

Lo Kit 3 to 20 MHz
Hi Kit 20 to 170 MHz
(Specify when ordering)



**PAX-1 Transistor RF
Power Amplifier \$3.75**

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.



**BAX-1 Broadband
Amplifier \$3.75**

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur.

For The Experimenter!

International EX Crystal & EX Kits

OSCILLATOR / RF MIXER / RF AMPLIFIER / POWER AMPLIFIER



Type EX Crystal

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency)

\$395



OX Oscillator

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz
Hi Kit 20,000 to 60,000 KHz
(Specify when ordering)

\$295

Write for complete catalog



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

modifying the
Heath SB-200
amplifier
for the new
8873 zero-bias triode


Simple modification
of the SB-200 linear
to provide increased
power dissipation,
better frequency stability,
and lower drive.

Two designs are featured —
air cooled and
conduction cooled

Robert I. Sutherland, W6UOV, EIMAC Division of Varian, San Carlos, California 94070

The high power capability, moderate cost and compact size of the new 8873 family of zero-bias, ceramic/metal power triodes make them well suited for new design, as well as for retrofit into popular amateur equipment that uses older tubes having restricted power capability and limited frequency range. The well-known Heath SB-200, a one-kilowatt PEP linear amplifier, is a likely candidate. This article covers the modification of this unit to use the new power tubes. The modification provides increased power dissipation,

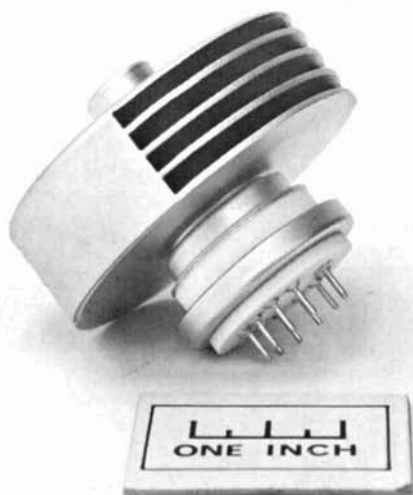The Eimac 8875 is a ceramic/metal zero-bias triode with a transverse cooler that provides 300 watts anode dissipation.



better high-frequency stability and lower drive requirements, and (in the case of the 8875) at a lower overall tube replacement cost than the original pair of tubes.

Based upon a study of the SB-200 circuit design, it was decided to try different modifications on two separate amplifiers. The first version uses the 8875, a high- μ power triode having 300 watts anode dissipation and capable of about 1200 watts peak input in Intermittent Voice Service (IVS).¹ The 8875 has five large, round, horizontal anode fins that may be adequately cooled with a small phono-motor fan, the type already in the Heath amplifier. This modification requires a minimum amount of disruption of the existing Heath circuitry.

The second amplifier has a more sophisticated and interesting modification: a conduction-cooled 8873 power triode (electrically equivalent to the 8875) is used with a finned heat sink for proper anode dissipation. The heat sink forms the vertical back wall of the rf enclosure.

This section discusses the first conversion, which provides full input level for the amplifier, with low intermodulation distortion and good tube life. The conduction-cooled version is described in the last part of the article.

the 8875 modification

The 8875 zero-bias power tube is shown in the photo and is capable of 1200 watts PEP input for ssb and 1000 watts when run in IVS service. The tube is about the size of a 4CX250B, has an 11-pin base and uses an inexpensive socket. Cathode and grid connections are brought out to multiple base pins, and, in addition, the grid is terminated in a low-inductance contact ring at the base of the tube which may be used for vhf operation. The anode is intended to be cooled by a horizontal air blast from a small fan. Dissipation is a function of cooling air, and a small phono-motor fan provides about 300 watts dissipation. For RTTY service, the power input level of the amplifier is dropped to about 600

watts. These levels are entirely compatible with the rating of the intermittent-duty power supply of the SB-200 amplifier.

The 8875 is mounted in a horizontal position in the approximate space previously occupied by the two glass tubes as shown in the chassis photo. The 11-pin tube socket is near the center of a small aluminum sub-chassis mounted to the rear wall of the amplifier enclosure. The existing cooling fan, mounted at the

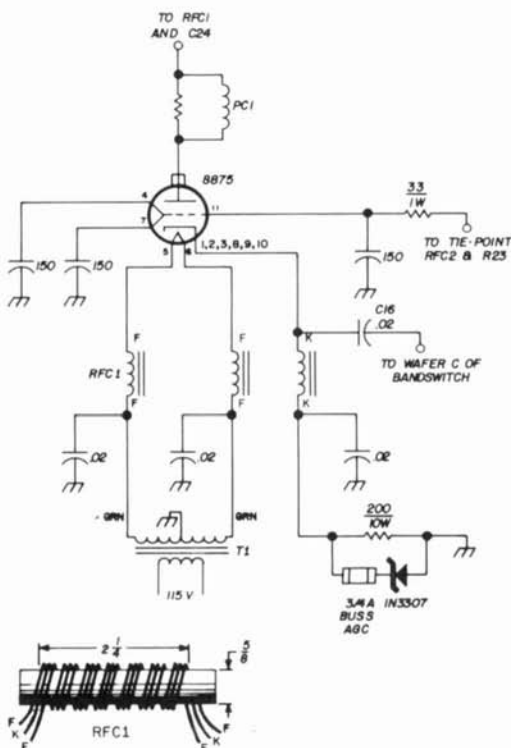


fig. 1. Revised schematic for the SB-200 shows the 8875 zero-bias triode. The 8875 requires 6.3 volts and the filament voltage in the SB-200 is on the high side because of reduced current drain. The original filament-choke windings are removed and three new windings put in their place. The filament windings are two 44" lengths of no. 20 enameled wire; the cathode winding is a 44" length of no. 26 insulated wire. Each winding has a 3" pigtail. Twenty trifilar turns are wound on the ferrite form. The ends are tied with twine and given a drop of epoxy to hold the windings in place. The socket for the 8875 is an E. F. Johnson 124-311-100. The 150-pF grid bypass capacitors are dipped mica units.

bottom of the enclosure, is moved to a new position in respect to the anode of the 8875.


The revised circuit is shown in **fig. 1**. It uses most of the original components. A new filament choke or dropping resistor is required, as well as zener-diode bias for the 8875. All new components, with the exception of the zener fuse, are mounted within the sub-chassis, as shown in the rear-view photograph.

mechanical modifications


The first step is to remove the components around the existing 4-prong sockets, and then remove the sockets themselves.

Remove the filament choke from tie-point M. Unbolt tie-point AB, leaving the wiring connected. (See pictorial 11, page 39 of the Heath Instruction Manual. Original components are identified by

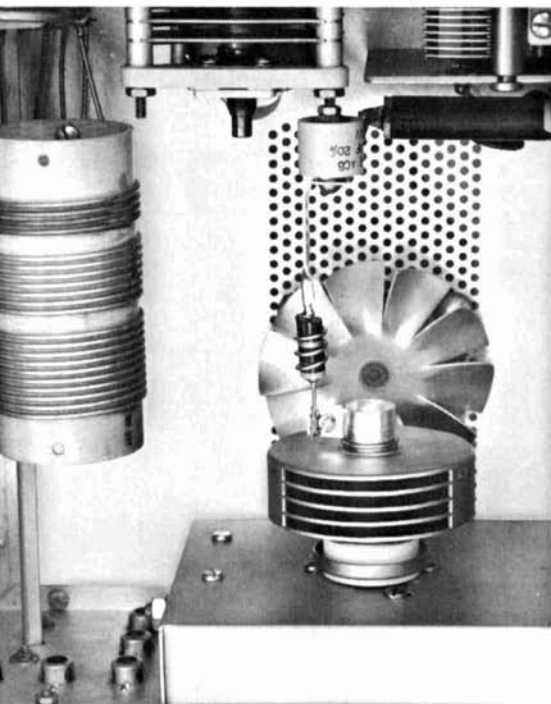In the modified Heath SB-200 the 8875 is mounted horizontally in the space formerly occupied by the two glass tubes. Major plate circuit components remain unchanged.



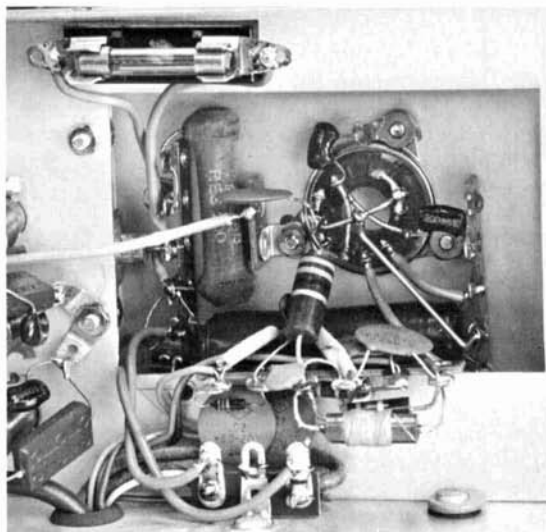their Heath nomenclature.) The next step is to cut out a rectangular hole on the rear wall of the enclosure as shown in the rear-view photo, with the dimensions



The rear panel of the SB-200 is cut out to allow access to the underside of the new sub-chassis. Untouched cathode coils are to left of the cutout. The zener fuse is at top of cutout with 200-ohm cathode resistor and zener diode mounted in sub-chassis. In this installation an extra cathode choke was used with the original SB-200 filament choke. The cathode choke has 15 μ H inductance and 1000 mA current rating (J. W. Miller 4624).

shown in **fig. 2**. The new sub-chassis for the 8875 is placed over this hole. The sub-chassis is a 4 x 5 x 2-inch Bud AC-1404 chassis cut down to 1- $\frac{1}{4}$ " height and held in place with spade lugs and bolts. The tube socket is placed on the sub-chassis as shown in **fig. 2**.

The new sub-chassis interferes with various bolts holding the rf enclosure to the main chassis deck along the bottom rear edge, and it is necessary to provide clearance for these bolts. Proper clearance is provided by noting position of the bolts and drilling $\frac{1}{4}$ -inch clearance holes in the sub-chassis at the points of interference.

Once the sub-chassis is in position, the

tube is placed in the socket and the phono fan moved until the blades are positioned beneath the anode of the tube as shown in fig. 3.

and it is necessary to drop it slightly to avoid over-volting the tube filament; a 0.3-volt drop is necessary. This may be readily achieved by placing a 0.1-ohm wirewound resistor in series with one filament lead, or the filament choke may be rewound with the proper wire length and size to develop the required voltage drop. Since a cathode rf choke is required, the builder has the option of rewinding the present filament choke and adding a cathode winding as shown in fig. 1 or using the existing choke and adding a cathode rf choke and filament dropping resistor. The latter was done for the first tests, and a new trifilar rf choke was substituted at a later date.

amplifier testing

When the modification is complete, all wiring should be checked and the resistance to ground from the anode clip should be checked. As in the original amplifier, before modification, the resistance should be about 180,000 ohms (the resistance of the filter bleeder resistor, R₅ - R₁₁). The amplifier should be connected to the exciter and to a dummy load. Before the amplifier is turned on, the exciter is tuned up, feeding through the unenergized antenna relay of the amplifier. The amplifier is now turned on, and the panel meter should read about +2400 volts in the HV position. Amplifier plate current is zero because of the cut-off bias voltage.

The amplifier controls are set as des-

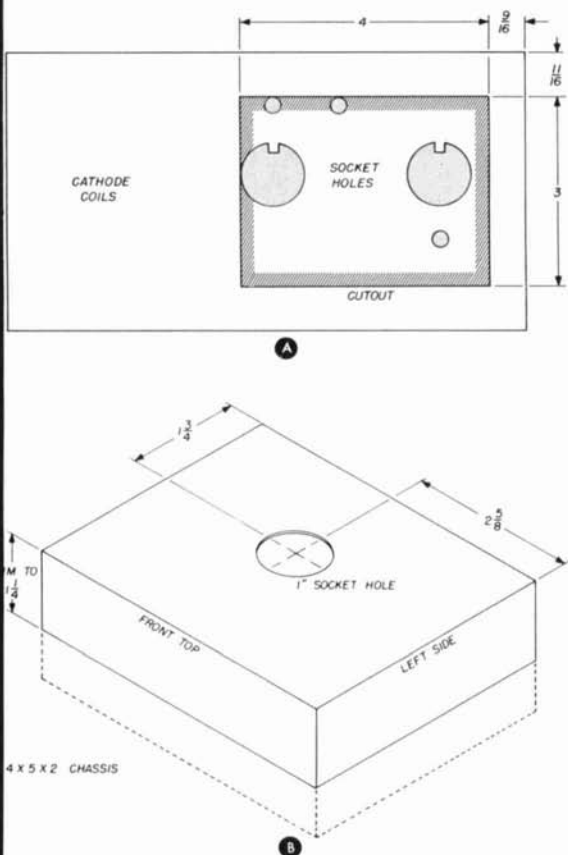


fig. 2. SB-200 chassis modifications to accommodate the 8875. The enclosure cutout for the sub-chassis is shown in A. The modified sub-chassis for the 8875 socket is shown in B.

electrical modifications

The portion of the original schematic of the SB-200 that is revised is shown in fig. 1. The 1N3307 8.2-volt zener diode is bolted firmly to the wall of the sub-chassis, using a thin coating of *Wakefield Thermal Compound* smeared on the zener stud to allow a good thermal bond. The new component layout in the sub-chassis is shown in the rear-view photograph.

Using the new tube, the existing filament voltage of the SB-200 is too high,

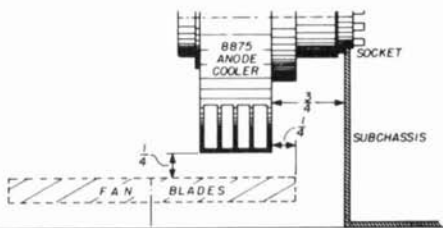


fig. 3. Phono-motor fan installation for the 8875. The motor must be moved so the shaft is in line with the center of the anode, and the tip of the fan blade clears the bottom of the tube by $\frac{1}{4}$ inch. The blade should also clear the edge of the anode by $\frac{1}{4}$ inch.

cribed in the *Operating Procedure* section of the Heath Manual (page 47), and the amplifier is again turned on. With no driver output, the meter of the amplifier should indicate an idling plate current of about 20 milliamperes. A ninety-second cathode warm up time should be observed before excitation is applied to the

plate and grid current. At maximum input the power output (measured with an accurate wattmeter) is between 520 watts (10 meters) and 630 watts (at the lower frequencies). Power gain is about 10 decibels. Under voice conditions, with no speech processing, voice peaks will run about 200 milliamperes on the meter.

Thanks to Merle Parten, K6DC, and Dick Rasor, WA6NXB, for their help and assistance in modifying the amplifier and making measurements on the completed version.


conduction-cooled linear

Modern power tubes such as the 8873-family have the capability of developing anode power dissipation densities (watts per square centimeter) comparable to the power densities in many jet and rocket engines. For this reason, effective cooling techniques are essential for long life and high tube reliability.

Conduction cooling is an efficient system of heat elimination, making use of the *heat source* (power tube or transistor), a heat transmission path (*thermal link*) and a *heat sink*, wherein the heat is removed. Many amateurs have seen transistors with tiny heat sinks on them; far fewer amateurs have observed heat-sink systems capable of dissipating several kilowatts of power. Such large systems exist, and the general design (suitably scaled down) may be adapted for use at amateur power levels. Although common in commercial and military gear, the heat-sink conduction-cooled system is just beginning to appear in amateur equipment (i. e., the Signal-One transceiver).

In the case of a power tube whose anode operates at a high voltage potential, the thermal link must have the dual properties of a thermal conductor and an electric insulator. One of the most practical materials for this task is *Beryllium Oxide* (BeO), an insulative ceramic (refractory) material which has the thermal conductive properties of aluminum.

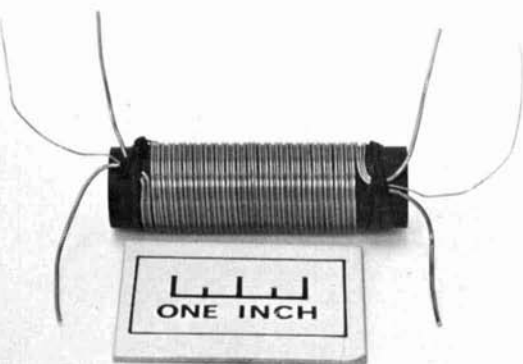The 8873 zero-bias power triode makes use of a BeO thermal link and external heat sink. The link is detachable,



New trifilar filament and cathode choke for the modified SB-200 uses ferrite rod from original unit. Winding details are shown in fig. 1.

8875. The drive level of the exciter is advanced until the plate current rises to about 200 milliamperes. Tuning and load controls are adjusted for maximum power output (minimum plate current) on the amplifier meter. Grid current should be about one division on the meter (25 milliamperes, or less). **Caution:** *The 8875 is easy to drive; watch out for excessive grid current.*

The amplifier may now be loaded for a maximum plate current of 500 milliamperes, using carrier injection from the exciter. Maximum grid current is 45 milliamperes. This corresponds to a drive level of 55 watts or less. Loading should be done quickly so as to not run excessive IVS plate current for more than 30 seconds or so.

When proper loading with carrier injection is achieved you will find that maximum power output occurs at this point along with the recommended values of


providing mounting flexibility and reduced tube replacement cost. However, since two thermal interfaces occur with the detachable link (tube anode to link and link to heat sink), attention must be paid to ensure low thermal resistance at these two interfaces if optimum cooling performance is to be achieved.

The heat sink, receiving heat through the thermal link from the tube anode, emits energy in the form of radiant heat. The quantity of heat radiated depends upon the absolute temperature of the sink relative to the surrounding environment and the nature of its surface. A heat sink operating at an elevated temperature compared to its environment will transfer heat to the environment by radiation, convection and conduction, as is done in this case.

The added output capacitance of the tube supplied by the thermal link and heat sink is typically 6 to 10 pF, and this

must be taken into account when vhf tank circuits are concerned.

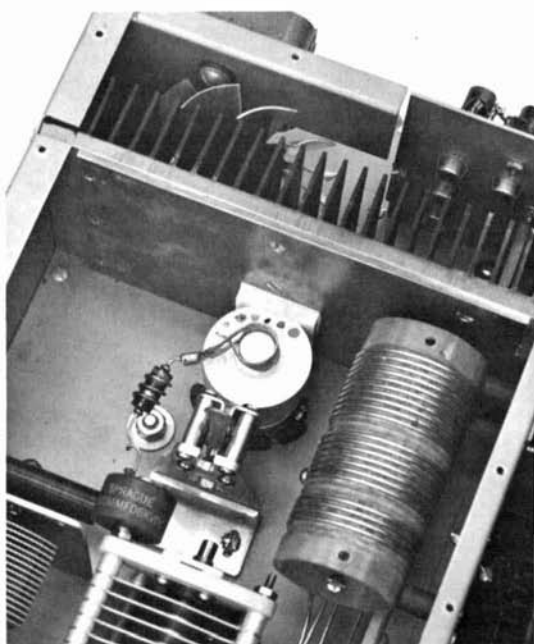The heat sink used with power tubes may be liquid or air cooled. In this case



The 8873 conduction-cooled zero-bias triode.



Conduction-cooled 8873 zero-bias triode mounted in the Heath SB-200 linear. The 8873 is held in place with a toggle clamp that presses the anode of the tube against a beryllium-oxide thermal link and finned heat sink. The flat surface of the heat sink is covered with 1/8-inch copper sheet to distribute anode heat evenly. Under normal voice operation heat-sink dissipation provides sufficient cooling. For cw or long-winded voice operation a thermal switch turns on a small phono-motor fan to hold the temperature of the heat sink at a conservative level. When heat-sink temperature drops to normal value, the fan is automatically switched off.

two or three hundred watts of anode dissipation are required so air cooling is feasible.

the 8873

The 8873, like the 8875, is a ceramic/metal, zero-bias triode intended for hf and vhf service up to 450 MHz or so. No air cooling of the base is required if the socket is mounted on a chassis which has

sufficiently low thermal resistance to drain the filament heat away from the stem of the tube.


The 8873 seemed a natural for retrofit in an existing Heath SB-200 amplifier. It was planned that the cabinet and power supply of the SB-200 could be used as a test bed for future experiments (such as a 50 MHz or 144 MHz amplifier) so a new, two-piece aluminum chassis was made. The power supply was rebuilt on one chassis and the amplifier section on another. Both units were then bolted together to resemble the original Heath chassis and shields. An amateur intending to modify his own SB-200 to this design probably would use the Heath metal work as-is.

heatsinking the SB-200 chassis

The 8873 anode is heat sunk to a finned radiator mounted at the rear of the amplifier enclosure. Generally speaking, the modification consists of removing the present tubes, sockets and auxiliary components and reworking the circuit electrically as described in the 8875 modification. Views of the heat sink installation are shown in the photographs. The heat sink measures 7-3/4 x 4-1/4 inches and is mounted to the chassis and side walls about 8-3/4 inches behind the front wall of the enclosure. The 8873 socket mounts in the center of the enclosure, with the center of the socket about 15/16-inch from the smooth surface of the heat sink.

Anode heat flows from the 8873, through a BeO insulating block into the heat sink. Good bonding is essential between these three components in order to hold anode core and seal temperatures below the maximum permitted rating of 250°C. To hold the components firmly together, a DE-STA-CO toggle clamp is mounted in front of the tube. A small 1/2-inch ceramic insulator is substituted for the rubber nose of the clamp, which presses against the tube and heat sink. While the clamping action takes place, the tube and socket should be free to move. Accordingly, the socket is mounted in a clamp ring so that a slight amount of

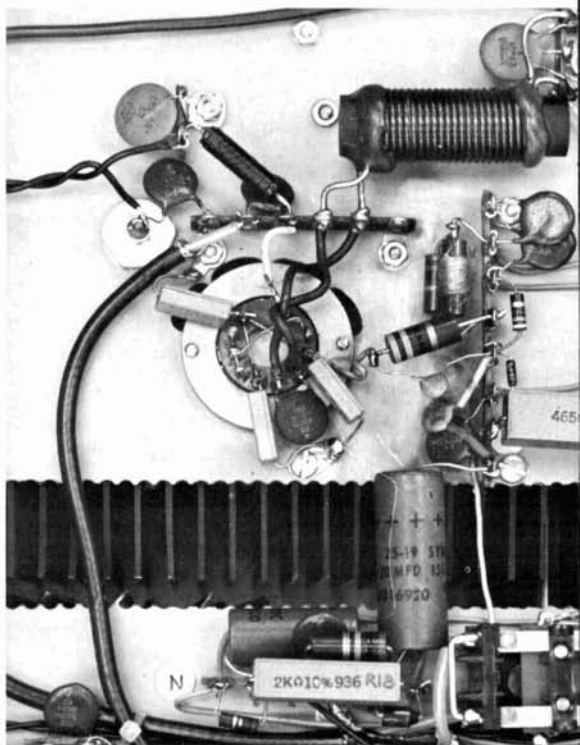rotational and lateral movement can be accomplished. The rotational movement is required in order to align the flat surfaces of the tube, thermal link and




Bottom view of amplifier chassis shows sub-mounted tube socket. Chassis bolt holes are slotted so tube and socket may be moved slightly so the anode is properly seated against the heat sink. The rear of the amplifier chassis has been cut away below the heat sink so cooling air may pass through the fins. Filament choke is at upper right with zener diode mounted on chassis at upper left.

heat sink. The socket is then tightened in position after alignment and clamping takes place.

The heat sink provides about 160 watts of continuous anode dissipation when cooled by normal currents of 20°C air (room temperature). It is possible to raise the dissipation of the sink to about 200 continuous watts by passing cooling

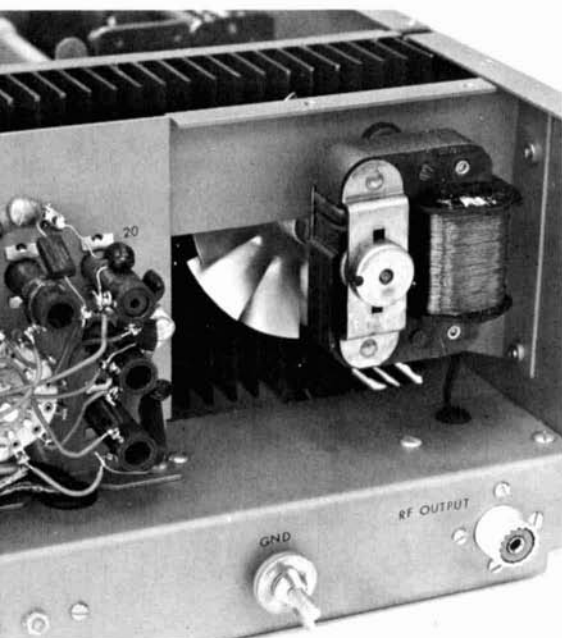air across it from the small phono-motor fan which was a part of the original SB-200 assembly. The fan was included in this design, along with a thermal switch.



Rear view of conduction-cooled amplifier shows cooling fan and cathode tuned circuits. Chassis beneath the heat sink has been cut away for proper flow of cooling air.

When the temperature of the heat sink approaches a value that indicates high anode temperature, the fan is automatically switched on, increasing the capacity of the sink and protecting it from long-winded rag chewers and marathon talkers.

To determine the capacity of the heat sink system, temperature runs were made on the sink and tube anode, with various values of anode dissipation. Heat-sink and anode temperature were measured with temperature sensitive paint, and the thermal switch was moved about on the sink until it switched on when anode temperature reached about 180° C, well


below the upper design limit of the tube.

To hold tube base temperature to a safe level, slots were cut in the chassis around the tube socket to allow cooling air from beneath the chassis to flow up and around the tube base (see under-chassis photo).

amplifier operation

Tuning and loading of the amplifier is normal, and follows the procedure outlined in the 8875 description. Under most operating conditions, the heat-sink temperature does not rise to the point at which the cooling fan is actuated, and amplifier operation is completely noiseless, a welcome "sound" these days!

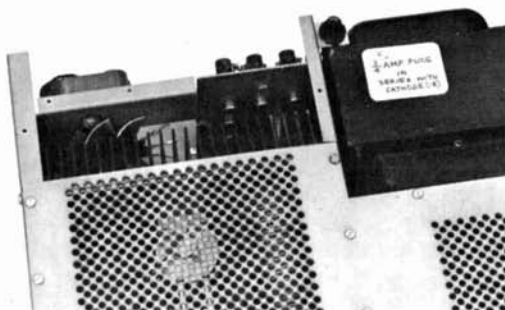While this unit is considered to be experimental, it points the way to the amplifier design of tomorrow: heat-sunk, noiseless, compact and highly efficient — quite a far cry from the old days of rack mounted gear, heavy, buzzing power supplies and black-crackle panels. How time flies!




Conduction-cooled amplifier with top shield in place. Shield has been trimmed at rear to allow air to flow over heat sink.

Again, thanks to K6DC and WA6NXXB for their assistance in this experimental project.

reference

1. William I. Orr, W6SA1, "Intermittent Voice Operation of Power Tubes," *ham radio*, this issue.

ham radio

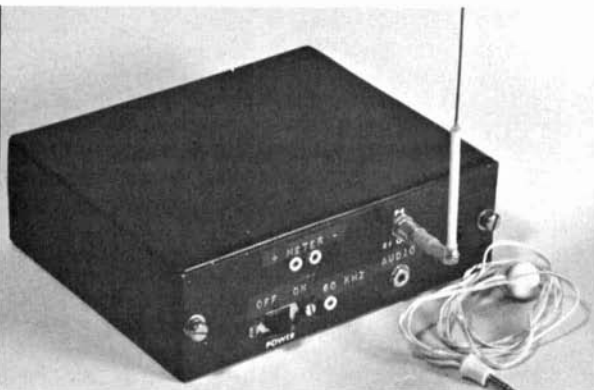

photographs by F. C. Lamm, WB4FUJ

two-meter fm frequency meter

A highly accurate
heterodyne-type
frequency meter
that provides
crystal-controlled
frequency markers
on two meters

C. A. Baldwin, W4JAZ 3406 Old Dominion Boulevard, Alexandria, Virginia 22305

On two-meter fm a .005% tolerance crystal can put your transmitter outside the passband of a narrow-band receiver, even if it is working into the same capacitance at which it was calibrated. If the capacitive load is very much different it can even put you closer to the next channel. This is why frequency-shifting capacitors must be adjusted to the crystal in use.

In the local area there are half a dozen hams who have access to laboratory standards and measurement equipment who will help you get your gear on *the* frequency — six *different* ones. These amateurs are performing a very useful service but one wonders where *the* frequency actually is. A fairly accurate answer can be provided by a relatively simple and inexpensive piece of gear.

The unit shown in the photographs measures 2x5x6 inches and weighs 26 ounces complete with batteries. It can be used to adjust a transmitter or receiver to any channel at 60-kHz intervals from 146.94 MHz to below 145 MHz. *Immediately* after calibration it will be within 15 Hz, which is roughly 1/100,000% or one part in 10^7 . From day to day, at comfortable shirtsleeve temperatures, the instrument stays within 100 Hz.

how it works

A crystal-controlled oscillator at 49 MHz feeds a buffer-tripler with an output at 147 MHz. This stage is coupled to the emitter of a mixer or modulated amplifier stage. Another crystal-controlled oscillator at 60 kHz with high harmonic output feeds an emitter-follower buffer which drives the base of the mixer, modulating the vhf signal at 60 kHz and its harmonics. The first lower sideband is on 146.94 MHz, and strong signals are available at 60-kHz intervals to below 144 MHz. The output of the mixer feeds a 19-inch whip antenna to radiate signals for receiver calibration.

The antenna and mixer also feed a full-wave diode detector to obtain a beat

the original circuits were used without any attempt to optimize the component values. In the 60 kHz oscillator, it was found necessary to provide a tip jack to read this frequency for calibration checks after the unit was in its case. Since the crystal in this circuit was within 0.1 Hz of the intended frequency, a variable capacitor in series or parallel with the crystal seemed unnecessary. The frequency of the 49 MHz oscillator is adjusted at L1. Substitution of parts or complete circuits of sections of the unit should work equally well.

The circuit is shown in block form in fig. 1; a schematic is shown in fig. 2. Parts layout is not critical and can follow the dictates of the available housing and the

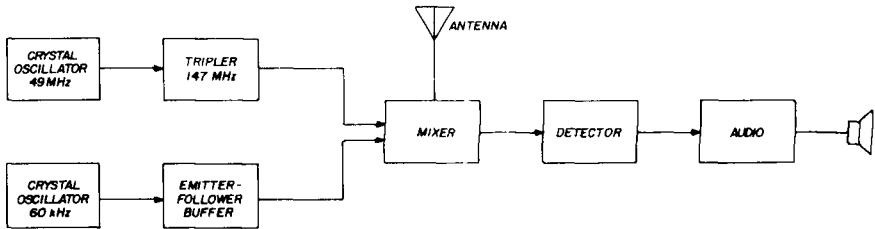


fig. 1. Block diagram of the two-meter fm frequency meter.

note between the internally generated signal and a signal at the antenna. A capacitively coupled transistor audio stage provides enough output to a broadcast receiver earpiece to permit adjustment of a transmitter to within about 30 Hz of the internal frequency. Tip jacks on the front of the unit allow connection of a low-range (5-volt) dc voltmeter across the dc detector output. Unless the meter is highly damped, the needle will quiver before the beat note becomes inaudible, and when the meter swings from minimum to maximum and back less than once a second, you have matched the frequencies within 1 Hz.

construction


The frequency meter shown in the photographs was built in a surplus module of uncertain source and purpose which contained most of the parts and circuitry of the calibrator. Where possible

preference of the builder. Some of the features of this unit, however, might deserve consideration.

First, a sturdy chassis is required for high-stability portable gear. All parts must be securely mounted; in this unit the crystals and their sockets are attached to the chassis with epoxy cement. Power to each oscillator is supplied through a dropping resistor with a 6.3-volt zener to ground; a 20% drop in battery voltage can be tolerated without affecting the frequencies. The enclosure was made from flashing copper sheet and permits rf coupling into and out of the unit only at the antenna jack. Audio and meter connections are bypassed at the jacks. Two paralleled 9-volt batteries provide long life at the 33 mA load.

calibration

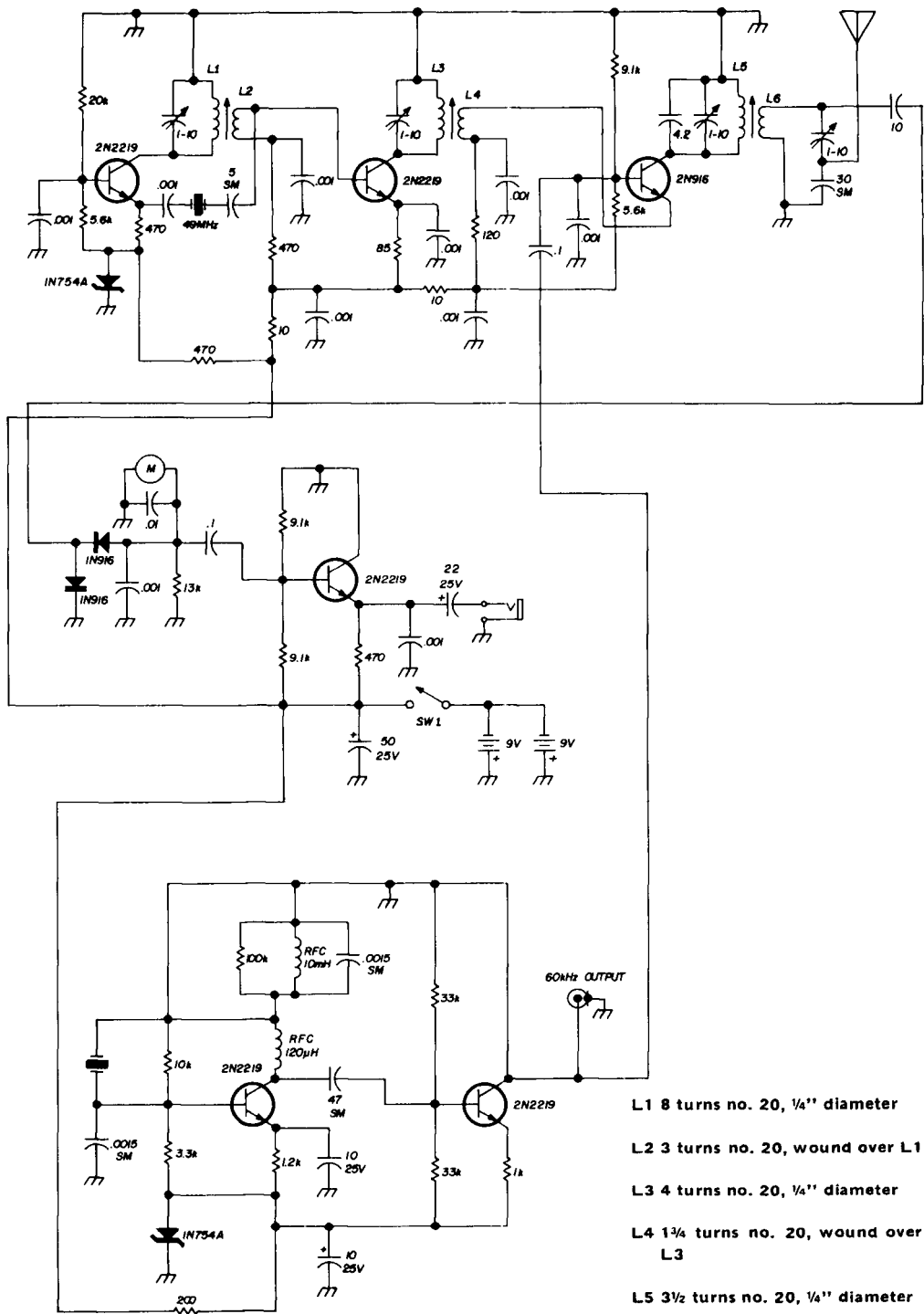This instrument was calibrated by using an available crystal standard con-



- L1 8 turns no. 20, 1/4" diameter
 - L2 3 turns no. 20, wound over L1
 - L3 4 turns no. 20, 1/4" diameter
 - L4 1 1/4 turns no. 20, wound over L3
 - L5 3 1/2 turns no. 20, 1/4" diameter
 - L6 2 1/2 turns no. 20, wound over L5
- 3 turns no. 20, wound over L1


fig. 2. Schematic diagram of the two-meter fm frequency meter. The extensive decoupling circuits and most of the component values were part of the original equipment.

stantly monitored against a WWV broadcast. 10 MHz was used, but where other frequencies are more reliable, the same principles can be applied. This 10 MHz oscillator will hold within 0.5 Hz for the duration of the calibration process. It is followed by a divider to 1 MHz and a multiplier to 50 MHz, both of which feed a mixer. This results in a signal at 49 MHz plus or minus 2.5 Hz. The unit can be adjusted so that its signal, when fed to a receiver along with the 49 MHz standard frequency, will swing the S-meter less than once per second. The cumulative errors at 49 MHz, when tripled, net a maximum error of 10.5 Hz at 147 MHz.

By a similar process, the 60-kHz oscillator can be compared with the WWV signal and adjusted easily to within 0.1 Hz. Since this frequency is multiplied by 1 at 146.94 MHz and by only 20 down to 145.80 MHz, this error does not exceed 2 Hz. It was found necessary to bring this frequency out to a tip jack on the panel for calibration purposes.

This system results in an error of less than 15 Hz within the intended range of the device. This is not as good as the best laboratory counters, but is cheaper, more rugged, portable, battery powered, and always available.

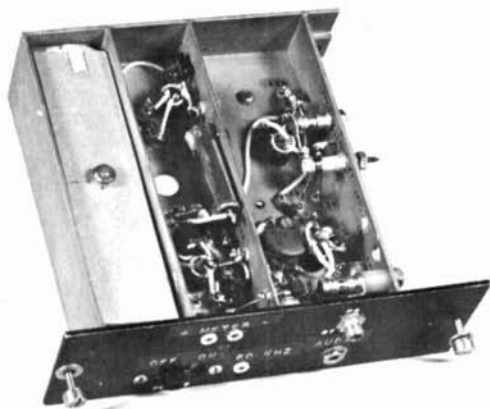Top view of chassis. The 60-kHz oscillator is located next to the batteries; buffer is at rear. On the right, front to back, are the antenna coupling capacitor, detector and audio stages, and tripler.



USE

The simple frequency meter is used just like the LM, BC 221, or other heterodyne frequency meters with an audio detector, except that a low-range, high-resistance dc voltmeter can be used to monitor the beat note at less than audio frequency. The signal from the unit can be picked up on the receiver under




Bottom view. The 49-MHz oscillator is at rear, mixer in front.

test, and the receiver's oscillator adjusted until its discriminator voltage is zero, or as otherwise directed for that receiver.

To adjust a transmitter frequency, the unit must be within about 20 feet of the transmitting antenna for powers of ten watts or above. The transmitter frequency is adjusted for zero beat as heard in the earpiece or shown on the meter. In practice, little equipment has been encountered which can be adjusted below the beat note range without meticulous care. But this is much better than most of the ham transmitters you are likely to hear. Also, it is comforting to know that the error is mostly in the transmitter or receiver adjustment, and not in the test equipment.

ham radio

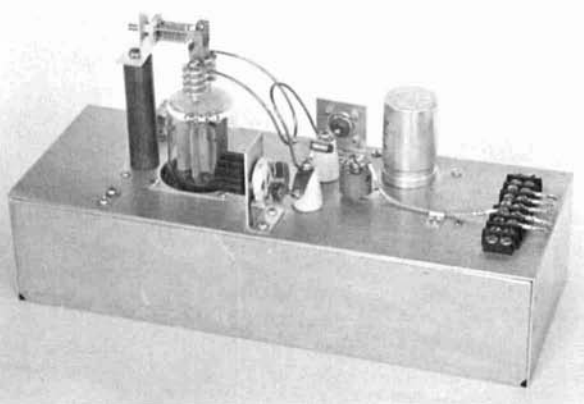

an rf power amplifier for 220 MHz

Have you been
avoiding vhf operation
because of
construction difficulties?
Then meet the
"220 Lady"

M. O. Beck, WB6DJV, 1637 Hood, Wichita, Kansas 67203

The apparatus shown in the photographs accompanying this article is a class-C rf power amplifier for the 220-MHz amateur band. It was designed and built to disprove the remarks made by hams who claim that operation on 220 MHz presents too many technical difficulties. The classic remark is, "220 MHz is just too hard to get on." Well, all that is changed now.

The amplifier described here has features that should appeal even to the most skeptical vhf critic. Standard parts are used, and if my layout and construction suggestions are followed, the amplifier will give a good account of itself with a minimum of debugging.

After a considerable amount of thought on the subject of why many hams shy away from building vhf amplifiers, I arrived at the real reason: neutralization. Since this is the main objection, I decided to put it out of the picture once

and for all by designing an amplifier that requires absolutely no neutralization whatsoever. I further decided that the amplifier should require such minimal drive that the driver could be a multiplier (again, no neutralization).

I dubbed this amplifier the "220 Lady," simply because it behaves like a lady — in the classic sense, that is! From the moment it was first fired up, it was a perfect example of what a good amplifier should be: tame, cool running, and efficient. In fact, the night it was completed this amplifier was the subject of a lecture given at the Wichita Amateur Radio Club.


Other than praise, there's little else to be said about the amplifier, as the schematic (fig. 1) and the excellent photographs (taken by a friend, Mike McConnell) just about tell the whole story.

publication for beginner and experienced vhf'er alike.¹

I'd like to emphasize one important point. It's strongly recommended that my design and layout be followed exactly. Parts layout, lead dress, and mechanical details have been very carefully worked out. The shielded wire (see photos) is an absolute necessity. Although some variation could be made in parts layout, I don't recommend it. The grid and plate tank circuits are rather old fashioned, but that's probably why the amplifier works so well. This construction method (fig. 2) is tried and true. If the amplifier "takes off" then you have made some mistake in wiring or have side-stepped my layout.

bias requirements

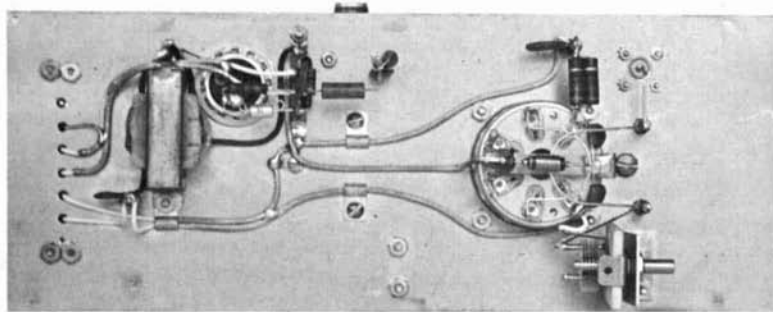I hope you'll put the little bias supply where I did — under the chassis where it belongs! As to setting the bias voltage,




Under-chassis view. Shielded wiring is necessary for circuit isolation at this frequency. Note simple bias supply, which doubles as tube-heater source.

construction

The fact that you've read this far indicates you're interested in getting on 220 MHz. I'll assume you've had some experience in construction and wiring techniques at the vhf-uhf level. If not, all you have to do is read one of the many articles published on the subject. The vhf-uhf manual by G6JP is an excellent

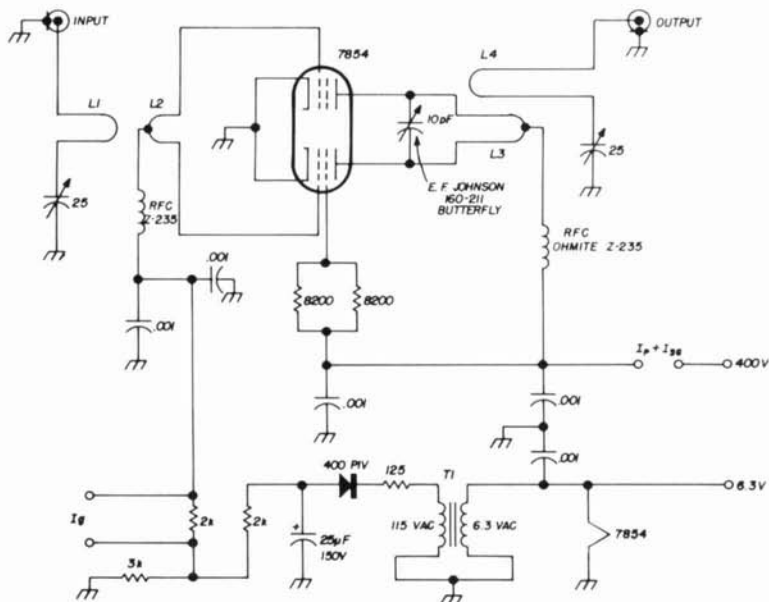I've included photos and the schematic of the supply I use. It may differ a bit from your idea of what class C should be, but before you knock it — try it. I strongly advise against keying the amplifier in the cathode, as instability could result. We're talking about class-C operation, so key the transmitter where it should be keyed — in the exciter.



Top-chassis view of the amplifier. Parts layout should be close to that shown for trouble-free results.

phone operation


You want to modulate the rig? By all means, go ahead and plate modulate; remember, the amplifier is operating at class C. Interested in ssb? Just decrease the bias and increase the screen voltage, which should be obtained from a separate source, of course. Your scope will tell you when you have the correct bias adjustments.

tube considerations

If you have a 5894 it may be substituted for the 7854 but this may present neutralization problems which we're trying to avoid. Using the 7854, I obtained rated output with a type 6360 tube as a driver-tripler. Drive power is no problem; only a watt or two is required.

The amplifier should not be operated at dc inputs exceeding 50-60 watts. Initial

fig. 1. Schematic of the "220 Lady." Neutralization has been eliminated in this amplifier. Full dc input of 50 watts requires only one or two watts of drive.

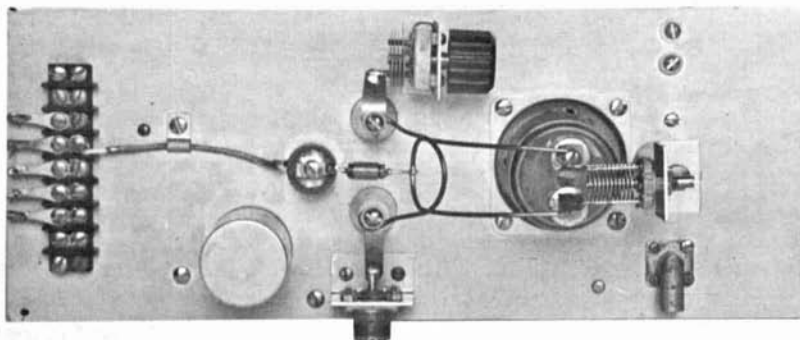

circuit adjustments should be made with the aid of a grid-dip oscillator. These dual tetrodes (7854, etc.) don't take kindly to excessive out-of-resonance maltreatment.*

conclusions

This amplifier is just about the ultimate from the standpoint of cost and construction simplicity, but don't be deceived — it's a real performer. The amplifier is designed for cw and really does a good job in this mode.

This article is a cart-before-the-horse thing. I told Jim Fisk I had an article on the exciter for this amplifier, but second thoughts led me to rebuild it for appear-

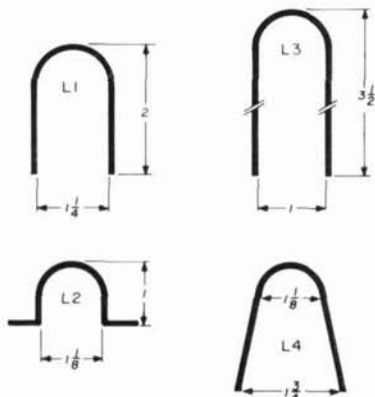


fig. 2. Dimensions for plate and grid inductances. Material can be small-diameter copper tubing or large-diameter copper wire.

ance as well as efficiency. So maybe this amplifier will at least sooth the editor as well as convince a few more fellows that it really isn't "hard to get on 220 MHz."

reference

1. G. R. Jessop, C. Eng., MIERE, G6JP, "Vhf-uhf Manual," Comtec Book Division, Box 592, Amherst, New Hampshire 03031 (\$3.75 ppd).

ham radio

*Although not shown in the schematic, good insurance against tube failure is a screen-grid protective circuit. Several schemes are shown in the ARRL handbook. editor.

NEW

TRI-EX'S

MW

SERIES

Pound for pound the strongest self-supporting steel towers available.

The new economy MW Series towers are designed to support up to 9½ sq. ft. of antenna area. Featuring Tri-Ex's extra strong torsional twist resistant "W" bracing, the all steel MW crank-up towers come in three sizes, each fully galvanized for carefree maintenance. Models available, by height, are: MW-35', MW-50', and MW-65'. Nested height is between 21' and 22'. Hinged base and wall bracket included with MW tower order! See your local dealer or write for free catalog today. Prices start as low as:

\$157.35

Tri-Ex TOWER CORPORATION
7182 RASMUSSEN AVE., VISALIA, CALIF. 93277

EIMAC's new 8873 family of grounded grid, zero bias triodes offers you top-man-on-the-frequency performance to 432 MHz.

(Imagine how these tubes will work at 14 MHz).

EIMAC's many contributions to grounded grid triode design and production have now been combined with the advantage of rugged, low-profile ceramic/metal assembly to bring you this new family of impressive high- μ triodes. They're inexpensive, and work up to 1000 watts PEP input at frequencies up through 432 MHz. Quickly, here are the outstanding features of these state-of-the-art tubes:

88 and 73

The numerals 88 and 73 have been a tradition in communications language for almost 120 years. The older of the two, 73, appeared in 1853, meaning "My love to you." In 1857, the first official definition made it a "fraternal greeting between operators." Two years later, 1859, Western Union made "73" a part of their "92 Code" to indicate "Accept my compliments." The final change came in 1895, when "73" meant "Best Regards" for the telegraph, and later for radio operators.

"88" never received the formality of an official listing until it was adopted as one of the "Ham Abbreviations." It had been one of the telegraph operators' traditional terms since well before the turn of the Century. During the First World War, "88" was used by the U. S. Army Signal Corps, again strictly as an operator's abbreviation in unofficial communications. At the close of WWI, "88" achieved official status as a part of amateur radio terminology: "love and kisses."

Louise Ramsey Moreau,
WB6BBO/W3WRE



8873
CONDUCTION COOLED
ANODE




8874
AXIAL COOLED
ANODE



8875
TRANSVERSE COOLED
ANODE

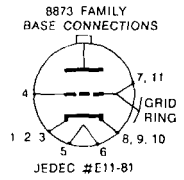1. Up to 1000 watts PEP input per tube to 432 MHz. Typically, 2000 volts at peak dc plate current of 500 milliamperes.
2. Indirectly heated cathode. No expensive filament choke needed for grounded grid HF operation as filament is electrically isolated from cathode.
3. Easy to drive. Extremely low grid interception plus EIMAC's exclusive self-focusing cathode combine to provide high power gain, high overall efficiency and low, low intermodulation distortion.
4. May be driven to full rated input with solid state driver in many cases.
5. Inexpensive (\$1.25) socket. No air ducting required. No expensive glass chimney. 11-pin low inductance base and VHF grid ring provide excellent intra-stage isolation.
6. Heat sink cooling available to full anode dissipation.
7. Tubes may be mounted in any position, greatly aiding circuit layout.
8. And, of course, no bulky screen or bias supply needed!



Another example of EIMAC's ability to provide tomorrow's tubes today!

Here are the numbers to prove it:

The EIMAC 8873 is a grounded grid triode designed for conduction cooling to a heat sink. See this 1971 design in tomorrow's ham gear.

The EIMAC 8874 is electrically equivalent to the 8873 but has a 400 watt anode designed for axial-flow, forced air cooling.

The EIMAC 8875 is also similar to the 8873 with a 300 watt anode designed for transverse air cooling with a quiet and inexpensive "phono motor" fan.

A pair of any of these exceptional triodes will fit in the palm of your hand. And will provide you a full 2000 watts PEP input for voice. They're rated for continuous RTTY service, too. We've built a single tube kilowatt 432 MHz stripline amplifier. It'll run 50% overall efficiency with 25 watts drive. More than adequate for successful moonbounce operation!

14 MHz DX operation . . . RTTY . . . moonbounce at 432 MHz . . . widely separated goals, but all met by one family of rugged, ceramic/metal grounded grid triodes, by EIMAC.




**TYPICAL OPERATION,
INTERMITTENT VOICE SERVICE TO 30 MHz**

Plate Voltage	Zero-Signal Plate Current	Single-Tone IVS Plate Current	Useful Power Output
2000 V	22 mA	500 mA	587 W
Peak Drive Power	Cathode Voltage	Resonant Load Impedance	Intermodulation Distortion Products
26 W	+8.2 V	2140Ω	3rd order: -35dB 5th order: -36dB

Write to EIMAC for full details and suggested circuitry for this new family of tubes. The 8873, 8874 and 8875. And 8873 to you. EIMAC, 301 Industrial Way, San Carlos, California 94070. Phone: (415) 592-1221.



division
varian

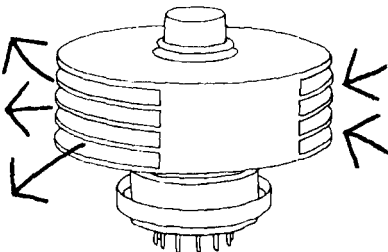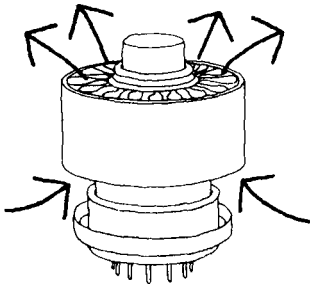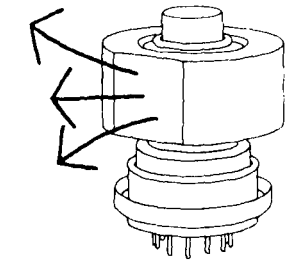

inexpensive swr indicator

**A simple,
easily constructed device
that indicates
behavior of your feedline
at any point**

The fact that this standing-wave indicator is inexpensive in no way detracts from its usefulness as a measuring instrument in the ham shack. It's not an in-line device and is not connected to the transmitter. Therefore it contributes no insertion loss and doesn't disturb the circuit with which it's used. It is simply an rf-current loop connected to a half-wave rectifier that actuates a sensitive dc microammeter.

antenna feedlines

I believe it's self-evident that there's no such thing as a perfect antenna. This leaves the ham with a choice of alternative compromises. He can erect a dipole antenna, which seems to be the most popular on the four lower-frequency amateur bands. Then comes the decision as to the best method of feeding the dipole. More and more hams are using RG-8/U 50-ohm coaxial cable. The reasons are low cost, trouble-free service, and high efficiency.

The low impedance of RG-8/U dictates a current-fed system. It's well known that the feedpoint impedance of a half-wave dipole is closer to 70 than 50

ohms. This means that a mismatch will exist between the feedline and the antenna, which is a starting point for a whole series of loss parameters.

cut-and-try matching

One of the usual ways of compensating for the mismatch between 50-ohm line and the antenna feed point impedance is to start cutting the line, which may partly reduce mismatch loss to a minimum. Another method is to use some type of matching device between transmitter and antenna so that the transmitter is looking into the terminating impedance for which it was designed. This involves added expense, so the average ham uses the cut-and-try approach until the transmission line electrical length is close to a half-wavelength or multiple thereof at the operating frequency. When this condition is met, the transmitter will load properly.

All the cut-and-try matching method does is improve the transmitter-to-line match; it does not improve the impedance match between transmission line and antenna. Transmission lines with a characteristic impedance of 70 to 75 ohms present a better match to a dipole, but this line is more expensive for the maximum legal power. Therefore, most hams use the more inexpensive 50-ohm cable and live with the consequent impedance mismatch.

Any mismatch — at the antenna or transmitter or both — can be indicated to a varied degree by an swr meter, which is generally inserted between transmitter and the load. When the swr meter indicates a 1:1 ratio, this means that the transmitter is presented with a load whose impedance is equal to that of the

J. A. Houser, WB2GQY, 23 Washington Street, Rensselaer, New York 12144

transmitter output circuit. It *does not* necessarily indicate that the transmission line is matched to the antenna.

matching at both ends


How then, you might well ask, can one tell how closely the feed line is matched at the transmitter *and* the antenna? Merely by building and using the swr indicator described here. Because this instrument will indicate the standing wave ratio at any point, and therefore at *all* points along the feedline, it is much more useful than the ordinary swr bridge/indicator usually employed.

If you doubt what I'm saying, just take that swr bridge you've purchased and insert it into your transmission line at various distances from your transmitter by adding lengths of line, and you'll see immediately what I'm trying to put across. You'll find that the swr meter reads differently for each length of cable added. If it doesn't, pat yourself on the back, because you have a near-perfect impedance match between your rig and the antenna.

construction

The swr indicator is simple to build, as the photo shows. Total cash outlay for parts will be somewhere between \$5.00 and about \$14.00, depending on how

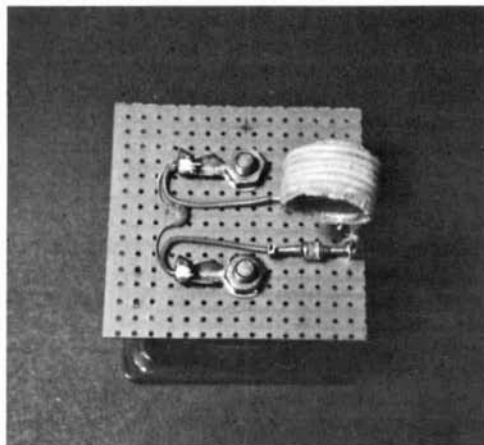Business end of the simple swr indicator. An inductor, diode rectifier, and a few simple pieces of hardware make up the circuit.




much you want to spend for the most expensive component — the microammeter. A complete parts list is provided in **table 1**.

The coil is constructed with no. 14 dcc wire. Six turns are wound on a 3/4-inch-diameter dowel, with one layer of Saran wrap between wire and form to make coil removal easy. A coat of polystyrene dope is then applied to the coil to make it rigid.

A 20-microamp meter makes a sufficiently sensitive indicator, which will indicate currents as low as 1 microamp — sufficient for very low-powered transmitters.

I used a 1N34A diode rectifier, as it

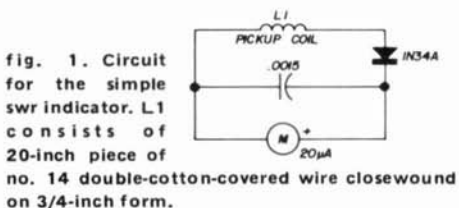

exhibits little frequency sensitivity from the lowest ham band to 250 MHz. Sufficient indication was obtained on all bands, so no tuned circuit was used. However, the sensitivity can be increased for one particular frequency by connecting a variable capacitor across the coil.

The coil and diode were mounted on a piece of perf board, which was mounted directly onto the two machine screws at the rear of the meter. Watch the rectifier polarity — the positive end is connected to the positive side of the meter, and vice versa.

The only other component is a 1500-pF ceramic capacitor mounted across the meter terminals to bypass rf around the meter movement. The current is small, so solder well.

operating principles

Quite heavy current flows in the center conductor of a coaxial cable. The same current also appears in the outside braid. The only difference is that the current is concentrated in the inner con-

table 1. Parts list for the inexpensive swr indicator.

quantity	Component
1	20-microampere meter
1	1N34A diode
1	.0015 μ F ceramic capacitor
1	perf board, 2- $\frac{3}{4}$ in. square
2	meter connecting lugs, washers
3	.065-in. connectors
1 length	no. 14 dcc wire, 20 in. long polystyrene coil dope 1 x 2 in. plastic sheet solder and hook-up wire

ductor but is diffused to a great extent in the outer braid, which is capable of conducting about ten times the current in the inner conductor. However, the same amount of current is carried by the braid. It is this diffused, very minute current, that is indicated by the swr meter.

using the instrument

The outgoing current and any reflected current in the feedline will add and subtract in the feedline to form nodes (high current) or near-nulls (low current) at various points, which are generally unpredictable. Sometimes a device called a transmatch is connected between transmitter and feedline to reduce the difference between these two currents; i.e., to tune the line. Such devices introduce some loss into the system.

The swr indicator described here is not an in-line device. It is slipped over the transmitter-end of the feedline, and the feedline reconnected to the transmitter. The transmitter is then turned on, but not keyed. Then, while the indicator coil is held in one spot on the line, the transmitter is keyed for length of time to make one dot. The meter should show an indication. The procedure continues as follows:

Slip the device along the cable a few feet, and again key a dot on the transmitter. This reading will probably be higher than the first. Either way, it will indicate a standing wave on your feedline.

Mark the feedline at one-foot intervals as far as possible with a

light-colored crayon. Generally, there will be from 6 to 15 feet of line inside the shack that you can so mark. Move the coil along the line, key the rig and record the data. At one point you'll get a maximum reading, either side of which the indication will decrease. At another point on the line you'll get a minimum reading, either side of which the reading will increase. In my case, a node and null were obtained in just 6 feet of line, so I knew I had a high swr. If your swr is low, you may have to move the device along the line a greater distance to determine where node and null occur.

determining swr

Once you have recorded the readings on the meter, merely divide the lowest into the highest reading. The quotient is a sufficiently accurate indication of swr for most ham purposes.

My feedline runs outdoors parallel to the ground for about 20 feet before heading up to hang at a right angle to the dipole. I used a coat hanger bracket to hold the meter onto a wood pole; this arrangement was slid along the cable to take additional readings. I obtained the same node/null readings as on the indoor section of line, so this procedure may not always be necessary or convenient. These indications, of course, occurred at distances further apart at 40 meters than on the higher bands.

conclusion

If, by chance, your swr is *really* low; i.e., very close to unity, this fact would be immediately obvious due to the very slight difference in meter readings over a quarter-wavelength of line at the operating frequency.

The main advantage of this little device over an in-line instrument, such as the swr meter, is that no insertion loss or mismatch occurs between transmitter and load. Such loss may be significant at certain frequencies and power levels.

ham radio

STEP UP TO TELREX

Professionally Engineered Antenna Systems

Single transmission line "TRI-BAND" ARRAY

By the only test that means anything . . . on the air comparison . . . this array continues to outperform all competition . . . and has for two decades. Here's why . . . Telrex uses a unique trap design employing 20 HiQ 7500V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-band performance.

ONLY TELREX GIVES YOU ALL THESE FEATURES . . .

- Power rating 4 KW PEP . . . rain or shine
- Wind rating survival 110 MPH
- Patented broad-band coaxial Balun
- Heavy-duty steel gusset mounting plate
- Aluminum boom 2 in., 2½ in. O.D. x 18 ft.
- Large diameter, .058 wall taper-swaged dural elements for minimum

weight and exceptional strength to weight ratio

- Stainless steel electrical hardware

With a Telrex Tri-band Array you get 49 lbs. of educated aluminum engineered and built to provide many, many years of performance unmatched around the world by any other make. Longest element 36 ft. Turning radius 20 ft. Shipping weight 65 lbs. Shipping container 13 in. x 5 in. x 13 ft.

Note: If not available from your dealer, order direct. You'll get fast, personal service.

Telrex Labs are design engineers, innovators and manufacturers of the world's finest ¼ to 160 meter communication systems and accessories priced from \$25 to \$25,000.

For technical data and prices on complete Telrex line, write for Catalog PL 70.

MONARCH TB5EM/4KWP

\$315

FOB Asbury Park, N.J.

OTHER
MULTI-BAND ARRAYS
AVAILABLE

BALUN



TRAP



TYPICAL TELREX MONOBAND ANTENNAS

Model 15M317 - 15 meter 3 element rotary, 10 DB gain, 4 KWP power rating, 2½" O.D. x 17' boom	\$165.00
Model 20M326 - 20 meter 3 element rotary, 10 DB gain, 8 KWP power rating, 3½" O.D. x 26' boom	355.00
Model 2M5C - 2 meter 6 element array, 14 DB gain, 300 W power rating, 1" x 9' boom	18.50
Model 2M814C - 2 meter 8 element array, 16.5 DB gain, 300 W power rating, 1.375" x 14' boom	32.50
Model 6M5C - 6 meter 5 element array, 13 DB gain, 400 W power rating, 1.5" x 16' boom	39.00

Communications and TV Antennas

SINCE
1921

telrex LABORATORIES

Asbury Park, New Jersey 07712 201-775-7252

fire protection

in the ham shack

With a few
simple precautions
the electrical
and fire hazards
in your shack
can be minimized

Hot rocks and hot receivers are fine to have around the ham shack, but not when they are caused by a "hot house" — in other words, *fire*. Wherever there's electrical gear, there's always the chance of fire. Furthermore, there is always other fire-prone stuff either in use or lying around the busy shack.

It shouldn't take much talk to convince any serious ham he should make a fire-safety check at regular intervals. The only trouble with this plan is that many fire-prevention precautions are so darn simple that they get overlooked. Let's look over some of the commonest hazards, and work up a check list to keep from missing any.

electrical fires

Hams have a special problem. A fire in the ham shack is always likely to be or become an electrical fire, because there is always electric power around. This situation demands special precautions. You can't just pick up a bucket of water and heave it on. (Assuming normal equipment in your shack includes a bucket of water — mildly unusual for a radio station, you must admit!)

First, what is an "electrical fire?" Well, it always begins with an arc. When in-

sulation breaks down, or the applied voltage is too high for the insulation, an arc "happens." Temperatures in even a tiny arc get pretty high — up into the thousands of degrees.

The heat can melt ordinary insulating

insulated wire, ceramic insulators, chassis coated with Teflon, and liquid asbestos sprayed over the whole thing... all would help, but would skyrocket the cost and be a lot of trouble. There's an easier answer — just give the thing better protection. If you can stop an arc as soon as it starts, you're in; the unit will easily keep its own cool. One way is simply by removing the power.


fuses as friends

The easiest way to stop an electrical fire is to keep it from getting started. What that boils down to is fuse protection on *all* electrical equipment in the shack! You might have the dangerous idea that "Aw, what the heck! It's only 110 volts!" That little ol' 110 volts has all the current available it needs to burn your shack to the ground. Current is what makes an arc so hot and destructive. (An arc-welder puts very low voltage on its electrodes, but the dozens of amperes that flow in them can melt steel.)

Fuses are affected mainly by current. The voltage rating you see on a fuse is put there so you won't use it in some circuit where the voltage is so high that an arc could form *across the fuse* after the fusible wire inside has melted. The principle of correct fusing is: use a fuse that can carry the normal current load, but will open up instantly whenever there is a serious current overload (such as caused by an arc).

There are also small circuit breakers, which do the same job of protection. Chassis-mount circuit breakers come in ratings from 0.325-amp up to 7.0 amps. The kind that go in the ac line range from 5.0 amps to any size you need. However, the small ones will protect ham gear.

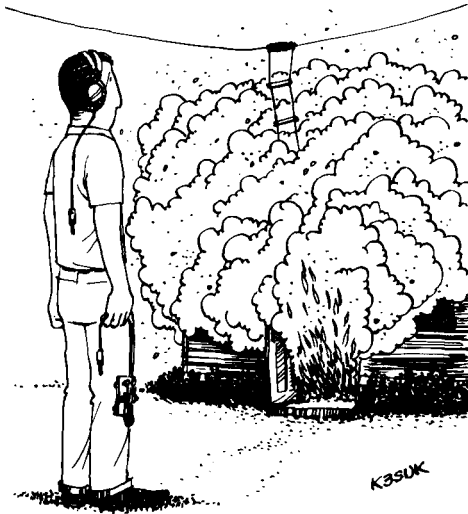So, there's the first point for your fire-prevention check check list. Make sure every piece of gear in the place, down to the soldering iron, is protected by fuses of the right size! When you build



Fuse it . . .

material, crack ceramic insulators, and raise the dickens in general. It can even make insulators into conductors, by carbonizing them! Phenolic and similar insulators turn into carbon when they're burned, and away we go with more arcing. Carbon encourages the arc, which gets hotter, which carbonizes more of the insulator, and so on and on. The heat generated melts other insulation on nearby wiring — which can start still more arcs. You can wind up with a real mess.

You could build a chassis that is absolutely fire-safe, if you want to. Glass-

anything, even kits, if the designer didn't use fuses where he should have, you add them! There is a simply amazing number of units that have no protection at all, or not enough.

The diagram in **fig. 1A** shows two places where they'll do the most good. If your rig uses the popular bridge rectifier circuit as in **fig. 1B**, the secondary fuse is best put in the dc output circuit. A short in one of the rectifiers or filter capacitors would have to blow the primary fuse.

You need to know only one thing to add a fuse: how much current the equipment draws normally. Add a little safety

is flowing (automatic Ohm's-law computer). On factory-built gear, there is a rating-plate, usually near the line cord. Divide the wattage by 115 to calculate the primary current.

If you have some piece of gear that needs a fuse, but the chassis is so crowded it would be hard to mount, try a "fusible plug" on the line cord. A pair of glass cartridge fuses, which can be any size from ¼-amp up to 20-amp or more, fit into push-in clips. To replace a blown fuse, you just push it out of one end with a stick or kitchen match, and push the new fuse in.


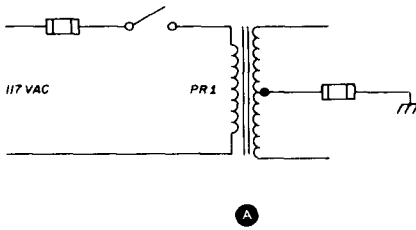


fig. 1. Methods of fusing power supplies.

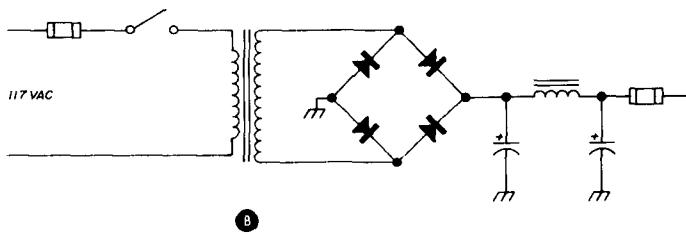

factor of about 50%. Up to about 10 amps, the fuse rating can be about double the normal current; in the higher values, up to 15 or 20 amps, use a smaller margin.


To find out normal current for a B+ fuse, insert a dc milliammeter at the point where the fuse is to be connected. Primary fuses aren't that easy to figure, since ac ammeters aren't common. Easy way: hook a 1-ohm wirewound resistor (big watts) in series with the primary, and read the ac voltage across it with the equipment operating at full load. A 1-volt drop means 1 amp of alternating current

So, the fuse is your answer. You can't usually clear a short once the arc has started, so you had better get power off that circuit as quickly as you can. The best way is with a fuse. Without current, the arc must stop. Result: no more fire hazard.

behind the wall outlets

An important factor in fire safety is the ac wiring. If you live in a house more than 20 years old, look it over. The fixtures (outlets, switches, etc.) used then weren't as good as those now. Besides, they're 20 years old. Wall outlets and

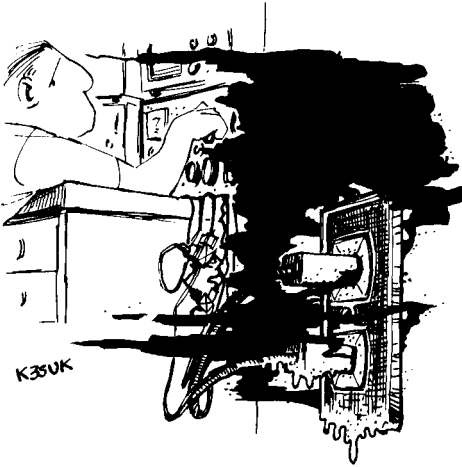receptacles *were* rated at about 600 watts, which isn't much today. Plug in a big transmitter, a receiver, and a soldering iron, and you've had it.



Plug in a big transmitter, a receiver, and a soldering iron, and you've had it.

So what happens? The contacts (even if they're bright and clean, which they're not) get hot. This makes them tarnish, which makes them get hotter, which makes them get dirtier, which makes them ... (sound of fire sirens approaching).

Modern outlets have a minimum rating of 15 amps, or 1800 watts, and you can buy 20-amp types for practically the same price. Contacts run cool.

The ac wiring in old houses is often only number 14 solid, which is not very heavy. Maximum current it can safely carry is a measly 4.6 amps. More than that makes the wire get hot. And there you have another fire hazard.

The shack can have surface-type fittings, with Romex cable along the surface of walls or floor, on the underside of the operating bench, etc. However, be sure the wire can carry your maximum load — and then some.

Don't start heavy shack-wiring at an existing outlet-box. This is worse than

useless; it's dangerous. If you tap a wall outlet that happens to be at the end of about 50 feet of number 14 wire, you can heat up the old wire with the overload. If special ham-shack wiring is installed, go all the way to the main breaker-box or load-center, and run new heavy wire from there.

If you have a big rig, say a full-gallon transmitter plus a good-sized receiver, those babies are going to draw a pretty good hunk of current. With a kilowatt of rf coming out, the transmitter alone can use up 2000 watts. The receiver takes another 150 - 200. That's crowding even the best modern outlets.

It would be better to run a special line right into the transmitter cabinet. A pair of standard home-type circuit breakers (one in each side of the line) can mount on the back of the cabinet in a neat metal box. You can also use them as a master switch when you want to work on the transmitter.

the lightning hazard

Lightning is a fire danger you can't always do a whole lot about. With that nice, big four-element "lightning-rod" sticking up outside, you're apt to get a shot once in a while. The basis of all lightning protection is keeping the hot stuff outside the building and shuttling it off to ground as quickly as possible.

Thing number 1 is a good lightning arrester. You can't actually "arrest" lightning, but you can "steer it" some place where it will do the least damage, and where it won't set the place afire. An arrester carries the energy off to ground by providing an easy path for it. The connection from arrester to ground had better be short, heavy, and direct. A too-small ground wire will simply vaporize if it gets a solid hit.

The coaxial transmission lines so popular now are safer than older open-wire lines. You can make a good lightning arrester from the cable itself. Carefully slit the outer jacket, near where the line enters the building. Turn the insulation back, and wrap 8-10 turns of clean,

heavy, bare copper wire snugly around it. Don't solder it; you'll melt the plastic insulation. Cover this with at least two layers of tightly wrapped plastic tape, and spray the outside with a couple of coats of an acrylic plastic like "Krylon Clear." Run the other end of the copper wire *straight down* (don't make sharp bends in it) to an 8-foot ground rod, driven all the way in.

For open-wire transmission lines, a wide-spaced spdt knife switch can be used to *disconnect the transmitter and ground the antenna* when you're not around.

Even with these precautions, a direct hit can wander all over your incoming leads and wires. To minimize the chance of a fire starting, run all transmission lines well away from wooden walls, drapes, and any flammable materials. Even a coaxial transmission line can get very, very hot if it's carrying a lightning surge.



... an 8-foot ground rod driven all the way down.

(We've seen coax line welded to a 100-foot tower, all the way up!)

A system of good grounds is one of your best lightning-damage preventives inside the shack. Run a good, heavy wire from your transmitter cabinet (receiver,

cabinet, too) over to a good ground — cold-water pipe if you must, but the deep rod outside is better. Upstairs shacks must use a very heavy ground cable; you can often get pieces of stranded pole-guy cable from the power company.

A surprising amount of energy is floating around on the ac power lines when you get smacked by lightning. So, proper-sized fuses can do a lot to protect your stuff. With a direct hit, the fuses will vaporize instantly (and the fuse-holder may, too — wait till you see a 2-pound ceramic fuse-holder blown to powder!). However, when they go, they'll leave the circuit open, and there won't be so much likelihood of arcing from the hot power-line to start fires.

diverse dangers

Watch the common things you're apt to forget. Take the soldering iron. It's handy and all that, but it does get plenty hot. Put yours on a heavy stand that can't tip over. A stand with a screen or mesh cover over the barrel is best. Keep rags or scratch-paper away from the barrel of the iron. Be a good housekeeper, and you'll be much more fire-safe.


Now and then you have to use chemical compounds to clean things around the shack. Switches and such things get dirty, and you have to police-up so they'll work again. Be darn sure the cleaner is fireproof. Nobody in his right mind would use gasoline for this, but lighter fluid can be just as dangerous. A little vapor ... a spark ... and BOOM.

Carbon-tet is fireproof, but the vapor can make you pretty sick. The safe stuff is the spray-can cleaners. They're non-flammable, and there are no noxious vapors. Also, they do a better job of cleaning.

If your shack is in its own separate little building, a gas stove for heating can be dangerous, especially the open-flame type without a vent to the outside. Check the connecting hose at the gas outlet often, to make sure there's no leak. Natural gas is bad enough, but bottle-gas is worse in one respect: It's heavier than

air. If there's a leak, a layer of gas forms from the floor up. When the layer gets high enough, any spark (like turning on the shack lights) can set it off. Then, if you don't have a fire, you may have an air-conditioned shack — no windows, and maybe no door (and probably no roof).

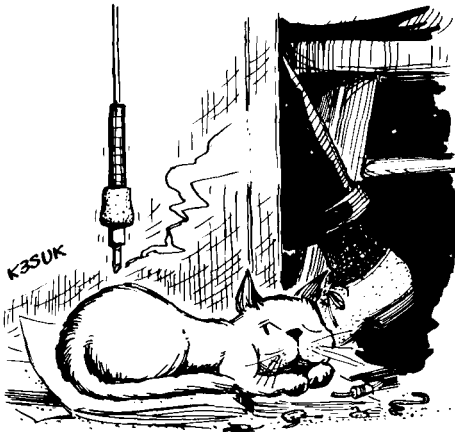Heating gas is odorized so you can smell a leak. So, if you think you smell a skunk when you walk in, keep your



take the soldering iron . . .
it does get plenty hot.

fingers off the switches until you find out what's causing the smell.

if prevention fails

We've mentioned the most likely conflagration-commencers, and how to keep them from starting a fire. What do you do if a fire suddenly blazes up anyway? Easy — grab your fire extinguisher and pour it on. That's fine, but . . . be darn sure you grab the right kind of fire extinguisher! The wrong kind can get you killed.

If there is any electrical hot stuff in or near the fire, and there probably will be somewhere, *DON'T* use a soda-acid, a foam, or a carbon-tetrachloride extinguisher.

The soda-acid types are those old ones

you see hanging on the walls with a hose on top. You turn them upside down to spray the fire. The solution in them is mostly plain water. You can figure out what can happen when a half-inch stream of conductive water hits a live 2,000 volts, with you hanging onto the metal case. You'd better hope you're standing on dry rubber.

The foam types contain mostly water mixed with special chemicals. The popular carbon-tetrachloride types are okay if you're out-of-doors. Carbon-tet is a very good fire-extinguishing fluid, but when it strikes a hot fire, the fumes are deadly poison! They are phosgene, the toxic gas used during World War I. In a small room, and most ham shacks are small, it can put you off the air permanently in just a little while. So, don't use carbon-tet in the shack, unless you have time to stop and put on a gas mask!

There are three types of extinguishers recommended for use on electrical fires. The best known of these is the CO₂-type . . . or "fogbottle," as some people call them. (Don't confuse it with what a fireman calls a "fog nozzle" which is a special hose-nozzle that sprays plain water in a very fine mist.) The carbon-dioxide gas smothers a fire by keeping it from getting enough oxygen to burn. It is harmless to humans.

The second type is a dry-powder extinguisher, which uses plain bicarbonate of soda as the fire-snuffer. The powder is often packaged in long paper tubes; you tear off the cap and toss the powder at the fire. Better ones are pressurized, and spray the powder on the fire.

Freon gas, the propellant in most pressurized spray-cans, is used in another electric-safe extinguisher. Freon provides its own pressure so is easy to spray at the base of the flame. It works just like carbon-tet, but does not liberate toxic fumes.

You can buy any of these three extinguishers in supermarkets and drug stores, in 1- and 2-pound capacities. These sizes are not recommended for big fires. The fire chief will tell you the best sizes are 5- and 10-pounders. These will


put out most fires completely, even though they have a good start.

fire alarms

If you're in the shack when a fire starts, you can combat it instantly. If something heats up while you're out of the shack, that's different. Some kind of automatic fire-alarm system can give you a warning that action is needed and needed right now!

The alarm itself can be a loud bell or anything else with an unmistakable sound. It can be ac-powered, or have a battery if you want a fail-safe system. You can rig up a little charger across the battery.

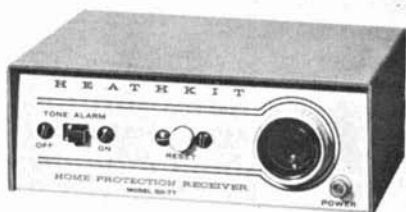You'll need some kind of sensors that will detect heat, flame, or smoke. This can be done in dozens of different ways. You can have a lot of fun thinking up



Heathkit GD-77 receiver alarm sounds high-pitched electronic tone when actuated by GD-97 transmitter.

FIRE-PROTECTION CHECK LIST


1. Electrical
 - (a) Does all equipment have fuses?
 - (b) Are they small enough to give real protection?
 - (c) Is all wiring heavy enough to carry its normal load without heating?
 - (d) Are all outlets and switches in good shape — not dirty or loose?
 - (e) Is the radio gear fully protected by suitable lightning arrester?
 - (f) Are your fire extinguishers the correct type for use on electrical fires?
2. Housekeeping
 - (a) Is the shack neat?
 - (b) Are papers, old magazines, or other flammable materials stacked around in corners?
 - (c) Worse still, are they stacked right on top of hot electrical equipment?
 - (d) Is the workbench soldering iron protected against rags or paper falling on the hot barrel?
 - (e) Is the wastebasket made of fire-proof metal or of meltable plastic?
 - (f) Is the wastebasket full, running over, or kept nearly empty?
 - (g) How are the ashtrays? Full? Clean? Big enough for a long rag-chew?

gadgets that will detect fire.

One of the simplest is shown in fig. 2. It's a clip-type clothespin swiped from the clothes-washing department. Put a couple of thumbtacks in the jaws for contacts. Then rig up something to hold it open until it senses fire. Years ago, a small loop of celluloid movie film was used, which burned instantly. Modern plastics aren't too good; most are fire-proof. However, a loop of fine thread is okay. Use just enough to hold the jaws open against the spring tension. This thread will burn open almost instantly; test it to make sure.

Transistors are heat-sensitive, some amazingly so. When a transistor's temperature goes above a certain point, it will conduct heavily, often going into ava-

fig. 2. Simple heat sensor consists of household clothespin, thumb-tack contacts and loop of fine cotton thread.

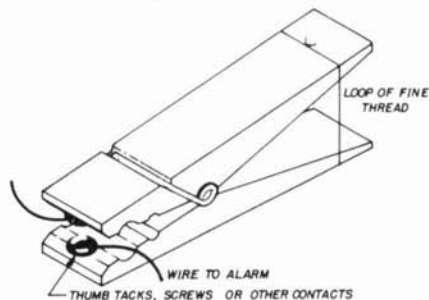




Heathkit GD-87 smoke detector actuates if smoke or 133° F heat is present.

lanche. You could connect the transistor across the input of a small dc-coupled amplifier. A change of resistance in the sensor transistor will trigger a stage that closes a relay.

Thermistors could be used, fastened to parts that might overheat. A bridge circuit will respond whenever the ther-

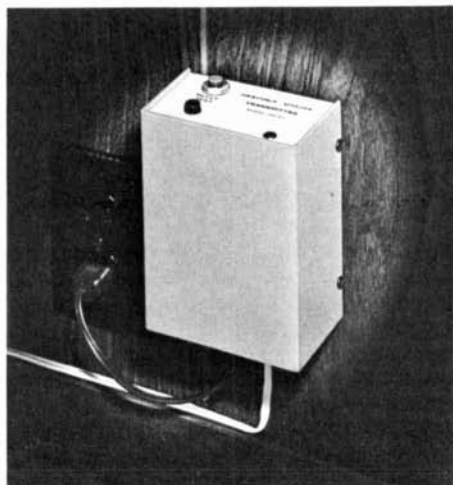Heathkit GD-97 utility transmitter accepts any type switch or sensor to detect hazard you wish to guard against.



mistor's resistance goes down as its temperature rises.

Smoke detectors can be simple: an amplifier circuit with a phototransistor at its input. Mount a pilot light to shine on it through a small light-tight tube. This setup is put just above any equipment where fire might start. If smoke comes up the tube, it will cut down the amount of light falling on the cell; this changes the cell resistance and . . . ding-a-ling-a-ling!

For maximum protection, make your system fail-safe. Design it to react, tripping the alarm, if its power supply or any of its parts fails. The principle is simple. Use a normally closed relay, and design the system so the relay is pulled in — energized — in the cool condition (no fire). If fire is detected, current is cut off and the relay drops out (closing the contacts). If the power-supply fails, or one of the amplifier parts should blow — same thing. No matter what happens, the relay armature is released, and the contacts close, sounding the alarm. The alarm bell must have its own separate battery supply, applied by the relay.

Ham ingenuity will bring out many other ways of doing this important job. Just look for some kind of device that responds to heat, or to smoke, and there you are. If you don't like to design things, there's a kit available from Heath Company; you can see it in the photo. It is wireless and has several kinds of sensors.

do it now

There are wise sayings we could finish with, like: "Don't throw lighted matches into the wastepaper baskets full of old message blanks." But this is kid stuff. If you're not smarter than that, you haven't read this far.

There is a surprising amount of unprotected gear around the average ham shack, if you get right down and look for it. When you find something like that, add the needed protection. It won't take long, it won't cost much, and the peace of mind will more than make up for it.

ham radio

mosfet converter

for receiver instrumentation

The Heathkit SB-610
monitor scope
can be used
in the receive mode
with this circuit

An old saying is that necessity is the mother of invention. In this case the adage is quite precise. I own a Drake TR-4 transceiver and wanted to use a Heathkit SB-610 monitor scope to observe signals in the i-f passband of the TR-4 receiver section. However, the TR-4 i-f is 9 MHz, while the vertical amplifier in the SB-610 is only capable of responding to signals up to 6 MHz. This article describes a simple local-oscillator/mixer I built to put the TR-4 receiver i-f passband where the SB-610 could handle the frequencies involved.

Robert A. Schiers, Jr., WA9ZMT, 5522 Laurel Hall Drive, Indianapolis, Indiana 46226

The SB-610 vertical amplifier has a peak sensitivity of 70 mV/inch (rms) of the vertical deflection if the vertical amplifier is tuned to 455 kHz. This is in contrast to 600 mV/inch at 6000 kHz. A mixer is obviously needed, and, as can be seen by comparing sensitivities, 455 kHz offers the best response.

A tube-type mixer involves cumbersome components for heater and plate power. I, therefore, decided on a transistor mixer, which requires only a small battery.

conversion gain

A conventional bipolar transistor mixer, operating in the driven-emitter configuration, requires substantial drive from the local oscillator. Furthermore, this circuit gives conversion gain. Conversion gain is defined as

$$\text{gain in dB} = 20 \log_{10} E_{\text{out}}/E_{\text{in}}$$

where

E_{out} = converted-frequency output voltage

E_{in} = amplitude of the voltage to be converted as presented to the mixer transistor base

After reading some articles on the dual insulated-gate mosfet mixers, I decided that this device fulfilled the goals of this project; i. e., simplicity, light loading of the local oscillator by the mixer, and a conversion gain of up to 18 dB.

the circuit

The converter schematic is shown in fig. 1. The LO signal is applied to gate 2 of the 3N159, which must be biased to 4 volts by the divider across this part of the circuit. Both gates of an igfet present a very high impedance to the driving signal, usually of the order of 100k ohms. The rf signal to be converted is applied to gate 1, where no special biasing is needed. However, this gate is tied to ground through a

local oscillator

The diagram shows a typical circuit available from International Crystal.* The oscillator is specified for 0.2 volt across a 50-ohm load. The obvious impedance mismatch is unimportant in this application, because distortion and power transfer are not an issue when trying to obtain a voltage swing across such a high impedance as that presented by the igfet gate.

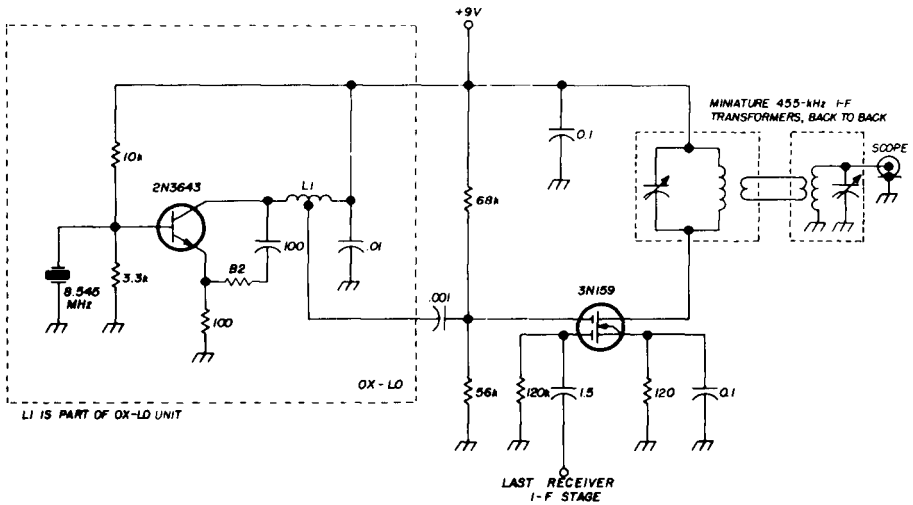


fig. 1. Schematic of the 9-MHz to 455-kHz i-f converter for driving a Heathkit SB-610 monitor scope in the receive mode. The igfet mixer provides 18 dB conversion gain with very low injection voltage.

high resistance to protect the device from static charges or transient voltages.

The 3N159 drain contains two 455-kHz i-f cans. The first i-f can is in the drain to present a high impedance to the converted signal. The other i-f can is used to match the low-impedance output of the first i-f can to the high-impedance input of the tuned vertical amplifier of the SB-610.

* The LO may be obtained from International Crystal Manufacturing Co., 10 North Lee, Oklahoma City, Oklahoma 73102. The type OX in kit form is about \$3.00. Crystals for any frequency can be ordered for about \$4.00. The 3N159 is available from Allied Electronics, 100 North Western Ave., Chicago, Ill. 60680. Cost is about \$2.00 in small quantities.

construction and operation

Construction is not at all critical, nor is the supply voltage. The conversion frequency can be changed easily by tracking the LO frequency 455 kHz below the incoming rf signal. I varied the voltage applied to both the igfet and the oscillator from 4 to 9 volts without any degradation of signal quality or amplitude. Current drain varied from 12 mA at 4 volts to 40 mA at 9 volts. The voltage for the 3N159 can be varied anywhere between 5 and 9 volts with no noticeable deterioration in output amplitude or quality.

The current drain for the entire circuit is approximately 40 mA, depending on

the all "NEW"


CRYSTAL CALIBRATOR

FROM



- 100 - 50 - 25 KC MARKERS
- ZERO BEAT TO W W V
- USES NEW 100 KC CRYSTALS
(included in all units)
- GLASS EPOXY BOARDS
 - VERY COMPACT
2" x 3" x 1/2"
- 3.5 V. OPERATION

\$12⁹⁵ KIT
with
100 KC
CRYSTAL

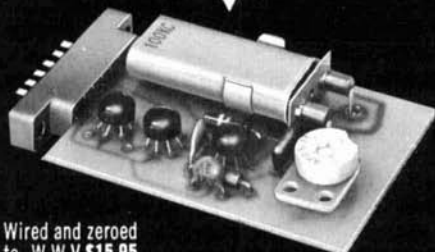

Wired and zeroed
to W W V \$15.95

INTEGRATED CIRCUITS

FACTORY FRESH — NO REJECTS
W/SPEC. SHEET

FAIRCHILD — MOTOROLA

UL 900 BUFFER	80c—10/6.00
UL 914 GATE	80c—10/6.00
UL 923 J.K. FLIP-FLOP	\$1.50—10/9.00
MC 790P DUAL JK FLIP-FLOP	\$2.00—10/18.95
MC 789P HEX INVERTER	} 1.10 ea. 10/9.50
MC 724P QUAD 2 INPUT GATE	
MC 799P DUAL BUFFER	
MC 780P DECADE	\$3.50
MC 767P QUAD LATCH	\$3.50
MC 9760P DECODER DRIVER	\$5.50
THREE ABOVE \$11.95	



R & R ELECTRONICS
311 EAST SOUTH ST.
INDIANAPOLIS, IND.
46225

\$2.00 minimum order FOB Indianapolis.

supply voltage. Despite the impedance mismatch, no problems were encountered in driving the very high impedance of the 3N159 gate.

The coupling capacitor from the plate of the last i-f stage in the receiver was selected for the smallest value necessary to ensure adequate display height on the SB-610.

The reason for the dual 455-kHz i-f transformers was based on impedance-transformation considerations. The miniature transformers available to me had a high-impedance input with a low-impedance output, whereas the input of the SB-610 is about 100k ohms.

precautions

The igfet comes with a shorting clip that connects all leads together. This clip should be left on the device until it is placed in the circuit. Don't allow your fingers to come in contact with any part of the device except the case during installation. A small piece of solder can be wrapped around all leads, then the solder can be removed after installation.

final observations

The RCA 40673 dual-insulated-gate mosfet is zener-protected and may be directly substituted for the 3N159 in this circuit. Such substitution is highly recommended, as the special-handling problem of the device is eliminated.

If at any time you think you may have damaged the 3N159, the device can be easily checked. With a drain voltage of 10 volts and 120 ohms in the source; and with both gates tied to ground through a high resistance (100k), a drop of a few tenths of a volt should be observed across the source resistor. In addition, if gate 2 is biased up 1 or 2 volts, the current will rise sharply to 4 mA or greater, depending on source resistance and drain voltage. Note that the characteristics described pertain to *n-channel depletion-mode fets* only!

I'd like to express my thanks to Leo Bovard, W9SCK, for his help in the development of this project.

ham radio

a simple cw monitor


Did you ever try to send code without using a cw monitor? To have consistently good sending characteristics without a monitor is like trying to drive an automobile blindfolded. Hundreds of articles on cw monitors have been published, but many of them are elaborate in design and expensive to build. The "minimonitor" is quite the opposite — it's the ultimate in simplicity. It costs pennies to build, is extremely reliable, and has a clean, pleasant-sounding tone.

The complete circuit is shown in fig. 1; components are mounted on a 1¼" x 2¼" circuit board. Although I use the mini-monitor with an automatic keyer, it can easily be used with straight or semiautomatic keys. It can also be used as a code practice oscillator; volume is sufficient for group listening.

Perhaps the most desirable features of the minimonitor are its small size and easily obtained components. It is small enough that it can be built into practically any keyer already completed by fitting it into a convenient space.

Choice of parts is not at all critical. Virtually any npn and pnp transistors can be used. The capacitor value can range anywhere from .01 to .05 μ F. The resistor depends upon the desired tone. The

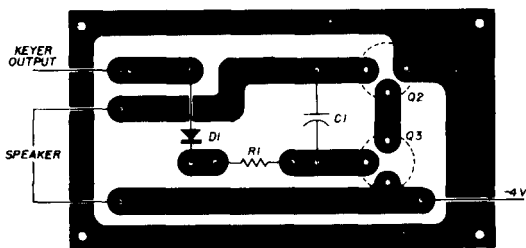Printed-circuit board for the simple cw monitor.



diode is not critical; I used a 200 PIV unit. If you want, a 50k potentiometer can be used in place of the resistor to provide variable tone adjustment. Power to the unit may range from 3 to 6 volts,

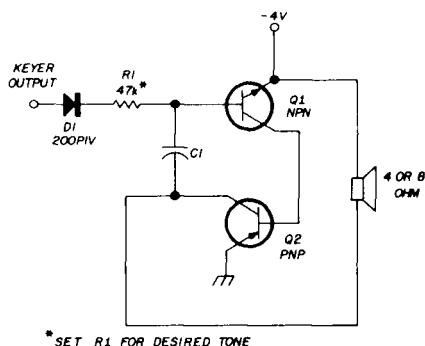


fig. 1. Schematic diagram of the simple cw monitor. Capacitor C1 is 0.01 to 0.05 μ F.


and any small 4- or 8-ohm speaker may be used.

If you're skeptical about using the minimonitor, dig the parts out of your junkbox and connect them on top of the kitchen table. With a small 4.5-volt battery for power you'll get an idea of how the oscillator sounds. You'll also be able to select parts for the circuit board since tone quality depends on component choice.

Few amateurs realize just how simple a keying monitor can be until they get down to the basic principles of the more elaborate types. The simple minimonitor described here will provide trouble-free service for the life of the keyer, and help you develop and maintain a good "fist."

ham radio

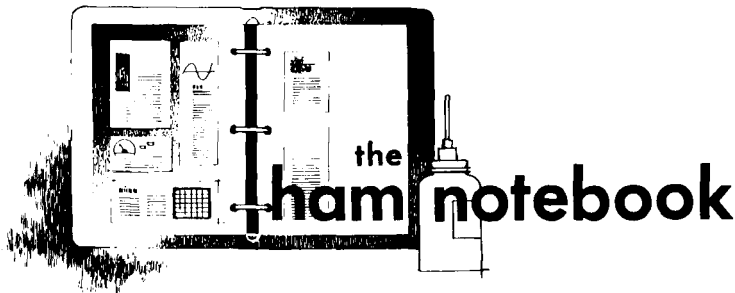James Wiesmueller, WA90HR, 315 East Freistadt Road, Thiensville, Wisconsin



testing unknown meters

A typical 10-megohm or higher vtvm is an excellent tool for testing unknown meters to determine their approximate current ranges without the danger of pinning the needles or burning out the windings.

Set the vtvm to OHMS and the range dial to R x 1 MEG. Connect the test leads to the unknown meter. Move the range dial, one step at a time, through R x 100k, R x 10k, etc., until the meter under test reads upscale.

The maximum current through the meter from a typical 10-megohm vtvm (Lafayette KT-174, for example) is as follows:

range	I max	vtvm 1% series res.
R x 1 meg	0.156 μ A	10 meg
100k	1.56 μ A	1 meg
10k	15.6 μ A	100k
1k	156.0 μ A	10k
100	1.56 mA	1k
10	15.6 mA	99.1*
1	170.0 mA	9.1*

*0.9 ohm is allowed for the internal resistance of the D cell and test lead.

The effect of the meter resistance on the first four ranges of the vtvm is usually negligible. Don't try this idea with a vom.

The currents will almost surely be much greater than those shown above, and the meter being tested may be destroyed.

Harold E. Brown, W1ONC

adjustment screwdriver

Many transceivers have internal adjustments for the S-meter, final-amplifier bias, carrier null, etc. Trying to get a screwdriver into these adjustments through the perforations in the cover is next to impossible. Here's what I use.

I fashioned an ordinary wire coat hanger into an adjustment tool by clipping the hanger about 1½ inches each side of where the Y is formed. Then I straightened this section until it was perpendicular to the hook. Next, I straightened the hook and filed the end until it was flat enough to fit into the transceiver adjustment slots. The finished tool should have the appearance of a T.

The tool is small enough and long enough to go through the holes in the transceiver cover, and it is strong enough to withstand the torque of some of the more stubborn adjustments. It's also handy for tapping those sticky change-over relays that hang up once in awhile.

Dan F. Davis, WAØKGS

75A-4 modifications

To anyone who has owned and cherished a 75A-4 receiver for many years, as I have, the discovery that it has developed sensitivity and frequency-stability problems is like discovering a trusted friend to be unfaithful. Here are some solutions to these problems, plus a hint to improve the receiver's audio response.

insensitivity

Loss in sensitivity first appeared as a loss of one or two S-units after about an hour of operation. (I use the "calibrate" signal as a sensitivity reference for a specific S-meter reading at 14.2 MHz, with a 50-ohm dummy antenna.) Sensitivity loss gradually increased until it was 6 or 7 S-units after 15 minutes of operation.

After several frustrating weeks of signal tracing and a new set of tubes, I was about to give up when I stumbled onto the answer. The "rejection tuning," which is a bridged-T filter, has a sharp, deep null when properly adjusted. I noticed that when the set was first turned on, the "rejection tuning" behaved normally, but after warmup the null deteriorated and finally became useless. It seemed as though a comparatively low resistance was across the bridged-T inductor, L26.

The schematic shows one-half of V7, the Q-multiplier tube; some resistors; a choke; and C71, a 1000-pF capacitor in series across this inductor. Checking with a vtvm between ground and either side of L26 showed a *positive* voltage, which varied between 2 and 5 volts. I disconnected C71 from the inductor, but left the other end connected to the plate of V7 (and hence, B+). When I touched the vtvm probe to the free end of C71, I found the positive voltage to be even higher and still varying.

I checked other grids in the receiver with the vtvm and found four other leaky capacitors. When these were replaced, the sensitivity problem cleared up com-

pletely. A vtvm must be used, however. A 20k-ohms-per-volt vtvm simply shorts the leaky voltage to ground and gives no indication.

probable cause

When checking for leaky capacitors the set must, of course, be on and the rf gain control positioned fully clockwise. If the rf gain control is backed off, the higher bias voltage will swamp the leakage voltage on some of the grids. I can only conjecture as to the cause of the capacitor leakage; but my friend Ray Wood, W9SDY, suggests migration of the silver coating on the mica. Until a better explanation comes along, I'll accept Ray's theory. Migration is supposed to accelerate in the presence of a dc voltage. However, some unused mica capacitors of the same type and vintage showed leakage to some degree; new units showed no leakage at all.

frequency instability

The frequency instability problem became evident in exactly the opposite manner. The pto frequency jumped around for about ten or fifteen minutes after the set was turned on, then settled to its usual rock-steadiness.

According to an article in *QST*,¹ instability in the pto can be attributed to several factors, including capacitor C205, a 51-pF mica of the same type as those giving sensitivity problems. When I originally read the *QST* article, I assumed C205 might be changing value. However, after the previous experience with leakage, I found that a vtvm check between pin 1 of V15 and ground showed the telltale positive voltage.

After the set had been on for 10-15 minutes, the positive voltage disappeared, and the pto became stable. I suspect that, since a current flows through the capacitor when the pto is operating, the leakage path burns off after several minutes, then regenerates when the set is turned off. At

ALL SOLID-STATE SSB TRANSCEIVER —



- Complete single-band SSB transceiver 4 to 5 watts PEP output 15, 20, 40, or 75 mtrs.
- VXO tuning up to 100 KHz or 2 fixed freq.
- Suitable for dry battery operation.
- Light weight, small size makes excellent portable - boat, aircraft, field or mobile.
- Contains 15 transistors, 1 MOSFET, 2 darlington amps., 1 I.C. and 17 diodes. Four-pole filter.
- Some options available to customer requirements.
- Furnished with spare switching and final amp. transistors, dummy load and extra plug.

JUSTIN, INC.

2663 NORTH LEE AVENUE
SOUTH EL MONTE, CALIF. 91733

CQ de W2KUW

5% BONUS PAID FOR
EIMAC AND VARIAN TUBES

ESPECIALLY:

4-65A, 4-125A, 4X150A, 4-250A,
4CX250B-K or R, 4-400A, 445A,
4-1000, 4CX1000, 4CX5000, X13,
etc.

EQUIPMENT:

R390A, GRC 106-108, PRC 9, 10,
25, 74, 77, URC9, VRC 12, etc.

The TED DAMES Co.

308 HICKORY ST., ARLINGTON, N. J. 07032

Phone: 201 998-4246

any rate, the pto remained stable after installing a new capacitor for C205.

audio response

I became increasingly annoyed by an emphasis on the bass of the audio response as both the 75A-4 and I grew older. I realize that as we grow older our ears become less sensitive to the higher frequencies, but retain their response to the lower frequencies, thus accenting the bass.

A newly acquired audio generator provided the opportunity to check the 75A-4 audio response. A surprisingly high peak (10 dB) appeared at 100 Hz, which decreased sharply on either side, to a level output between 300-3000 Hz.

Reference 1 suggested that feedback resistor R71 be removed. I tried this when I first read the article, but I didn't like the increase in audio, which required riding the af gain control; nor did I like the unpleasant audio quality.

The audio-signal generator showed that, with resistor R71 disconnected, the 100-Hz peak disappeared and the entire audio response became a broad peak centered around 3200 Hz. Substituting a 100-k resistor for the 33k originally used for R71 eliminated the objectionable 100-Hz peak and smoothed the entire audio response. A 1-meg resistor in series with the af gain control improved its action.

less bass response

Another source of bass emphasis is the cathode network associated with the noise-limiter diode, V 12. Since the limiter is useless for cw and ssb, I removed V 12 and inserted the leads of a 0.005- μ F capacitor into the tube socket (holes for pins 2 and 7). This connects the detector output directly to the af gain control and eliminates the cathode network. If you would like even less bass, use a 0.001 μ F capacitor.

reference

1. P. Rockwell, W3AFM, "Station Design for DX," *QST*, November, 1966, p. 53.

Albert G. Shafer, W4SD

HAL DEVICES



**HAL 311BC
ELECTRONIC
KEYER
\$53.00**

THE most versatile keyer available. Send for full details on the HAL 311BC and the complete line of HAL electronic keyers. There is a model to fit your requirement and budget from \$16.50 to \$53.00. Shipping extra. Now available in kit form for even greater value.



HAL MAINLINE ST-6 RTTY TU

Complete parts kit for the W6FFC ST-6 now includes all parts except cabinet. Only 7 HAL circuit boards (drilled G10 glass) for all features. Plug-in IC sockets. Custom transformer by Thordarson for both supplies, 115/230V, 50-60Hz. \$135.00 kit. Wired units available. Shipping extra. Write for details.



**HAL
TOUCHCODER II
KIT
\$55.00**

Complete parts kit, excluding keyboard, for the W4UX CW code typer. All circuitry on one 3 x 6" G10 glass PC board. Plug-in IC sockets. Optional FM repeater ID, contest ID, and RTTY features available. Keyboard \$25.00. Shipping extra. Write for full details.



**HAL RT-1
TU/AFSK
KIT
\$51.50**

HAL DIP BREADBOARD CARD

Drilled G10 glass PC board accepts 6 16 pin DIP IC's in plug-in sockets. Each IC pin fanned out to two pads. Plugs into standard 22 pin edge connector (.156" finger spacing). \$5.50

All TU and AFSK generator circuitry, including PS, on 3x6" G10 PC board. 850, 170, and CW 10 shifts. Zener protected transistor loop switch. High and low impedance audio output. Price \$45.00. Shipping extra. Write for full details. HAL Designer Cabinet for the above \$6.50. 3 pole Butterworth filter drilled PC board \$2.50.

DOUBLE BALANCED MODULATOR KIT

For the DBM in March 1970 Ham Radio 7/8 x 2" drilled G10 glass PC board
4 HP-2800 hot carrier diodes matched by HAL.
2 Indiana General CF102-Q1 toroids.
Wire and instructions included. \$6.50

HAL MAINLINE ST-5 RTTY TU

ST-5 kit now includes drilled G10 glass boards, custom Thordarson transformer, meter and metering components. Boards accept both round and DIP 709 IC's. \$50.00. Less boards, meter & meter components \$37.50. Boards only \$6.00. Shipping extra.

HAL 25KHz MARKER GENERATOR

Generates 50 KHz or 25KHz markers from 100 KHz oscillator (not supplied)
Drilled 1 x 2" G10 glass PC board
Strong markers to 148 MHz. Divides any signal up to 2MHz by 2 or 4. \$4.25 kit form.

HAL MAINLINE AK-1 AFSK OSC

HAL now offers a parts kit for the AK-1 AFSK osc. Drilled G10 glass PC board plugs into 12 pin edge connector for compatibility with the HAL ST-6, or for ease of use alone. Requires 12vdc. \$27.50. Shipping extra. Write for parts list.

Hot Carrier Diodes: HP2800 90¢, 12/\$10.00 Matched by HAL 4/\$4.25
IC's: 1 µL 900, 914 60¢ 1 µL 923 90¢
MRTL MC790P, MC890P \$2.00, 10/\$19.50
MC724P, MC789P, MC792P, MC725P \$1.05, 10/\$9.50
Also available: MC723P, MC788P, MC880P, MC767P, MC9760P.
OP AMP: SN72709N (DIP), SN72709L (TO-5), \$1.25
TOROIDS: Indiana General CF102-Q6, CF102-Q1, CF101-Q2, 50¢
CINCH IC sockets, 14-DIP, 8-ICS, 60¢ HAL DEVICES 50¢
Add 50¢ Postage, send for complete list. Box 365 Urbana, Illinois 61801

ORDERING INFORMATION

Postage is not included in the prices of HAL products. Please add 50¢ on small parts orders, and \$2.00 on larger kits. Shipping is via UPS when possible, and via insured parcel post otherwise. Please give a street address.

HAL DEVICES, Box 365H, Urbana, IL 61801

new products

heathkit wattmeter/ swr bridge



The new Heathkit HM-102 wattmeter/swr bridge covers the frequency range from 1.8 to 30 MHz with wattmeter accuracy $\pm 10\%$ of full-scale reading*. The power capability of this new instrument is 2000 watts with full-scale readings of either 200 or 2000 watts. The built-in swr capability allows proper antenna tuning and transmission line impedance matching. The unit has a nominal 50-ohm impedance and provides negligible loss when inserted in a 50-ohm line. The remote torodial-type detector permits placement of the meter in a convenient location. The HM-102 kit is priced at \$29.95 from the Heath Company, Benton Harbor, Michigan 49022, or use *check-off* on page 94.

*When calibrated on the 40-meter band through 300 feet of RG-58/U into a 50-ohm load.

collins receiver



The new Collins 651S-1 is one of the most versatile general purpose receivers ever developed, providing highly reliable reception from 0.4 to 30 MHz, with tuning phase-locked in 100-Hz steps. Because of the unique tuning system of the 651S-1, the convenience and "feel" of traditional receiver tuning is not sacrificed as a result of using discrete 100-Hz frequency steps. Large changes in frequency are aided by the 0.1-MHz and 1-MHz selector knobs.

Capabilities of the radio include computer programming, independent sideband, narrow band fm, operation from a remote control head, compatibility with secure voice modems, phase-locked or manually adjusted vbfo, and syllabic squelch providing better reception of a weak voice signal in the presence of background noise.

Frequency readout on the front panel is provided by six light-bar devices, each of which consists of a seven-bar fluorescent segment tube.

The receiver construction techniques include Collins multilayer circuit boards mounted in plug-in card installations with blue-line connections. Micro-electronics logic and linear circuits are utilized. The plug-in card technique, along with convenient arrangement of other parts of the radio, provides easy accessibility. The receiver has no mechanical linkages — all tuning and band switching is performed electronically.

For information on the new 651S-1, write to Collins Radio Company, Cedar Rapids, Iowa 52406, or use *check-off* on page 94.

slow-scan television equipment

Robot Research, Inc., has announced a system of slow-scan television equipment that enables you to transmit and receive live television pictures with your existing station equipment. The model 80 slow-scan camera uses an efficient sampling technique that permits operation with everyday room lighting and transmits clear sharp pictures without involved adjustment. Features include digital timing chain, vidicon camera tube, built-in modulation calibration and solid-state construction.

The model 70 slow-scan television monitor demodulates and displays pictures transmitted by another amateur radio station. Simple connections between the monitor and your receiver are all that is required to receive an sstv picture. Included with the monitor are all of the switches and interconnections required to integrate sstv into your station. The monitor features balanced discriminator, automatic sync threshold, phase-locked horizontal sweep and solid-state construction.

The model 80 slow-scan camera and model 70 slow-scan monitor are available from Robot Research, Inc., 1250 Prospect Street, La Jolla, California 92037, or use *check-off* on page 94.

cubical-quad book

Bill Orr's new book, "Cubical Quads," features a wealth of new information not available in the previous edition. The new 2nd edition includes revised quad gain figures, analysis of the quad vs yagi, 4- and 5-element monster quads, miniature quad construction and performance, improved tri-gamma match for three-band quads, charts with dimensions for single- and multiband quads for 6 through 80 meters, as well as construction details for the delta quad, Swiss quad and birdcage quad.

IT'S WHAT'S INSIDE THAT "COUNTS"

Accuracy and stability has been placed first in the design of the TBL-1 Marker. We feel a marker should be more accurate than the receiver it is going to calibrate — so no compromise has been made with quality.

Fairchild, Motorola, JFD, Jan, Mallory, IRC and Keystone components are used throughout. It costs more, but calibrates with the best. Hundreds have been sold to government, amateurs, SWL's, schools and laboratories around the world.

Try one today.



Frequency marker, less cabinet and switch
Specifications: Glass Epoxy Board. Adjustment to zero beat with WWV. Uses 100 KHz crystal (not supplied). 3 to 4 VDC. Compact — 1.75 x 3.75 inches. Install anywhere!

Complete easy-to-assemble kit \$16.50 Wired and Tested \$19.95

SWITCH \$1.00 CRYSTAL ONLY \$3.50
with purchase of any of above

or



SELF-CONTAINED UNIT

The TBL Marker is a complete unit including the circuit board shown at left and powered with 3 "C" type flashlight batteries. Merely connect to your receiver antenna — no internal wiring necessary. A front panel control allows zero beat with WWV.


Special introductory price \$29.95
Less crystal and batteries

POSTPAID U.S.A.

SOLD WITH MONEY BACK GUARANTEE

THE RADIO SHOP, LAB 1

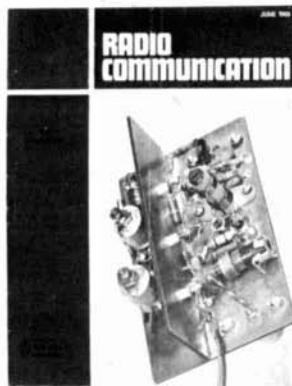48 ELM STREET, NEW CANAAN, CONN. 06840
Tel. 203-966-3553



Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

This is the oldest and most widely read British amateur radio magazine. Published monthly it provides complete coverage including such popular features as: Technical Topics, a monthly survey of the latest ideas and circuits, Four Meters and Down, a rundown of the latest in VHF and UHF and much more.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$9.60 a year.

book division

comtec

Box 592 · Amherst, New Hampshire 03031

This new book also includes information on feeding your quad for maximum swr; clear details on matching procedure; use of baluns; hints for sturdy, inexpensive quad construction; and how to adjust your quad for strongest signals. Quad installation, adjustment, evaluation and maintenance is covered along with quad facts; angle of radiation, directivity, power gain and front-to-back ratio.

"Cubical Quads" is \$3.95 from Comtec, Book Division, Box 592, Amherst, New Hampshire 03031.

heathkit frequency counter



The new Heathkit IB-101 digital frequency counter provides accurate counting from 1 Hz to over 15 MHz with five-digit readout. The Hz/kHz selector switch and overrange indicator give eight-digit capability. The new counter features high input impedance, automatic trigger level for with range input without adjustment, storage circuitry for non-blinking, no-count-up adjustment, and temperature compensated crystal-controlled time-base oscillator. The *automatic decimal locator* puts the decimal point in the right place for any measurement with no need for interpolation or figuring.

The IB-101 uses 26 integrated circuits, 7 transistors, 6 diodes and one mosfet. The dual-gate diode-protected mosfet in the input circuit provides proper triggering over a wide range of input levels. It will operate properly with input levels

from less than 100 mV to greater than 200 volts (depending on frequency). There is no input adjustment, and the instrument cannot be damaged by inputs within the specified range. Input impedance is 1 megohm shunted by less than 20 pF.

The new counter goes from kit to finished counter in about five hours, and complete adjustment can be made in a few minutes using only an a-m radio. No exotic test equipment is necessary. The IB-101 kit is complete with input cable. Priced at \$199.95 from the Heath Company, Benton Harbor, Michigan 49022, or use *check-off* on page 94.

wideband rf power amplifier

The RF Communications has announced a new RF-806 linear amplifier module that features flat response within ± 1 dB from 50 kHz to 80 MHz, and 3-dB bandwidth of 100 MHz. Gain is 47 dB with class-A amplification providing 10 watts with low harmonic and intermodulation distortion.

Input and output are overload protected against overdrive or operation into a short or open circuit. Unit is all solid state and operates from +28 Vdc. Standard options include 75-ohm input impedance and extended frequency response to above 100 MHz or down to 14 kHz. Accessories include impedance-matching transformers and power combiners.

Applications include use as a sub-assembly in test systems or amplifier chains to raise the power level of signal sources and generators without tuning or bandswitching. A-m, fm, pulse, ssb and other modulated signals can be amplified to 10 watts PEP with minimum distortion. Price is \$795. For more information, write to RF Communications, Inc., 1680 University Avenue, Rochester, New York 14610, or use *Check-off* on page 94.

NOW from 

ROSS AND WHITE COMPANY
Electronics

SOLID STATE TONE BURST ENCODERS

(to the frequencies of your choice)



MODEL TE-2
2 tone,
Factory preset
only
\$29.95
postage paid.

MODEL TE-5
5 channel model
Factory preset
only
\$39.95
postage paid.

GUARANTEED FOR ONE YEAR

Use it for 10 days, if not completely satisfied return for a full refund.

- Easy to install, 3 wire hookup, attaching bracket included for car or home.
- Operates from a single factory supplied internal 9 volt battery.
- All frequencies factory preset. Can be field adjusted from 1500 to 2500 cycles. Other frequencies on special order.
- Nominal .4 sec. tone burst length.
- American made commercial grade components on glass epoxy PC board for maximum reliability.

ROSS AND WHITE CO., Electronics Dept. HR-12
50 West Dundee Road, Wheeling, Illinois 60090

Gentlemen:

Send me model tone burst encoder.

Check or money order enclosed. Please set frequencies for

Send additional information. Check

Name

Address

City State Zip

Transceiver: Make..... Model.....

NEED CRYSTALS?



We can supply crystals from 2KHz to 80 MHz in many types of holders.

SPECIALS

Color TV crystal (3579, 545KHz) wire leads	\$1.60	4 for \$5.00
100 KHz frequency standard crystal (HC 13/U)	4.50	
1000 KHz frequency standard (HC6/U)	4.50	
Any CB crystal, trans. or rec. (except synthesizer crystals)	2.50	
Any amateur band crystal in FT-243 holders (except 80-160 meters)	1.50	4 for \$5.00
80 meter crystals in FT-243 holders	2.50	

We have in stock over six million crystals which include types CR1A/AR, FT243, FT241, MC7, HC6/U, HC13/U, HC25/U, HC18/U, etc. Send 10¢ for our 1970 catalog with oscillator circuits, listing thousands of frequencies in stock for immediate delivery. (Add 10¢ per crystal to above prices for shipment 1st class mail; 15¢ each for air mail.)


Special Quantity Prices to Jobbers and Dealers.

ORDER DIRECT
with check or money order to

2400H Crystal Drive
Fort Myers, Florida 33901



scope camera

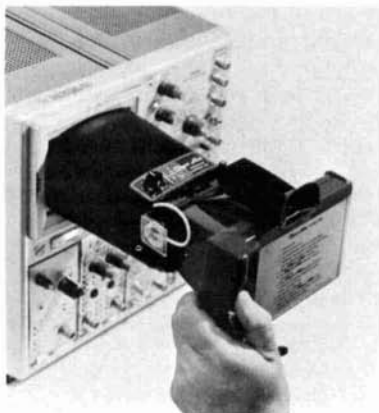

Integrated Controls, Inc., has announced a low cost, hand-held oscilloscope camera set, Scope-Mate, which fits virtually all oscilloscopes. Fitting either three, four or five-inch round or rectangular scope faces, Scope-Mate can capture and record — either one shot or recurring trace — oscilloscope data. A standard Polaroid Colorpack II or III camera, in conjunction with the Scope-Mate hood, provides high-quality, high-contrast, black-and-white oscilloscope pictures in 15 seconds. The object-to-image ratio is one to one.

The Scope-Mate electronic control provides automatic adjustment of camera shutter speed, allowing you to vary photo contrast for perfect pictures.

The camera set, including a Colorpack II camera and Scope-Mate hood sells for \$119.50. The Scope-Mate hood is available separately for \$89.50. Order from Integrated Controls, Inc., Post Office Box 17296, San Diego, California 92117, or use *check-off* on page 94.

MORE 2 METER FM MINI AMPLIFIERS FROM DYCOMM

GIVE US YOUR FLEA POWER
AND WE'LL GIVE YOU HORSE POWER

NOW FOR IMMEDIATE DELIVERY . . .

101-500D: 40W, broadband*, two-meter, FM power amplifier, auto RF antenna switching. Completely ready to go. Just plug in your existing antenna and 10 watt transceiver, add 12-14V and QSO. Size: 3"x5"x6".

Low Introductory Price: \$79.95

101-500B: 10 watts output AM or FM for 2 watts input. Auto relay and connectors are included. Size: 2"x2"x6". Just plug in, add 12V and get out. Price: \$49.95

101-500C: Have 5 watts to spare? This is just the thing. AM, FM, SSB, 20-25W output. You add 12.6V, your own antenna switching, and you're on the air. Size: 2"x2"x6".

Price: Only \$39.95

101-500: For those who want to "roll their own". The highly accepted 2"x2"x6", 12.6V, 25Mw in, 10W out, AM-FM-SSB, power amplifier. Price: Still only \$59.95

All **DYCOMM** Power Amplifiers handle "worst case" load mismatch, overvoltage, under-voltage, have extremely low input/output VSWR, and are fully guaranteed to perform.

Drop us a line for the whole picture.

*Bandwidth allows entire two-meter coverage with no retuning required.

For exciting antennas see our ad page 92.

Call or write Jim, W4MRI

DYNAMIC COMMUNICATIONS, INC.

(305) 844-1323

948-A AVE. E, RIVIERA BEACH, FL 33404

darlington power transistors

Five new series of complementary, power Darlington transistors — the first available in the industry — have been introduced by Motorola. The new silicon

power transistors provide gain up to 2500 (typical) and are available in current ratings from 4 to 16 amperes. With their high gain, the power Darlington transistors can be driven with integrated-circuit milliampere output current levels. The new devices are supplied in 60 and 80 V collector-emitter breakdown voltage ratings (a 100 V rating is available in the 16 A series).

The Darlington incorporate both driver and output transistors plus necessary resistors in one monolithic structure. Thus, the usual separate driver and associated emitter-base resistors employed in a Darlington amplifier are eliminated.

Darlington transistors are useful in relay and solenoid drivers, servo amplifier, audio amplifier and power supply regulator circuits. Because they're available in both polarities, they can be used in either positive or negative ground systems. And, used in pairs, they are especially useful in complementary applications such as direct-coupled pairs in audio amplifiers.

4 ampere MJ4000/MJ4010 series, 1000 minimum gain at 1.5 amp, 60 or 80 BV_{CEO} , 75 watts, TO-3 package.



5 ampere MJ900/MJ1000 series, 1000 minimum gain at 3 amps, 60 or 80 BV_{CEO} , 90 watts, TO-3 package.

5 ampere MJE1090/MJE1100 series, 750 minimum gain at 3 or 4 amps, 60 or 80 BV_{CEO} , 70 watts, plastic thermopad-type package.

10 ampere MJ2500/MJ3000 series, 1000 minimum gain at 5 amps, 60 or 80 BV_{CEO} , 150 watts, TO-3 package.

16 ampere MJ4030/MJ4033 series, 1000 minimum gain at 10 amps, 60, 80 or 100 BV_{CEO} , 150 watts, TO-3 package.


For more information, use *check-off* on page 94, or write to Technical Information Center, Motorola Semiconductor Products, Inc., Box 20924, Phoenix, Arizona 85036.

 DIODES 				
PIV	TOP-HAT 1.5 AMP	EPOXY 1.5 AMP	EPOXY 3 AMP	STUD- MOUNT 6 AMP
50	.04	.06	.12	.15
100	.06	.08	.16	.20
200	.08	.10	.20	.25
400	.12	.14	.28	.50
600	.14	.16	.32	.58
800		.20	.40	.65
1000		.24	.48	.75

CAPACITORS

ALL NEW FULL AXIAL LEADS


1000 MFD @ 12 V	3 for \$1.00 ppd.
5 MFD @ 15 V	5 for \$1.00 ppd.
30 MFD @ 15 V	5 for \$1.00 ppd.
100 MFD @ 15 V	5 for \$1.00 ppd.
1000 MFD @ 50 V	2 for \$1.00 ppd.
3 MFD @ 6 V	5 for \$1.00 ppd.
10 MFD @ 6 V	5 for \$1.00 ppd.
1 MFD @ 25 V	5 for \$1.00 ppd.
80 MFD @ 2.5 V	5 for \$1.00 ppd.
1500 MFD @ 25 V	2 for \$1.00 ppd.
500 MFD @ 25 V	3 for \$1.00 ppd.

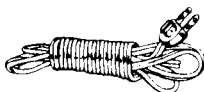

6 Foot Gray Line Cord. UL Approved. Very nice. 40¢ ea ppd.



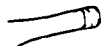Panelmount Fuseholder for standard 3AG fuses. Complete with all hardware. New. 3 for \$1.00 ppd.



Factory fresh TRW Dipped Mylar Capacitors. New with full leads. .022 @ 50 V, .047 @ 50 V, .1 @ 50 V. Your choice - may be mixed. 20 for \$1.00



88 Mhy Toroids-CT-unpotted 5 for \$1.50 ppd.

TI 1N914 Diodes 16 for \$1.00 ppd.

1N4007 Diodes .28 ppd.

Unmarked Germanium diodes, similar to 1N34.

25 for \$1.00; 100 for \$3.00

400 MW Zeners 3.3 V, 3.6 V, 3.9 V, 4.3 V

4 for \$1.00 ppd.

Mallory Computer grade Capacitors. Your choice. 1250 MFD @ 180 V, 1500 MFD @ 80 V

\$1.00 ea; 10 for \$7.50 ppd.

2N3055 Transistor \$1.50 ea or 3 for \$4.00 ppd.

SEND STAMP FOR BARGAIN LIST

Pa. Residents add 6% State sales tax

ALL ITEMS PPD. USA

M. WEINSCHENKER K3DPJ

BOX 353 • IRWIN, Pa. 15642

THE RADIO CONSTRUCTOR

Vol. 22 No. 11

JUNE 1969

THREE SHILLINGS

Top Band "Quartet" Transmitter



Special
IN THIS ISSUE

Semiconductor Sound-operated Switch
Pocket Continuity Leakage Tester

A New Magazine?

Not really. New in the U.S.A. perhaps, but very well known in Great Britain and now being offered to you here.

RADIO CONSTRUCTOR is almost exclusively construction material. Clearly written, concise articles give you full details on:

- Audio Construction Projects
- Receiver Construction Projects
- Transmitter Construction Projects
- Test Equipment Projects
- Radio Control Projects
- ... and much more

Try a subscription to this interesting magazine, we are sure that you will not be disappointed.

ONE YEAR SUBSCRIPTION — \$5.00

Write
RADIO CONSTRUCTOR
Greenville, N. H. 03048

Name

Address

City State

Zip

... THE BEST 2 METER CONVERTER



Model 407
\$42.95
ppd.

144-146 MHz in. 28-30 MHz out
or 146-148 MHz with a second crystal
available for \$5.95 each

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of thousands of satisfied users) that it's the best. The reason is simple — we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$42.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

VANGUARD LABS

Dept. R, 196-23 Jamaica Ave., Hollis, N.Y. 11423



Radio Amateurs
Reference Library
of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables . . . postpaid \$1.25

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. . . . postpaid \$1.25

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries . . . postpaid \$1.25

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 3/4" x 12" postpaid \$2.00

Complete reference library of maps — set of 4 as listed above postpaid \$3.50

See your favorite dealer or order direct.

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR
callbook INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

50% off on FET experimenter kits and the Siliconix FET handbook



The Handbook: The ink is barely dry on this one. It takes you from basic FET principles and manufacture through characterization and biasing to audio and RF amplifiers, VCRs, current limiters, switches, chopper and analog gates . . . just to mention a few. More than 30 practical circuits are shown. Additional references are included for those who want to go deeper into a given subject.

KIT #1

2N3368 Amplifier	1.40
2N4223 VHF Amplifier	1.50
E300 VHF Amplifier	1.40
U183 Amplifier	1.40
VCR7N VCR	2.25
CL2210 Current Limiter	3.25
and new FET Handbook	2.50
VALUE	\$13.70

LIMITED-TIME PRICE

Only \$6.50

KIT #2

2N3368 Amplifier	1.40
2N3437 Amplifier	1.90
E101 Amplifier	2.20
E300 VHF Amplifier	1.40
U202 Switch	2.95
VCR7N VCR	2.25
CL1020 Current Limiter	3.25
U234 Matched Dual FET	5.00
and new FET Handbook	2.50
VALUE	\$22.85

LIMITED-TIME PRICE

Only \$11.50

KIT #3

2N3370 Amplifier	2.15
2N5398 UHF Amplifier	4.50
E101 Amplifier	2.20
U184 HF Amplifier	2.75
U241 10 Ohm Switch	9.70
CL1020 Current Limiter	3.25
U234 Matched Dual Fet	5.00
LM201H Op. Amplifier	6.50
and new FET Handbook	2.50
VALUE	\$38.55

LIMITED-TIME PRICE

Only \$16.50

Kits may be purchased less handbook as noted on coupon. This is your half-price chance to really get to know FETs, so send in the coupon today!

Siliconix
incorporated

2201 Laurelwood Rd. • Santa Clara, Calif. 95054
(408) 246-8000 Ext. 201 • TWX: 910-338-0227

SILICONIX INCORPORATED

Dept. F — 2201 Laurelwood Rd. — Santa Clara, Calif. 95054

Please send items as checked below, for which payment is enclosed. (Sorry, no Purchase Orders or CODs.)

- | | |
|---|---|
| <input type="checkbox"/> Kit #1 \$ 6.50 | <input type="checkbox"/> Kit #1 Less Handbook \$ 5.00 |
| <input type="checkbox"/> Kit #2 \$11.50 | <input type="checkbox"/> Kit #2 Less Handbook \$10.00 |
| <input type="checkbox"/> Kit #3 \$16.50 | <input type="checkbox"/> Kit #3 Less Handbook \$15.00 |
| <input type="checkbox"/> Handbook only \$2.50 | |

Name _____

Address _____


City _____ State _____ Zip _____

(California residents add 5% sales tax)

QUARTER OF A CENTURY OF MANUFACTURING KNOW-HOW, 1946 TO 1971

CELEBRATING OUR 25th YEAR

Classic Line Multi-Band Beams

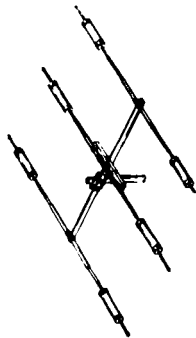


MODEL CL-33 10, 15, & 20 meters

Designed to provide the extra gain for working hard-to-reach DX, incorporates the exclusive Mosley patented "Balanced Capacitive Matching". Features include six Trap-Master traps with resonant frequency stability, improved boom for even wider element spacing. Stainless Steel hardware. Fits up to 2" mast. Use with most heavy duty rotors. The CL-33 is designed for 1000 watts AM/CW or 2000 watts P.E.P., SSB.



Multi-Band Beams

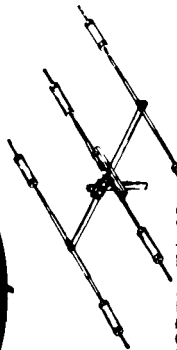

MODEL TA-33 10, 15, & 20 meters

The most widely used 3-element beam in the amateur universe. The TA-33 features the Mosley "Trap-Master" traps, known for rugged construction and resonant frequency stability under all weather conditions. Power rated: 2000 watts P.E.P., SSB.

MODEL TA-33Jr.

10, 15, & 20 meters


The TA-33Jr incorporates the same famous "Trap-Master" performance found in the TA-33 at a reduced price. Offering a power rating of 1000 watts P.E.P., SSB.

Anniversary Special

Free QSO Index

Keep track of over 200,000 contacts. Recall in seconds whether you have contacted a station before, and if so, the operators name. The deluxe Mosley QSO Index will never increase in size or weight and is light enough, only 28 ounces, to carry with you on those field day operations. This unique QSO Index will provide you with hours of pleasure and it is yours free with the purchase of any one of the Mosley Antennas shown here.


Free offer expires December 31, 1971.

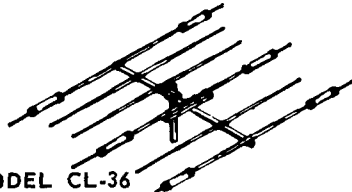

MODEL CL-36
10, 15, & 20 meters

The Classic 36, incorporating the Mosley superior feed system "Balanced Capacitive Matching". This wide-spaced, six-element beam employs 4 operating elements on 10 meters, 3 operating elements on 15 meters and 3 operating elements on 20 meters. Automatic bandswitching is accomplished through Mosley designed high impedance paralleled resonant "Trap-Circuits".

Single-Band Beams
20 Meters

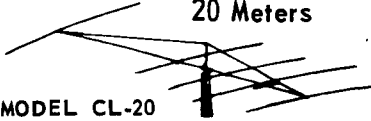

MODEL CL-20

The improved electrical balance, "Balanced Capacitive Matching," combines with optimum spacing to provide maximum gain, increased bandwidth for greater efficiency in performance.

MODEL CL-203

Designed for full power, the new Classic 203 will out-perform many four to six element arrays. The Classic Feed System, combined with optimum spacing to provide maximum gain, increased bandwidth and rugged construction, offers the most in 3-element, 20 meter beam performance.



New Six-Band Mobile Antenna System

A unique mobile antenna system offering the greatest number of money-saving options ever available in the amateur radio market. Your choice of 6, 10, 15, 20, 40, and 75/80 meters. Select from five new interchangeable coils, all of which are especially designed for the thrifty, economy-minded Ham.

Each "Rode-Master" coil is precision wound on phenolic form, housed and sealed in a durable, water-proof phenolic case and power rated for 200 watts AM; 400 watts P.E.P. SSB. VSWR 1.5/1 or better at resonance on each band.


The upper whip section of the "Rode-Master" Support-Mast is a Six-meter antenna, adjustable for the entire 6 meter band and may be purchased separately.

The lower section of the mast has a host of features that include provisions for bumper or deck mounting. A break-over (hinge) to lower and swivel, align and secure antenna to gutter rail.

"RODE-MASTER"	Models
6 meter antenna	MD-6
10 meter coil	MD-10
15 meter coil	MD-15
20 meter coil	MD-20
40 meter coil	MD-40
75/80 meter coil	MD-78
Matching Network	MD-48

Signal-Master

40 METERS BEAM

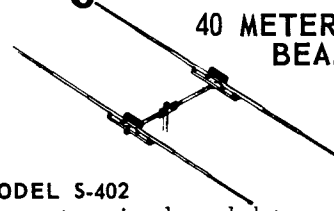

MODEL S-402

For a top signal needed to push through 40 meter QRM, the Mosley Signal Master S-402 will do the trick! This 100% rust-proof 2-element beauty constructed of rugged heavy-wall aluminum is designed and engineered to provide the performance you need for both DX hunting and relaxing in a QRM free rag-chewing session. Beam is fed through coupling, resulting in an excellent match over the entire bandwidth.


TRAP MASTER Multi-Band Verticals

MODEL RV-3C

Three band vertical for 10, 15, and 20 meters. RV-3C features automatic bandswitching and low angle radiation. Complete with guy line, "Cyclac" base, coax fitting and all necessary hardware.

MODEL RV-4C

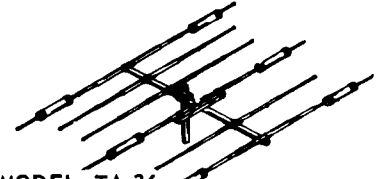Mosley RV-4C, vertical antenna is ideal for installation where space is an important factor. Designed for 10, 15, 20, and 40 meters. With automatic bandswitching. Entirely self-supporting.



MODEL TA-36
10, 15, & 20 meters

The voice of authority! This wide-spaced 6-element configuration employs 4 operating elements on 10 meters, 3 operating elements on 15 meters, and 3 operating elements on 20 meters. Automatic bandswitching is accomplished through the Mosley exclusively designed high impedance paralleled resonant "Trap-Circuits".

For more information see your nearest Mosley Dealer or specify area of interest and write factory direct.
Dept. 205

Mosley Electronics, Inc.
4610 N. LINDBERGH BLVD.
BRIDGETON, MO. 63044

Mosley, manufacturer of quality TV Antenna Accessories for nearly a Quarter of a Century.
Write Dept. 198TV for free Booklet!
'How to Improve Your TV Picture'

HOLD THE PRESS — NEW TTL IC's

REVISION



**NIXIE
READ OUT
STAGE**

~~\$18.25~~

"NEW"

FROM



By converting to TTL logic price reductions enable R & R to sell at a low, low \$12.49 per stage. Send for information.

KIT INCLUDES:

- 1—PC BOARD and CONNECTOR
- 1—NL 940S READ OUT TUBE and SOCKET

USES:

- FREQUENCY COUNTER for doublets and quads
- DIGITAL VOLTMETER
- TIME INTERVALMETER
- DIGITAL CLOCK (has facilities for dividing by six for clock)

R & R ELECTRONICS, 311 E. SOUTH ST., INDIANAPOLIS, IND. 46225



**ANTENNA
MATCHING
TRANSFORMERS**

- 50 ohm co-ax to 50 ohm balanced load (for doublets & inverted vee's) **\$14.95**
- 50 ohm co-ax to 75 ohm balanced load (for doublets and quads) **\$14.95**
- 50 ohm co-ax to 75, 120, and 140 ohm load (for single feed three band quad) **\$18.95**
- Other impedance ratios available on request

All units are rated at full legal power and shipped post paid. Calif. residents add 5 1/2 % sales tax.

H & H ENGINEERING

P. O. Box 68, La Mirada, Calif. 90638

SURPLUS CRYSTAL FILTERS

- 6 XTAL-11.5 MHZ-35 KHZ 6 DB BW- MOD. MEL-3 **\$14**
- 60 DB BW 100 KHZ MAX-50 OHM TERMINATIONS
- MATCHING XTAL DISCRIMINATOR- MOD. MAL-1 **\$10**
- ±10 TO ±15 KHZ DEVIATION-DOPE SHEET INCL.
- 10.7 MHZ-13 KHZ 6 DB BW- 6 XTAL-MOD. FB-5M **\$19**
- 60 DB BW 25 KHZ MAX-1000 OHMS IN & OUT
- 10.7 MHZ-30 KHZ 6 DB BW- 6 XTAL-MOD. IO-MA **\$14**
- 60 DB BW 75 KHZ MAX-2000 OHMS IN & OUT
- 10.7 MHZ-34 KHZ 6 DB BW- 10 XTAL-MOD. GB-79 **\$28**
- 60 DB BW 55 KHZ MAX-1000 OHMS IN & OUT **\$28**

SEND DIME FOR LIST OF OVER 50 TYPES SURPLUS XTAL FILTERS & NEW & SURPLUS TOROIDAL CORES

CARBONYL "E" TOROID CORES
 2" DIA T-200-2 EACH \$2.75 OR 3 FOR \$7.00
 .69 DIA. T-68-2 EACH 50¢ OR 7 FOR \$2.75
 MINIMUM POSTPAID ORDER 2.75 TOTAL

J. T. McCULLOUGH, W08HG

ESE E. S. Electronic Labs
 301 AUGUSTUS, EXCELSIOR SPRINGS, MO. 64024

Cir-kit

A revolutionary new material for the construction of experimental and prototype "printed" circuit boards.

Cir-Kit is high purity .002" copper protected by lacquer and coated with an exclusive heat resistant pressure sensitive self adhesive. Just remove backing paper and place in selected position. Press down firmly. If modifications are necessary just rip it up and start over.

Cir-Kit can be used for modifying existing boards or building up new ones. The perfect answer for small quantity applications or one of a kind amateur projects.

- 100 feet 1/16" or 1/8" wide **\$9.95**
- 5 feet 1/16" or 1/8" wide **\$6.00**

Sheets 6" x 12" — **\$3.00 each**
 or 5 for **\$9.95**

**Order Now
Cir-kit**

**BOX 592
AMHERST, N. H. 03031**

Pro CW from amateur fingers.

Ten-Tec's KR 40 squeeze keyer makes the perfect signal from the imperfect hand. Built-in memories insert characters in correct place and spacing with only a momentary closure of either paddle. Spacing and speed are adjustable to match your sending speed, from 6 to 60 words per minute. Built-in monitor provides side tone for headphones, speaker or off-the-air practice. Output is handled by reed relay. Circuitry is all solid state. The KR 40 is a good looking, rugged keyer with a beautiful feel. Easy to learn. Easier to use.

OUR BEST FOR THE
SERIOUS AMATEUR \$89.95



Write for complete information on the Ten-Tec family of five keyers. Priced from \$34.95. Send coupon to:



TEN-TEC INC. Dept. V
SEVIERVILLE, TENNESSEE 37862

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

B A R R Y

COLLINS MECHANICAL FILTER, Type F250A-67. Center frequency 250kc, Bandwidth —6db is 6.7kc ±5%, Bandwidth @60db is 14kc, Reasoning capacity 110 mmfd., Sig. input voltage from 0 to 5v RMS, DC voltage 300 volt maximum, Signal source impedance 50kc, Load impedance 50K Ohms. \$9.75

JENNINGS UCS-300 VACUUM VARIABLE CAPACITOR. Capacity range: tunes from a min. of 10 pf. to a max. of 300 pf. Units are unused, "mint" condition, Lab-tested and certified O.K. in Aug. 1970. With out turning head at \$50.00 With turning head at \$66.75

AIR DUX KILOWATT PI-NET COIL No. 195-2. Provides an economical K.W. Pi-Net Assembly when used with proper loading capacitor and R.F. Switch 80, 40, 20, 15 and 10 meter taps are clearly marked on coil. No. 195-2 \$22.50 Same as above but 500 Watt capacity. Order No. 195-1 \$15.90 net.

JOHNSON SINGLE SECTION MINIATURE VARIABLE CAPACITOR, TYPE "L". Capacity: 3.5 to 27 Mmfd. 1/4" shaft. Ceramic Insulation. Reg. net price: \$1.70. 75¢ Each

JOHNSON MINIATURE BUTTERFLY CAPACITOR. TYPE "L". Capacity: 4.3 to 25 Mmfd. per section. 1/4" shaft. Ceramic Insulation. Reg. net price: \$2.25. 95¢ Each

HICKOK 2.5 MICROAMMETER. Hickok Model 46HR Tautband 3 1/2" round hermetically-sealed meter. Extreme sensitivity. 2.5 Microamps either side of center. (Orig. cartons.) \$9.95

KW. PLATE TRANSFORMER. Pri: 210, 220 or 230 VA C@ 50 or 60 Hz. (Single Phase). Sec: 3500 VAC R.M.S. (approx.) @ 500 to 600 Ma. (No C.T.). Modern 2 KVA. Hipersil Core. Approx. 8" x 7" H. Ship'g Wt.: 35 lbs. approx. (Open Frame type.) \$34.95

DYNAMIC MICROPHONE DESK/HAND SET. 28" Shielded Mike Cable terminates in an angle type PL55 Phone Plug. Microphone quickly removes from base. Attractive Beige Color. (Reg. net \$12.95). Mike and Base Only \$4.95

R.F. TRANSMITTING CHOKES. 800 Ma. 3 to 30 Mhs. 90 Microhenries. 2500 V.D.C. Size: 4 3/4" H x 3/4" Diameter. Tapped on bottom with threaded 10/32" hole. \$4.95

R.F. TRANSMITTING CHOKE. 2 Amps. 3 to 30 Mhs. 90 Microhenries. DC Current: 2 Amperes @ 4 KV. plus. Size: 5 1/2" H x 7/8" Diameter. Tapped on bottom with threaded 10/32" hole. \$8.95

GROUNDING GRID FILAMENT CHOKES
Bilifar types:
30 Amps \$8.90
60 Amps \$11.90

EIMAC AIR-SYSTEM SOCKET. For 4-125A, 4-250A and 4-400A, and similar tubes. Supplied with screws and chimney hardware. Mfd. by Eimac. Type No. 4-400A/4000 (SK400). (Reg. price \$28.50). Special: \$14.95, for Socket SK-406 Chimney (Reg. Stock) at \$6.50 Each

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Fair dealings since 1938. Write or call now! Barry, W2LNI. We buy factory termination and from individuals.

We ship all over the World. DX Hams only. See Barry for the new Alpha 70. (See front inside cover of this magazine.)

Send 35¢ for 104 page catalog #20.

BARRY ELECTRONICS
DEPT. H-1
512 BROADWAY, NEW YORK, N. Y. 10012

WANTED! DRAKE T4X
REWARD: \$320.00
 trade allowance on new T4XB



T-4XB TRANSMITTER

Use VFO of either R-4B or T-4XB for transceiving or separately.

L.A. ELECTRONIX SALES


Home of L.A. Amateur Radio

23044 CRENSHAW BOULEVARD
 TORRANCE, CALIFORNIA 90505

READY FOR 432 MHz?

High performance, high quality equipment for 432 MHz operation. All solid-state. Silverplated, brass enclosures. Stripline 432 MHz circuits. Silverplated, glass-epoxy printed circuit boards.

432 MHz DUAL GATE MOSFET CONVERTER

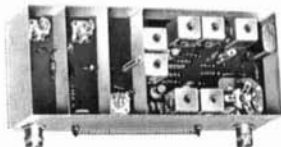

Noise figure: 3.2, cross mod. 80 mV min., gain 5-20 db, T-match output attenuator. I.F. 144-146 MHz. Model DGTC 1702.\$69.00
 I.F. 28-30 MHz. Model DGTC 1710.\$71.50

144/432 MHz TRANSVERTER



Transmitter input: 50 mW to 1.2 Watts. Efficiency: 60%. Receiver noise figure: 8. No antenna switching required. Simply connects between two-meter AM/FM/CW transceiver and 432 MHz antenna. Requires 12 Volts in "Receive" only. Model TTV 1270.\$47.50

144/432 MHz VARACTOR TRIPLER



AM, FM and CW. Input up to 30 Watts. Efficiency: 50%. Input-frequency suppression: 50 dB min. Harmonics suppression: 80 dB min. Model LVV 270 ..\$75.00

ALSO:

DUAL GATE MOSFET CONVERTER FOR TWO METERS



Noise figure: 2. Excellent cross modulation and image rejection (116 MHz xtal oscillator.) IF 28-30 MHz. All inductors shielded. Model DGTC 22.\$35.00

si

SPECTRUM
 INTERNATIONAL
 BOX 87, TOPSFIELD
 MASSACHUSETTS 01983

flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

SWAFFEST National Guard Armory, St. George, S.C., Sunday, February 7, 10:00 a.m. - 4:00 p.m. Talk-in 3950 SSB - 146.94 FM. "Hoss trading", Displays, Prizes. Bring all your gear for sale. Please let us know in advance how many to seat, number of tables, etc. Write Chamber of Commerce, Box 348, St. George, S.C. 29477 or call W4DTW, 803-563-4377.

W6AG SELLING OUT. Lifetime collection goodies. Example: Immaculate 7544, \$300. SASE for fantastic steal list. 213-764-4401.

SAVE. On all makes of new and used equipment. Write or call Bob Grimes, 89 Aspen Road, Swampscott, Massachusetts, 617-598-2530 for the gear u want at the prices u want to pay.

GREENE — center of dipole insulator with or without balun . . . also the GREENE DRAGON FLY antenna . . . send for free flier . . . GREENE, Box 423, Wakefield, R. I. 02880.

WICPI.
WORLD WIDE SSTV CONTEST. 1st Period 07.00-14.00 GMT Feb. 13, 1971. 2nd Period 16.00-23.00 GMT Feb. 13, 1971. All authorized frequencies. Suggest: 3.740 - 7.050 - 14.230 - 21.100 - 28.100 kHz. Messages: Exchange of picture. The message number may be given by voice. Scoring: A two-way contact with a station receives one point. (Total points will be the number of individual stations contacted.) No extra points for contacting the same station on different bands. A multiplier of 5 points is given for each continent worked. Logs must contain: date, time (GMT), band, call sign, message number sent and received, points. SWL: To encourage those who have no SSTV transmitting gear, a special prize will be awarded for the best collection of photographs of received SSTV pictures. All logs must be received by 28th February 1971. They should be sent to: Prof. Franco Fanti, IILCF, Via Dallolio, 19, 40139 Bologna, Italy.

SELL: Hallicrafter SR150 AC PS, \$275.00; HT32 Transmitter, \$200.00; National NC 109 Receiver, \$65.00. John Fearon, 3384 Peachtree Rd., N. E. Suite 705, Atlanta GA. W4WKP.

"DON AND BOB" new guaranteed buys. Monarch KW relative power SWR dualmeter bridge (reg. 24.00) 14.95; RCA 6LQ6 3.50; AmpereX 8802/3600Z 32.00; 6146B 4.45; Ham-M 99.00; TR-44 59.00; Hygain TH6DX 139.00; TriEx W51 329.00 prepaid; Regency HR2 6 channel 20 watt 2M. FM 195.00; Jennings vacuum variable capacitor 300PF/7.5KV 20.00; (no drive) Motorola HE170 2.5A/1000PIV diode 39¢; write quote SPR4, R4B. Prices FOB Houston. GECC Finance. Madison Electronics, 1508 McKinney, Houston, Texas 77002. (713) 224-2668.

SURPLUS MILITARY RADIOS, Electronics, Radar Parts, tons of material for the ham, free catalogue available. Sabre Industries, 1370 Sargent Ave., Winnipeg 21, Manitoba, Canada.

THE 20th ANNIVERSARY DAYTON HAMVENTION will be held on April 24, 1971 at Wampler's Dayton Harra Arena. Technical sessions, exhibits, hidden transmitter hunt and an interesting program for the XYL. For information write Dayton Hamvention, Dept. H, Box 44, Dayton, Ohio 45401.

DIGITONE TONE CONTROL DEVICES — decoders, encoders, logic. Compact, solid-state modules. Application Notes/Catalog. Write Digitone, Box 73-HR, Bellbrook, Ohio 45305.

JANUARY CLEARANCE SALE: "HOSS TRADER" ED MOORY is REDUCING INVENTORY: On a first come first serve basis at ridiculous prices: USED RECONDITIONED EQUIPMENT. 78A-4, \$276.00; 78B-3, \$349.00; KWM-2, \$649.00; Drake 2A, \$129.00; 2-B, \$149.00; TR-3, \$329.00; 8X-11A, \$99.00; HQ-110C, \$95.00; Marauder HX-10, \$125.00; HX-20, \$75.00; National NC-183D, \$99.00; NC-303, \$149.00; NCX-3, \$149.00; Swan 380, \$259.00; Ham-M, \$79.00; Slightly Used Drake SPR-4, \$325.00; TR-4, \$395.00; Swan 800CX, \$425.00; 702B Cygnat, \$375.00; NEW WATERS 336 Coaxial Switch, \$8.75; New W2AU Quad, \$80.00; New Moseley Classic 33 and Demo Ham-M Rotor, \$199.00; Write for quotes on other new and used equipment; Moory Electronics Co., Box 506, Dawitt, Ark. 72042. Phone (501) 946-2820.

QSL5. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

TORIODS 44 and 88 myh. Unpotted, 5 for \$1.50 ppd. W. Wenschchen, Box 353, Irwin, Pa. 15642.

WORLD QSL BUREAU — see ad page 86.

7289 (3CX100A5) Ceramic replacement for 2C39 tube, \$3 ea; 6/\$15. Also 432MHz and 1296 MHz cavities. Trade for 2 mtr. FM gear. W48OD, Box 73, Folly Beach, S. C. 29439.

CLEARING OUT HAMSHACK - Ten years of chassis collecting Military Surplus, FM, AM electronic counters. Send stamped self-addressed envelope for list. A. C. McIntosh, P. O. Box 572, Mundelein, Illinois 60060.

DX STATIONS: W2KF can provide QSL cards and serve as your QSL Manager at no monetary cost to you. Write W2KF for details, 309 Cherry Hill Blvd., Cherry Hill, N. J. USA.

ELECTRONICS YOUR BAG? Looking for an electronics course . . . that you can pay for by the subject AND take ONLY the subjects you NEED? . . . that you can change into ANY PHASE of electronics after completion of basics WITH NO PENALTY? For full information, write: EDCO ENTERPRISES INC., P. O. Box 432, Sparks, Nev. 89431.

NOVICE CRYSTALS: 40-15M \$1.38, 80M \$1.83. Free flier. Nat Stinnette Electronics, Umatilla, Florida 32784.

CIRCUIT BOARDS, Bishop Prekuts, Photo Resist, Litho negatives made. Send for free list: WA800B, Box 563, Waynesville, Ohio 45068.

NOISE GENERATOR: Kay Electric Model 3000 \$175. Esterline Angus whart recorder; 0 - 5 ma \$55., 0 - 1 ma \$65. CB6LLT, 162 S. La Luna, Ojai, CA 93023. 805-646-6387.

ROCHESTER, N. Y. will again be headquarters for the huge W.N.Y. Hamfest, V.H.F. Conference and Flea Market May 15, 1971.

TELL YOUR FRIENDS about Ham Radio Magazine.

FOR THE MAN WHO TAKES CW SERIOUSLY.

model KB-1 • \$265 net



FOR YOU, ONLY THE BEST WILL DO. YOUR TRAFFIC, YOUR QSO'S MUST BE PERFECT. THIS IS THE KEYS WHICH WILL DO IT FOR YOU, PERFECT LETTERS AND SPACES, ALL AUTOMATICALLY. 12-72 WPM. KEYS POSITIVE OR NEGATIVE LOADS. BUILT-IN MONITOR OSC/AMP FOR SPEAKER. WEIGHT CONTROL TO SUIT YOUR PREFERENCE. ONE-YEAR PICKERING WARRANTY.

READ THE QST WRITEUP ON THE KB-1 IN THE AUGUST, 1970 ISSUE. THEN SEND FOR OUR ILLUSTRATED BROCHURE ON THE KB-1.

TO ORDER, SEE YOUR AMATEUR EQUIPMENT DEALER, OR ORDER DIRECT FROM FACTORY. YOU MAY USE YOUR MASTERCHARGE OR BANKAMERICARD. SIMPLY GIVE US YOUR ACCOUNT NUMBER.

YOUR CW SENDING DESERVES THE BEST
ORDER YOUR KB-1 NOW!

PICKERING RADIO CO.
Post Office Box 29B
Portsmouth, R.I. 02871



HAL DEVICES

FOREIGN HAMS

DO YOU NEED AMERICAN
CONSTRUCTION COMPONENTS?

Send us a list of your needs and we will give you a quotation on any standard American parts which you may require.

No longer need you avoid construction projects in Ham Radio or any other U. S. amateur publication because of hard to find parts. We'll find them and send them to you.

Send 4 IRC's for catalog.

HAL DEVICES

BOX 365 HF
URBANA, ILLINOIS 61801 U.S.A.

IT'S
1971
ARE YOU ALL SET?

•
**1 year
ham radio
\$6.00**

•
3 years — \$12.00

•
HAM RADIO
GREENVILLE, N. H. 03048

TOLEDO MOBILE RADIO Association's 16th Annual Hamfest and Auction will be held February 21, 1971, Lucas County Recreation Center, Maumee, Ohio. \$1.00 Registration, open table sales. Map and info write: TMRA W8HHF, Box 273, Toledo, Ohio 43601.

SELL: 75A4 EXCELLENT CONDITION, vernier knob, 800 Hz, 3kHz filters, noise blanker, speaker, \$325.00. KOEXD, Carl Thorsell, 1195 E. 77th, Kansas City, Mo. 64131.

FOR SALE: KG 636 10 MC 'scope with triggered sweep. Dual trace plug-in pre amp, extra CR tube, excellent condition, \$145.00. BC 221-T original calibration book, AC supply \$30.00. B & W grid dipper, all coils \$17.00. Many other bargains. SASE for list. Bill Blake W5SCM, St-Rt., Box 1350, Columbus, Miss. 39701.

TELETYPE #28 LRXB4 reperforator-transmitter "as is" \$100; checked out \$175. Includes two 3-speed gearshifts. Alltronics-Howard Co., Box 19, Boston, Mass. 02101. 617-742-0048.

READ RADIO CONSTRUCTOR for many interesting home-brew projects. Radio Constructor, Greenville, N. H. 03048.

FOR SALE: Squire-Sanders SS1R, SS1RS, SS1S, (all new), \$550. 75S3B #85399, \$550. KWM2-A #18922, Noise Blanker, 516F2, \$950. 75S1, 32S1, 516F2, \$600. MP1, or 516E1, \$125. 351D2, \$100. 312B4: new, \$175; used, \$135. 75S3, 32S3, 516F2, \$950. 30L1, #25752, \$400. SR160, P150DC, \$200. P500AC, \$65. SR150, P150AC, \$295. 312B5, \$275. SW500C, 117XC, 14C, mobile mount, \$475. Galaxy 300, PSA300 p. s. /console, \$165. Waters Nuverter, \$100. Viking Thunderbolt, \$225. C. E. 100V, \$235. Waters Hybrid Coupler, #3002, \$40. Motorola 80D, complete, \$75. Capacitors: 4 mfd/10KV, \$15. Powerstat Model 136, 0-140V/20 amps, \$25. Simpson Model 260 VOM (factory-reconditioned), \$45. Telex headset, (new), \$5. Lafayette HA750, HB502, mike, squalo, \$100. TA33 (new), \$120. Filter F455Y60 (for 75S1/S2/S3), \$20. TR44 (new), \$60. Lambda VR supplies, write for details, \$25. Messenger III, AC supply, \$100. Transformers: 115/2880VCT@500 ma, \$15; 115/5VCT@30 amp, \$8. RTTY Converter Electro-Com FSC-250 with TK-100 and filters, cables for use with KWM2/S-Line, all for \$250. Polarad UHF rcvr to 10GHz (plug-in supplied for 1-2 GHz), \$50. Model "B" Powerstats, 2 1/2 amp, \$6. 813's, \$5. Bell & Howell Model 200EE 16 MM movie camera, with case, \$50. Measurements Corp Model 80 RF Signal Generator, \$100. Ferris Model 20-A Micro-volter, \$50. Transformers: UTC S44, \$12; S49, \$20; S57, \$4; S63, \$7; Stancor P8026, \$20; 1300/3 amp, \$35. H-P 212-A Pulse Generator, \$35. Clegg 66'er, \$135. Drake DC-4, new, \$95. James W. Craig, W1FBG, 29 Sherburne Avenue, Portsmouth, N. H. 03801. (603) 436-9062

HRO-60 RECEIVER with ABCD coils, \$100.00. Johnson Challenger Transmitter \$37.50. Hammarlund HB-1K Electronic Keyer \$12.50. FOB certified check or M.O. Don Baker, W8CVA, 4606 Wickford Dr. E., Sylvania, Ohio 43560.

ASK FOR FREE LIST of used Ham gear or for prompt personal attention on any new gear. Mail your order direct to VanSickle Radio, W9KJF, Indianapolis, Indiana 46205. 40 years experience.

CODE PRACTICE TAPES - Novice - General - Extra Class - Specify - \$8.00 each. W9CJJ, 1105 Schaumburg Road, Schaumburg, Illinois.

MECHANICAL FILTERS: 455 Khz. 2.1 Khz \$18.95. 300 Hz \$22.95. J. A. Fredericks, 314 South 13th Avenue, Yakima, Washington 98902.

IRISH HOLIDAY exchanged for VHF, mobile, side-band gear. Stay in friendly guesthouse. Scenery, seascapes, sports local. Des Walsh EI5CD, Carrick-on-Suir, Co. Tipperary, Ireland.

HEATH SSB SB401-E, SB300, SSB/CW, VOX/PTT, \$440. KW lineal, H.B.-similar to SB200, 4CX250B's, solid-state supply \$150. \$550 for all. Ray Grimes, WB9CTT, 2146 Maple, Evanston, Illinois 60201.

NCX3, NCXA AC SUPPLY, \$150, W9OEQ, R. R. 2, Mokena, Illinois 60448.

Digital Frequency Meter




- Monitors your "transmitted" signal
- Measures kHz and MHz
- Operates with any exciter-transmitter (1 to 600 watts — up to 30 MHz)
- Large-bright "Nixie" display
- Now - 100 Hz (.1 kHz) Readout through 35 MHz

FM-6 Kit . . . \$139.50

Micro-Z Co.

Box 2426 Rolling Hills, Calif. 90274

radio amateur
callbook

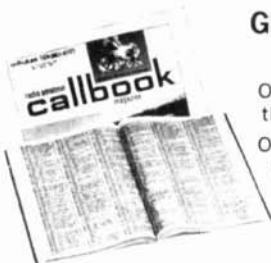

GET YOUR NEW ISSUES NOW!

Over 285,000 QTHs in the U.S. edition **\$8.50**

Over 165,000 QTHs in the DX edition **\$6.50**

NEW EDITION EVERY:
MARCH 1 — SEPT. 1
JUNE 1 — DEC. 1

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes!
- Prefixes by Countries!
- Zips on all QTH's!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

WRITE FOR FREE BROCHURE!



RADIO AMATEUR **callbook** INC

Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

TEST EQUIPMENT SPECIALS!!

BALLENTINE Model 314 AC VTVM, 1000V to 1000V FS. These are less probe which consists of a 10 Meg. Res. in parallel with 0.6 pf. Add \$7.50 and we will make probe. Condition very good & calibration checked. \$50.
Beckman Model 5571/1 or 5572 Eput Counters. 1 MC \$175
Model 7570 Pwr Supply & 7571 Conv. for above 110 MC \$75
Sell separately or by the set & save. PKG. \$225
Beckman Model 5571 Frequency Meter. \$50
Beckman Model 5580 Pwr Supply with 5581/4 Reference Generator. \$100
Hewlett Packard Mdl 460AR Wideband Amp. \$50
Spencer Kennedy Model 202D Chain Amp. \$40

RF TOROIDS

PREWOUND RF & OSC SET FOR ARRL RCVR. The Pair \$3.00 PPD.
Unwound Cores as above only. \$50 ea PPD.

TOROID ASSORTMENT FOR THE SERIOUS BUILDER — 20 CORES — Only \$3.50 PPD.

COLOR CODE

1-C Core	50KHZ-5MHZ	Blue
5-E Core	500KHZ-30MHZ	Red
1-TH Core	2MHZ-40MHZ	White
2-Q1 Core	500KHZ-30MHZ	Red & Blue
1-Q2 Core	10MHZ-90MHZ	Black
9-SF Core	10MHZ-90MHZ	Yellow
1-Misc. Core		

We Bought Thousands to Bring You This Buy! I

CIRCUIT BOARD ASSEMBLY



Unusual Find!!! Digital Assembly. 3 Boards mounted on a frame with panel. Fixed center board. Outside boards are hinged and swing out. Use frame for breadboard assemblies. Panel 2 1/2 x 8 1/2. Depth 1 1/2". All parts easy to remove. 300 1N658, 77-114 Sw. Xsistors, 1N754 Zeners, Unijunctions, Tan-talums, & much more.

Board #1 - As above \$4.00
Board #2 - As above + 1 Clare Mercury wetted relay module, #HGSM1001 \$5.50
Board #3 - As above + 3 Clare Mercury wetted relay modules, #HGSM1001 \$6.50
SHIPPING WEIGHT 5 LBS.

Dual Four-Digit DOWN COUNTERS



Front panel adjusts to any number up to 9998. Counts down to zero. 28 volts DC coils. 2-28 volts DC or AC Panel Lamps.

Like New \$4.50 PPD.

HAYDON TIMER MOTORS \$0.75 PPD.
1-RPH 115 VAC % # Shaft

TRANSFORMER SPECIALS

1. Ptl. 115VAC Sec. 1) 20-0-20VAC @ 10 A. Sec. 2) 14-0-14VAC @ 5 A.	\$6.50	4. Ptl. 115VAC Sec. 1) 6.3VAC @ 6A. Sec. 2) 18VAC @ 1/2 A. Sec. 3) 450VAC @ 50ma.	\$4.50
2. Ptl. 115VAC Sec. 1) 17-0-17VAC @ 2A. Sec. 2) 70-0-70VAC @ 50 ma. Sec. 3) 30-0-30VAC @ 25 ma.	\$3.50	5. Ptl. 115-230VAC Sec. 1) 150VAC @ 250 ma. Sec. 2) 115VAC @ 1.5A. Sec. 3) 23VAC @ 0.7A.	\$8.00

ALLOW 20 LBS. SHIPPING ON ALL TRANSFORMERS AND WE WILL REFUND ANY DIFFERENCE. WE SHIP UPS.

COPPER CLAD LAMINATES

G10 EPOXY GLASS
1 oz. Copper 1 Side

Pkg. Quant.	3/64"	1/16"	3/32"	1/8"
1 9x12"	\$1.50	\$2.50	\$3.50	\$5.00
2 6x9"	"	"	"	"
4 4 1/2 x 6"	"	"	"	"
6 3x4 1/2"	"	"	"	"

This item postage prepaid.

Every order unconditionally guaranteed.

TRI O

2614 Lake Shore Dr. *Electronics* LaCrosse, Wis. 54601

AT LAST a SPEECH COMPRESSOR that REALLY WORKS

- LOW DISTORTION CIRCUIT
- 5-10 DB IMPROVEMENT IN TALK POWER
- FULLY WIRED & TESTED NOT A KIT
- SEVERAL MODELS TO CHOOSE FROM
- WORKS WITH PHONE PATCH
- Quality construction includes Silicon transistors, FETs Glass circuit boards
- FULL WARRANTY—ONE YEAR
- Performance second to none
- INTRODUCTORY LOW PRICES — \$22.50 to \$34.95 (Illinois residents add 5% sales tax)



Write for specifications and information sheets (free)

RP Electronics

Demonstration Tape cassette available (\$2.00 deposit)

BOX 1201H
CHAMPAIGN, ILL.
61820

WORLD QSL BUREAU

PLAN 1. WE FORWARD YOUR QSLs (PLEASE ARRANGE ALPHABETICALLY) TO ANY PLACE IN WORLD, INCLUDING ALL FOREIGN COUNTRIES, AND TO OR WITHIN USA, CANADA, AND MEXICO, FOR 4¢ EACH.

PLAN 2. YOU USE OUR SPECIAL LOG FORM AND SEND US A COPY. WE SUPPLY QSL — MAKE OUT QSL — DELIVER QSL, ALL FOR 8¢ EACH.

5200 Panama Ave., Richmond, CA USA 94804



ELECTRONIC FIST... THE PROFESSIONAL KEYSER

Every feature you need for easy, accurate CW

- IAMBIC FOR SQUEEZE KEY'S
- VARIABLE WEIGHTING FOR DX'S
- MESSAGE GENERATOR FOR CONTEST'S
- COLORS TO MATCH YOUR RIG

KIT OR WIRED. PRICES START AT \$69.95

WRITE FOR SPECIFICATIONS

Box 4090, Mountain View, California — 94040

GURTIS ELECTRO DEVICES

THE AMATEUR RADIO

QSO WITH W2CFP

HE HEARD OVER

WHCU

IN ITHACA, NEW YORK EVERY SATURDAY

For further information, contact Dave Flinn, W2CFP, 10 Graham Rd. W., Ithaca, N. Y. 14850, (607) 257-2424. Watch for Dave and his tape recorder at Hamfests and Conventions throughout the country.

5-RANGE DC AMPERE 26.95 Meter



Ranges: 1-2.5-5-10-25A. Extra-wide meter with mirrored scale. Includes test leads. Bakelite case: 7 1/4 x 4 1/4 x 2 1/2". Schools, shops, labs. SM321

ALCO Order: Box 1348H SHIPPED POSTPAID
Lawrence, Ma. 01842 Other Functions Too!

WANTED — BACK ISSUES HAM RADIO March 1970. Can swap with any other issue or how much. Missed any issues? Maybe can help. Eskil Persson, SM5CJP, Frotunagrand 1, 19400 Upplands Vasby, Sweden.

DERRICK ELECTRONICS will not be undersold on new Swan, Drake, Galaxy, Hy-Gain or Mosley equipment. Check around, then write, 108 East El Paso, Broken Arrow, Oklahoma 74012.

THE WHEATON COMMUNITY RADIO AMATEURS will hold their ninth annual Mid-Winter Swap and Shop on Sunday, February 21, 1971 at the DuPage County Fair Grounds, Wheaton, Illinois. Hours - 8:00 A.M. to 5:00 P.M. \$1.00 Advance/\$1.50 donation at the door. Send SASE for advanced tickets P. O. Box QSL, Wheaton, Illinois. Refreshments and unlimited parking. Bring your own tables. Free coffee and doughnuts 9:00 to 9:30 A.M. Hams, CBers, electronic hobbyists, friends and commercial exhibitors are cordially invited. Contact John Stockberger, W9THI, P. O. Box QSL, Wheaton, Illinois 60187 for information.

DON'T BUY QSL CARDS from anyone until you see my free samples. Fast service. Economical prices. Little Print Shop, Box 9848, Austin, Texas 78757.

WANTED: Following back issues of Ham Radio: April, November, December 1968. July 1969. March, April, May 1970. Jerry Ellinger, 1829 Edenside, Apt. 9, Louisville, Ky. 40204.

MANUALS for R-390/URR, R-390A/URR, USM-24C, URM-25D, BC-348J, BC-639A, \$6.50 each. S. Con-salvo, 4905 Roanne Drive, Washington, DC 20021.

DRAKE TR3, AC3, set spare tubes \$350. MM2 scope plus RM50 and RM455 receiver adapters \$100. Heath HA-10 1 KW linear \$150. Norman Webster, 19545 Ingomar, Reseda, Calif. 91335.

SELL: COLLINS 51J3/R388 excellent \$400.00; Hammarlund SP600JX/R274 excellent \$250.00; Galaxy 5 Mark 5 Transceiver, remote VFO, accessory console W/clock AC power supply, complete \$350.00; CV89 audio teletype convertor \$125.00; CV57 IF convertor \$100.00. WA0KLC, 315 East 20th, Grand Island, Nebraska 68801.

B.A.R.T.G. SPRING RTTY CONTEST, 0200 GMT Saturday, March 13th until 0200 GMT Monday March 15th 1971. Not more than 36 hours of operation is permitted. Times spent in listening periods count as operating time. Off-periods may not be less than two hours. Times on and off the air must be summarized on the Log and Score sheets. The Contest is also open to SWL RTTYers. 3.5, 7, 14, 21 and 28 Mhz. Amateur Bands. Stations may not be contacted more than once on any one Band, but additional contacts may be made with the same Station if a different Band is used. ARRL Countries List, except VO to be considered as separate Country. Messages exchanged will consist of: Time GMT, Message Number and RST. Two-way RTTY contacts with one's own Country will earn TWO points. Contacts outside one's own Country will earn TEN points. A bonus of 200 points per Country worked including their own. Any one Country may be counted again if worked on another Band but Continents are counted once only. Two way exchange points time total Countries worked plus Total Country points times number of Continents worked. Use one log for each Band and indicate any rest periods. Logs to contain: Band, Time GMT, Message and RST Numbers sent and received and exchange points claimed. All Logs must be received by May 22nd 1971. Send Logs to: Ted Double G8CDW, 89, Linden Gardens, Enfield, Middlesex, England.


SELL: LATE MODEL SX101A RECEIVER excellent \$200.00. K0GZD, 4228 W. Capitol Ave., Grand Island, Nebraska 68801.

IC'S — MRTL, MC 790 P. \$1.90 each, 10 for \$18.00; μ L 914, .55 each, 10 for \$5.00; 100 KHz freq. std. crystal HC 13/U, \$4.00. Please add postage. Logic Components, Box 224, New Canaan, Conn. 06840.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

GEM-QUAD FIBRE — GLASS

ANTENNA FOR 10, 15, and 20 METERS.

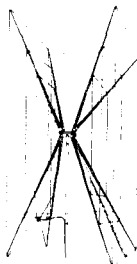

Two Elements \$87.00
Extra Elements \$50.00 ea.

Submit Payment with Order
Shipped Freight collect.

Price includes
Canadian Federal Sales Tax
or U.S. Customs Duty.

KIT COMPLETE WITH

- SPIDER
- ARMS
- WIRE
- BALUN KIT
- BOOM WHERE NEEDED

SEE OUR FULL PAGE IN MAY ISSUE

Buy two elements now — a third and fourth may be added later with little effort.

Enjoy optimum forward gain on DX, with a maximum back to front ratio and excellent side discrimination.

Get a maximum structural strength with low weight, using our "Tridetic" arms.



MANITOBA DESIGN INSTITUTE
AWARD WINNER

Structural Glass
LIMITED

Canadian Patent No. 794506
U.S. Patent No. 3532315

20 Burnett Avenue, Winnipeg 16, Manitoba, Canada

— SPECIAL COUNTER SALE — Northeastern Eng. 14-20C

\$179.50 FOB MONROE

10 Hz - 10 MHz - 8 digit nixie readout. Similar to HP524C and takes same plug-ins. Unchecked but appear exc. With manual. These units are without internal time standard but are otherwise complete. Construction details for solid-state replacement standard are supplied. Similar units complete, checked and operating - \$295 with manual FOB. All sales money back (less shipping) if not satisfied. Also have a limited number of 10-100MHz plug-ins - \$115. Time interval plug-ins - \$65. Send SASE for more counter data and list of other test equipment.

GRAY Electronics
P. O. Box 941 Monroe, MI 48161
Specializing in used test equipment

REVIEWED IN DECEMBER, 1968 HAM RADIO

the permaflex key

- both a twin lever & straight hand key in a pivotless 2 paddle design.
- gives instant choice of automatic semi-automatic & straight hand keying when used through an electronic keyer.
- use directly with any transmitter
- 8 amp. gold diffused silver contacts adjust from 0-060° & 3-50 grams.
- distinctive blue paddles are of rugged G-10 fiberglass epoxy.
- cabinet is 16 gauge polished chrome steel: 1.56" sq. x 3.75", paddles extend 1.25", weight 10 oz.
- silicone rubber feet for stability.
- 100% US made & guaranteed for 1 yr.



1995 complete, ppd usa & can. send a check or m.o. sold by mail only

James Research company, dep't:HQ-K
20 willits road, glen cove n.y. 11542



MONARCH SWR AND POWER METER

Reads output and reflected power simultaneously. May be left in line up to 2000 watts. Low insertion loss. Size 5x2x2. Good to 175 Mhz.
PRICE \$14.95 Insured Postage & Handling \$1.50

MADISON ELECTRONICS SUPPLY

1508 MCKINNEY — HOUSTON, TEXAS 77002
(713) 224-2668

radio amateur callbook

Radio Amateur
Emblems engraved
with your call letters.



Charm

- Gold
 Rhodium

call letters
\$6.00 Ea.



Tie Bar

- Gold
 Rhodium

call letters
\$6.00 Ea.



All illustrations
are actual size.

Lapel Pin

- Gold
 Rhodium

call letters
\$6.00 Ea.

Two or more emblems at the same time \$5.00 each.

Rush Order To: RADIO AMATEUR CALLBOOK, Inc.
Dept. E. 925 Sherwood Drive, Lake Bluff, Ill. 60044

NEW SECOND EDITION



Well Known as

"THE" Reference on Quads this Second Edition contains

NEW — revised gain figures for Quads

NEW — Delta Quad, Swiss Quad, Birdcage Quad

NEW — analysis of Quads vs. Yagi — which is best?

NEW — Miniature Quad construction and performance

NEW — Monster Quads (4 and 5 elements) — power gains up to 14!

NEW — charts with correct dimensions (feet and inches) for single band and multiband Quads, 6 thru 80 meters

NEW — improved Tri-Gamma match feeds triband Quad efficiently with one line

PLUS . . . The exhaustive storehouse of information that made the 1st edition so popular.

Still only \$3.95 postpaid

Send your order today to

book division

comtec

Box 592 • Amherst, New Hampshire 03031

BOOKS . . .

Radio Society of Great Britain publications

RADIO COMMUNICATIONS HANDBOOK — An outstanding technical guide to all phases of amateur radio. In 832 pages 20 complete chapters are devoted to such subjects as single sideband, antennas, mobile equipment, RITY and much, much more. This excellent book has received wide acclaim on both sides of the Atlantic and belongs in your library . . . now. **\$11.95**

AMATEUR RADIO CIRCUITS BOOK — Completely revised — new edition. A very handy collection of many useful circuits for amateur use. Loaded with good ideas for that new converter, exciter or other project you are working on. **Only \$2.00**

VHF-UHF MANUAL — G. R. Jessop, G6JP — Probably the most comprehensive work of its kind ever published. Covers everything from beginners to advanced material. **Only \$3.75**

AMATEUR RADIO TECHNIQUES — Third Edition — J. Pat Hawker, G3VA — Brand new edition — completely revised. A very complete collection of short articles and ideas covering many aspects of amateur radio. Includes new enlarged semiconductor section. 160 Pages. **Only \$3.50**

RADIO DATA REFERENCE BOOK — Second Edition — By G. K. Jessop, G6JP — Here in a 148 page book is one of the most complete compilations of radio and electronic charts, nomographs, formulas and design data available. Whether you design, build or operate, this is a book you must have. **Only \$2.50**

WORLD AT THEIR FINGERTIPS — John Clarricoats, G6CL — A very interesting history of the RSGB and of amateur radio in Great Britain. It gives a great insight into the development of our hobby. **Paper back edition \$2.50**
Deluxe edition \$6.50

Other Important Volumes

RADIO HANDBOOK — 18th Edition — How to design, build and operate the latest types of amateur transmitters, receivers, transceivers and amplifiers. Provides extensive, simplified theory on practically every phase of radio. 848 pages. **Only \$13.50**

ALL ABOUT CUBICAL QUAD ANTENNAS by W6SAI — Construction and tuning data. Multi-band Quads. Charts, drawings and photos for your Quad. Full complete data on homemade Quad antennas. The new X-Q Quad. **\$3.95**

VHF HANDBOOK by Orr W6SAI & Johnson W6QKO — First complete Handbook covering the VHF spectrum! Many VHF construction projects. Design and construction of VHF transmitters, receivers and antennas! Make your VHF station work! **\$3.95**

THE CARE AND FEEDING OF POWER GRID TUBES by Robert Sutherland, W6UOV — Just as the title says, a very complete rundown on the use of power tubes. Be sure to read this before you start work on your new linear. **Only \$3.95**

BEAM ANTENNA HANDBOOK by William Orr, W6SAI — New edition. Theory, design, construction, and the installation of rotary beam antennas! SWR data! Multi-band beams, 40 meter beams, 20 meter DX beams! How to make your beam work! 200 pages. **\$4.95**

NOVICE & TECHNICIAN HANDBOOK by W6SAI and W6TNS — All about amateur radio in non-technical language! How to learn the code. How to assemble your ham station. Transmitters! Receivers! DX! How to get QSL cards. **\$3.95**

ELECTRONIC CONSTRUCTION HANDBOOK by Robert Lewis, W8MQU — All about design - construction - layout and testing of electronic equipment. Non-technical guide for kit-builders and your best key to better performance of your equipment! **\$3.95**

comtec

Box 592 • Amherst, New Hampshire 03031

REVIEWED IN MARCH, 1968 HAM RADIO

mark 2 oscillator/monitor



- makes an audible tone to monitor the RF of any CW transmitter from 10Mw to 1 Kw & 100Kc to 1000Mc, using only an 8' pickup antenna.
- can be self-triggered for code practice or the testing of solid state components and circuits.
- aids in tuning up & testing RF oscillator and power circuits.
- 4 transistor, 2 diode circuit, speaker, tone adjust, AA pencil, test tips, 8" ant., & magnetic base.
- cabinet is 16 gauge black & clear anodized aluminum, 3.4 x 2.3 x 1.7" US made & guaranteed for 1 year.

14.95 complete, ppd use & can. send a check or m.o. sold by mail only

James Research company, dep't: HQ-M
20 willits road, glen cove n.y. 11542

5 India Pennies \$1.00
100 Foreign Coins \$3.95

BELLS COIN SHOP

Box 276
Tolleson, Arizona 85353

JOHN MESHNA JR.

WINTER SPECIALS HAND CRANK GENERATOR

Small hand crank fun-generator. Turning the crank puts out over 100 volts. Shock your friends, no-dig worm-linder, etc. Surplus govt. ringer generator. **Ham galore.**
#GEN \$3.50



TRANSISTOR IGNITION COIL \$3.50

Brand new trans. ign. coil w/kit. for automotive trans. ignition. Possibilities for patio-bug-killer. #TRANS \$3.50

2000 FEET FIBRE OPTICS \$1.00

FIBRE OPTICS light pipe. 200 fibre bundle unshathed. 10 ft. length. Pipes light around corners, under water, etc. Unbelievable price of only \$1.00 for 10 foot length. #LP-10 \$1.00

LED LIGHT EMITTING DIODE \$1.25

FANTASTIC price break thru on this INFRARED LED. You've been reading about them, now you can experiment. #LED 1.25

16 BIT MEMORY DIP PACKAGE \$1.75

Dual in line package at new low price

TUNNEL DIODE GE #TD-717 75¢

Open a new world of experimentation

10.7MC IF XFMR'S 5/\$1.00

Transistor type midget chromed style

ACA OP-AMP #CA3008 \$1.50

SIGNETICS CORP. DTL DIP PACKAGE
On boards - You remove 'em .40 ea. 400/doz.

- ST616A Dual 4 input expandable mand gate
- ST620A Dual JK Flip flop
- ST629A RS/T Binary element
- ST631A Quad 2 input gate expander
- ST659A Dual 4 input buffer/driver
- ST670A Triple 3 input mand gate
- ST680A Quad 2 input mand gate

CA3008 RCA OP AMP \$1.50

MOTOROLA DUAL INLINE IC'S

Factory marked, new.

- MC724P Quad 2 input NOR gate \$1.00
- MC725P Dual 4 input gate \$1.00
- MC790P Dual JK flip flop \$1.50
- MC792P Triple 3 input gate \$1.00
- MC795P Dual buffer \$1.00
- MC826P JK flip flop \$1.00

MOTOROLA TRANSISTORS FACTORY MARKED

- JAN 2N2907A 1.8 watt 60 volt 125mc 3/\$1.00
- 2N2218A 3 watt 40 volt 250mc 2/\$1.00

7400 SERIES IC GRAB BAG
Pack of assorted dual inline (10 units) unmarked, untested. Schematics included. Pkg. of 10 IC's \$1
IC SOCKET for DUAL INLINE 50¢
Add 25¢ postage on above orders. New catalog now out.

MESHNA, PO Box 62, E. Lynn, MA 01904

HAVE YOU TRIED A TRIANGLE ANTENNA?

"73 VERTICAL, BEAM and TRIANGLE ANTENNAS"

A BOOK by ED. NOLL W3FQJ

1/4 Verticals	Low Band Triangle	High Band Triangles
Ground Systems for Verticals	Triangle & Parasitic	Two-Element Antennas
10-15-20 Vertical	160M Two-Element Triangle	Yagi's
Base-Loaded Vertical	40-80 Three-Element Triangle	Quads
Base Tuner	Single Mast Triangle & Parasitic	Horizontal Phased Arrays
1/2 & 5/8 Verticals	80M Triangle & Ground Radials	End-Fire Beam
Phased Verticals	Triangle Turnstile	Broadside Array
Low Band Verticals	15-40-80 Triangle	Collinear, End-Fire
Four-Square Vertical		90° End-Fire
		AND MORE!


PRICE \$4.95 (\$5.95 Foreign) 160 pages 5 1/2 x 8 1/2

Plus Free Mimeographed Descriptions of Several New Triangles

TRIANGLE ANTENNAS
BOX 276 • WARRINGTON, PA. 18976



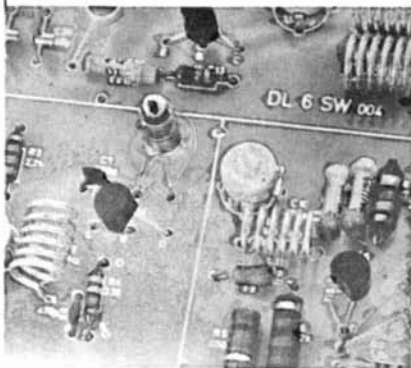A PUBLICATION FOR THE RADIO AMATEUR
ESPECIALLY COVERING VHF, UHF AND MICROWAVES



VHF COMMUNICATIONS is written for and by amateurs interested in VHF/UHF technology and equipment construction. Each issue contains at least sixty pages of complete and detailed construction articles on VHF and UHF receivers, converters, transceivers, transmitters, transverters, antennas and test equipment. Solid state devices and printed circuit techniques are used extensively. Special components, such as p.c. boards and complex metal work as well as component kits are made available so that the designs featured can be readily duplicated even by those with limited fabrication and testing facilities.

VHF COMMUNICATIONS also brings theoretical articles and reports on new technological developments of interest to the VHF/UHF amateur.

VHF COMMUNICATIONS is a quarterly, published in February, May, August and November. It is mailed to the subscriber directly from the publisher in West Germany. Subscriptions are by calendar year. The subscription rates are US \$3.50 surface mail, US \$4.50 air mail. Single issues US \$1.10.

Write to:


VHF COMMUNICATIONS

BOX 283
FORESTDALE, MASSACHUSETTS 02644

NEW G&G CATALOG! MILITARY ELECTRONICS

24 PAGES, crammed with Gov't Surplus Electronic Gear - the Biggest Bargain Buys in America! It will pay you to for your copy - Refunded with your first order. **SEND 25¢**

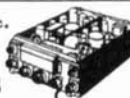BC-645 TRANSCEIVER 15 tubes, 435 to 500 Mc. Easily adapted for 2 way voice or code on Ham, Mobile, Television Experimental, and Citizens Bands. With tubes, less power supply in factory carton, BRAND NEW..... **\$16.95**



TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7
RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7
RECEIVER I.F.: 40 Megacycles
SIZE: 10-1/2" x 13-1/2" x 4-1/2". Shpg wt 25 lbs.

SPECIAL PACKAGE OFFER: BC-645 Transceiver, Dynamotor and all accessories, including mounting, UHF Antenna Assemblies, control box, complete set of connectors and plugs. Brand New **\$26.95**

AN/APR - 4Y FM & AM RECEIVER "FB" for Satellite Tracking!

High precision lab instrument, for monitoring and measuring frequency and relative signal strength, 38 to 4000 Mc. in 5 tuning ranges. For 110 v 60 cycle AC. Built-in power supply. Original circuit diagram included. Checked out, Perfect. LIKE NEW..... **\$88.50**



TG-34A CODE KEYS, self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM Built-in speaker. Brand new with tech manual, takeup reel and AC line cord. ... **\$24.50**
Code practice tapes for above P.U.R.



WILLARD 2-VOLT STORAGE BATTERY

Rated at 20 Amp.-Hours. Model 20-2. Rechargeable. Compact nonslip construction. Lightweight polystyrene container, 3x4x5 1/2". Shipped dry, uses standard electrolyte. Shipping Weight 3 lbs. NEW, each..... **\$2.79**



HEADSET

Low impedance. With large chamois ear cushions. 4-ft. cord and plug. Reg. \$12.50. OUR SPECIAL PRICE..... **\$2.95**
High impedance adaptor for above 69¢



SCR-274-N, ARC-5 COMMAND SET HQ!

Freq. Range	Type	Exc. Used	Like New	Brand New
RECEIVERS				
100-550 Mc.	BC-453	\$16.95	\$23.50	\$27.50
3-6 Mc.	BC-454	\$14.50	\$18.50	\$22.50
6-9.1 Mc.	BC-455	\$14.50	\$17.95	\$21.50
1.5-3 Mc.	R-25	---	\$19.50	\$23.50
TRANSMITTERS				
4-5.3 Mc.	BC-456	---	---	\$11.95
5-3.7 Mc.	BC-457	---	---	\$11.95
7-9.1 Mc.	BC-459	---	---	\$23.50

ARC-R11A Modern Q-5 Receiver 190 - 550 KHz **\$10.95**
ARC-R22 540 - 1600 KHz Receiver with tuning graph **\$15.95**
R-4/ARR-2 Receiver 234-258 Mhz, 11 tubes, NEW **\$8.95**

SCR-625 ARMY MINE DETECTOR Complete **\$32.50**
EE-8 SIGNAL CORPS FIELD PHONES **\$16.95**
T-30 THROAT MIKE, NEW 59¢ USED 39¢
T-17 MICROPHONE, NEW \$8.50 USED, checked out \$4.95
BC-605 INTERPHONE AMPLIFIER, NEW \$3.45 EXC. USED **\$1.95**
TELEPHONE HANDSET, W.E. type LIKE NEW **\$2.95**
SCR-522 TRANSMITTER-RECEIVER, with 18 tubes. LIKE NEW \$32.50

AM-300/AIC PUSH-PULL AMPLIFIER

4-tube PP power amplifier with dynamotor, works on 28 VDC. Automatic gain control. Shpg wt 15 lbs. LIKE NEW..... **\$4.95**



FREQUENCY METER MODEL LM

Fine general purpose Navy unit, range 125 to 20,000 Kc. Operates on 12/24 VDC & 200V 10 Ma DC. Complete with tubes, crystal, calib. book. Checked out, EXCELLENT USED..... **\$59.50**
As above, less book \$24.50 AC Power Supply. \$19.50



McELROY AUTOMATIC KEYS for keying transmitter or for code practice. Photoelectric cell & sensitive relay. Variable speed motor 110V 60 cy Complete with tubes, EXC. USED **\$11.25**



BC-733 RECEIVER Receives radio signals being transmitted by US satellite on approx. 108 Mc. AM, crystal-controlled on 6 preset freqs. In 108.3 to 110.3 Mc range. Operates on 12/24 V DC & 220 VDC 80 Ma. Complete with 10 tubes. Can be converted to FM Receiver 80 to 108 Mc. Exc. Used..... **\$5.95**
BC-732A Control Box for above, NEW... 1.75



T-41 / APS - 18 TRANSMITTER

ANTENNA UNIT designed for 115 V 800 to 1400 cps. Tubes included are two 15E and one 15R. Complete with shock mounts and blower motor, 7x3x18", NEW.... **\$7.45**



RADIO SET AN/ APR-21 TRANSMITTER & RECEIVER

Freq. modulated 152 to 174 Mc. Operated on any preset frequency within VHF range 152-174 Mc FM. Reliable voice communication over moderate distances. Includes antenna, handset H-33 and two carrying straps. Size 12x8-1/4x5-3/4. Wt 15 lbs. LIKE NEW, complete **\$69.50**



AM-26/AIC PHASE INVERTER AMP.

4-tube pushpull power amplifier. Carbon mike input, hi-la imp. output. Works on 24VDC. Easily converted to dandy 9-watt amplifier. Complete with tubes and dynamotor LIKE NEW **\$6.95**



DUAL AMPLIFIER has two input circuits each feeding a single 6SN7GT twin triode amplifier.

Complete with 115V 60 cy. power supply using 6X5GT rectifier. NEW..... **\$5.95**



IP-69A/ALA-2 INDICATOR 3" scope.

Front panel controls: Vertical Pos., horizontal pos. Intensity, focus, gain, width, center freq. Pan. Operates on 115 V 380 to 1000 cps. Complete with tubes. LIKE NEW..... **\$24.50**



BC-929 US GOVT SCOPE INDICATOR

Compact radar display unit uses 38P1. A favorite with TTY fans as foundation for converter with cross-line scope presentation. Also for Hams: Modulation-monitor foundation. Complete with all tubes. LIKE NEW.... **\$16.95**



TG-5B TELEGRAPH SET for code communications or code practice. Portable, with hinged lid. Two or more units operate up to 25 miles apart. Bell call system, 1000 cycle howler, key, headpiece, canvas case, book.

Size 5-1/2x5-1/2x10". NEW..... **\$8.95**



TS-100AP TEST OSCILLOSCOPE Small portable instrument used to test and calibrate range measuring circuits of radar systems. Used for viewing short video pulses on 3" screen. Power supply: 115 or 230 V 50-1200 cps. Complete with plugs, cables..... **\$59.50**



TS-126/AP RANGE CALIBRATOR TEST SCOPE Top quality 2" scope with all positioning, focus, gain and intensity controls. Complete with tubes and cables, NEW. **\$24.50**

Demilitarized, like new..... **\$13.75**



TELEPHONE TYPE RELAY

Made by J.H. Bunnell, has adjustable sensitivity, 150 ohm coil. NEW..... **\$3.45**



T-28 / APT TRANSMITTER radar jamming covering freq. 140 to 210 Mc. Osc. Amp. Plate, Grid Plate & Mixer Plate controls on front panel. Complete with tubes, 7-1/2x10x20" Wt 40 lbs. NEW..... **\$32.50**



TERMS: 25% Deposit with order, balance C.O.D. -or- Remittance in full. Minimum order \$5.99 F.O.B. NYC. Subject to prior sale and price change

G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. (2nd Fl.) New York, N.Y. 10007 Ph. 212-267-4605

Hi-Sensitivity Wide-Band AM / FM RCVR

38-1000 MHZ: AN/ALR-5 consists of brand-new Tuner/Converter CV-253/ALR in original factory pack and an exc., used, checked OK & grtd. main rcvr R-444 modified for 120 v, 50/60 hz. Packed with each tuner is the factory checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.3 mhz, 0.9 at 133 mhz, 5 at 538 mhz, 4 1/2 at 778 mhz, 7 at 1 ghz. With book & pwr-input plug, all for **275.00**

R-390/URR Rcvr: Collins xtl-zero-beating, driftless receiver, grtd 100% perfect. **795.00**

R-390A/URR has mech. filters, grtd perfect. **995.00**

Regul. Pwr Sply for Command, LM, Etc.

PP-106/U: Metered. Knob-adjustable 90-270 v up to 80 ma dc; also select an AC of 6.3 v 5A, or 12.6 v 2 1/2 A or 28 v 2 1/2 A. With mating output plug & all tech. data. Shpg. wt. 50 lbs. **19.50**

BARGAINS WHICH THE ABOVE WILL POWER:
LM-100 Freq. Meter .125-20 MHz, .01%, CW or AM, with serial-matched calib. book, tech. data, mating plug. Shipping wt. 16 lbs. **57.50**
Same less calib. book. **12.50**

TS-323 Freq. Meter: 20-480 MHz .001% **169.50**

A.R.C. R22: 540-1600 kHz rcvr, same size & shape as the popular and well-known Command rcvrs like the BC453, R23/ARC5, etc. No calib. dial but we furnish spline knob with graph of turns vs freq., and all tech data, connections, etc. **17.95**

A.R.C. R32: Same as above except 108-132 MHz with Squelch ckt, very hot. W/data & graph **12.95**

Our warehouses are bursting with good OSCILLOSCOPES, Digital Counters, Aeronautical Test Sets, Audio Test Sets, Oscillators, VTVM's, Precision Meters, Pulse Generators, Signal Generators, Differential Voltmeters, Regulated Power Supplies, Ham Receivers, Wattmeters, Line-Voltage Regulators, etc. etc. We can't possibly begin to list every thing in these ads. We have separate Catalogs for each Category of Equipment . . . so please ask for your needs by the type of equipment you need! Thanks!

WE ALSO BUY! WHAT DO YOU HAVE?

R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

ANTENNAS — GREAT — (Omnidirectional fiberglass whips) — Model DYCOMM 71-MB: 12' base station, especially for repeaters around 146-147. Gain peaks out at 8 db over dipole. Built to withstand 150 MPH winds. Price: Only \$79.95. 71-M6: 9'; 6 db, for mobile or base use. Price: Only \$69.95

Call or write Jim W4MR1

DYNAMIC COMMUNICATIONS, INC.

(305) 844-1323

948-A Avenue E, Riviera Beach, Fla. 33404

WE PAY **HIGHEST**
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS

H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK

ELIZABETH, NEW JERSEY 07206

(201) 351-4200

RF MULTIMETER — 1 mv. to 1v. DC and RF to 1 Ghz.. VSWR 1.35 & 3.00 full scale, 0 to 60 dB., many other features: Model RFM-1.
VSWR BRIDGE SET - Precise swept frequency or cw VSWR measurement to 2 Ghz., includes bridge, termination, and mismatches: Model RCS-1.
BROADBAND RF AMP — 30 dB. gain minimum 10 to 150 MHz., 10 dB. gain minimum to 500 MHz., noise figure is 6 dB. maximum: Model BBA-1.
PREMIUM RF AMP - Same as above but with low noise transistors and selected components, noise figure is 3 dB. maximum: Model BBA 1P.
BROADBAND DETECTORS - Coaxial RF detectors in BNC type male and female, high efficiency; 1 MHz to 1 GHz ± 1 dB Model CRD 1,2.
PEAK N NOTCH FILTER - Tunable by front panel control from 100 to 2500 Hz., 25 db. peak or notch selectable by switch; unity voltage gain; will drive phones or small speaker Model PNN 1.

Write for More Information and Discount Prices

RADIATION DEVICES CO.

P.O. Box 8450, BALTIMORE, MD. 21234

U.S.A. Coin Guide

Show the value of over 1400 United States coins. Only \$1.00.

BELLS COIN SHOP

Box 276

Tolleson, Arizona 85353

READOUT (NIXIE) TUBES

NL 940S, by National Electronics reads 0 to 9, decimal point either side. So can read "0; 1; 2; 8; or 9. BRAND NEW, individually cartoned. **10/\$60.00; 4/\$25.00; each \$6.50**

CO-AXIAL, T-R, SWITCHES and RELAYS

BIRD #72RS3. DPDT, double break, no cross talk or intermodulation. Will handle 1 KW, at 50 ohms to 2 KMC. Has 4 N type receptacles, take UG-21/U; pointer handle. 3 3/4" dia. 2 1/2" deep + 2" for handle, + 1" for connectors. Has mounting bracket, 5 Lbs. NEW. each **\$8.50** Above switch, with 4 UG-21/U co-ax connectors. NEW. **\$9.75**

ARC # RE-275/AR. DPST T-R relay. Has 3 BNC receptacles, UG-190/U. 100 watt, at 50 ohms, to 150 MC. 28v DC coil. Enclosed in metal box, 2 3/4" long + 1/2" for power receptacle, 1 1/2" wide + 1/2" for UG-190/U, 1 3/8" high. On base 2 3/8" x 2 3/8". 1 Lb. **4/\$6.50; each \$1.75**
RAX-16, for MOTOROLA 80D. SPDT, T-R relay. Has 2 SO-239, for receive and antenna; solder terminal for transmit. Fits inside of transmitter. 100 watts, at 50 ohms, to 150 MC. Has 12v DC, 75 ohm coil. 2 3/8" long, 1 3/8" wide, 2 1/2" deep. 1 Lb. **4/\$10.50 each \$2.75**

VACUUM T-R SWITCHES and RELAYS

in Glass Envelopes. Brand New.

SPERTI # AF-10, SPST, double break, on metal bracket, with 28v DC solenoid. each **\$2.50**
SPERTI # IS24, SPST, double break T-R switch. Spare for above. **4/\$5.50; each \$1.50**
CHATHAM # 1S22, SPDT switch. Heavy duty. **4/\$7.50; each \$2.00**

UG-190A/U, BNC chassis receptacle. TEFLON insulation. Really like-new takeouts; clean, bright. No tarnish. **10/\$3.50; 4/\$1.50; each 39¢**

All prices are NET, FOB store, Chicago. PLEASE include sufficient for shipping charges. Any excess returned with order. Insufficient postage is getting expensive.

B C Electronics

5696 North Ridge Avenue
Chicago, Illinois 60626

... Hours ...

Wednesday 11:00 AM to 2:30 PM

Saturday 10:00 AM to 2:30 PM

Other Times, Strictly by
Previous Appointment Only

... Phones ...

312-334-4463, no answer please call 312-784-4426
Mailing Address for all orders, inquiries and correspondence: c/o BEN COHN, 1249 W. ROSEDALE AVE., CHICAGO, ILLINOIS 60626.

Reginair Universal DC Supply

~~~~~

**\$119.95**

~~~~~

We announce to our ham customers the availability of the Reginair Universal DC supply complementing our line of Reginair products sold exclusively through this firm. This DC supply is a robust reliably built American-made product (actually made for us by Linear Systems Company of California), flexibly designed to provide years of highly efficient performance for nearly every transceiver available.

If you purchased your transceiver with an AC power supply and subsequently felt the need to operate in a car or a boat, you probably were somewhat aghast at the prices of comparably rated power supplies. Here is a heavier than average unit made to supply the needs of the Collins KWM1 or 2, the Drake TR3, 4 and 6, the Eico 753, the Galaxy 3, 4 or 550, the Hallicrafters 150, 160 or 500, the entire Heathkit SB100 or HW100 series, the National NCX3, 5, 200 or 500, and any or all of the Swan's including the 240, 250, 250C, 350, 350C, 400, 500 and the 500C. A special heat sink chassis with special extrusions and high quality fittings and measuring 9" long by 6" wide by 3 $\frac{3}{8}$ " thick houses this modern designed device. The power transformer is designed with three taps so as to provide 650, 750, 850 volts out of the transformer, while the second winding provides 250, 285 or 325 volts. Of extreme advantage to some owners is the built-in bias

control. Two rectifier bridges, both conservatively rated and with appropriate filters, provide exceptionally clean outputs.

The DC input circuit is worth commenting about. Four specially selected to operate at their highest gain Solitron high voltage transistors are employed in a two-stage closed loop oscillator in such a way that high magnetizing currents are not introduced in the power transformer. Amplified feedback insures splendid regulation and easy starting. Power resistors conventionally found in switching circuits are eliminated in this design adding to the efficiency. A 12 volt DC relay and a 40 amp circuit breaker complete the picture. Here is a unit which you can very definitely be proud of. A unit you will want to keep long after you have traded your transceiver. Very exceptionally built and constructed of the best quality components, this supply has nothing of skimpy design contained in it. The quality of workmanship is superb, and the over-all accessibility permits easy subsequent service should this be necessary in that rare eventuality. When your check accompanies your order, we will prepay to US and Canadian points. Supplied with heavy primary wiring and output cable. Mention of your specific transceiver will mean that we will furnish a mating plug to match. Warranted 180 days.

Open Tuesday and Thursday till ten.

~~~~~

## HERBERT W. GORDON COMPANY

HELPING HAMS TO HELP THEMSELVES



PHONE 617 456 3548

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

## INDEX

- |                        |                    |
|------------------------|--------------------|
| —Alco                  | —Meshna            |
| —BC                    | —Micro-Z           |
| —Barry                 | —Mosley            |
| —Bells                 | —Motorola          |
| —Collins               | —National          |
| —Comtec                | —Pickering         |
| —Cir-Kit               | —R & R             |
| —Curtis                | —RF Communications |
| —Dames                 | —R P               |
| —DyComm                | —Radiation         |
| —ES                    | —Callbook          |
| —Ehrhorn               | —Radio Constructor |
| —Eimac                 | —Radio Shop        |
| —Flinn                 | —Robot Research    |
| —G & G                 | —Ross & White      |
| —Goodheart             | —Sentry            |
| —Gordon                | —Siliconix         |
| —Gray                  | —Spectronics       |
| —H & H                 | —Spectrum          |
| —H & L                 | —Structural Glass  |
| —HAL                   | —Swan              |
| —Ham Radio             | —Telrex            |
| —Heath                 | —Ten-Tec           |
| —Henry                 | —Tri-Ex            |
| —International Crystal | —Tri-Rio           |
| —James                 | —Triangle          |
| —Jan                   | —VHF               |
| —Justin                | —Vanguard          |
| —LA                    | —Weinschenker      |
| —Madison               | —World QSL         |

January 1971

Please use before February 28, 1971

Tear off and mail to

**HAM RADIO MAGAZINE** — "check-off"  
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....

# Advertisers iNdex

|                                                     |                   |
|-----------------------------------------------------|-------------------|
| Alco Electronic Products .....                      | 86                |
| BC Electronics .....                                | 92                |
| Barry Electronics .....                             | 81                |
| Bells Coin Shop .....                               | 89, 92            |
| Communications Technology, Inc. ....                | 72, 88, 89        |
| Cir-Kit .....                                       | 80                |
| Curtis Electro-Devices .....                        | 86                |
| Dames Co., Ted .....                                | 68                |
| Dynamic Communications .....                        | 74, 92            |
| ES Electronic Labs .....                            | 80                |
| Ehrhorn Technological Operations .....              | Cover II          |
| Eimac Division of Varian .....                      | 48, 49            |
| Flinn, David G. ....                                | 86                |
| G & G Radio Electronics Co. ....                    | 91                |
| Goodheart Co., Inc., R. E. ....                     | 92                |
| Gordon Co., Herbert W. ....                         | 93                |
| Gray Electronics .....                              | 87                |
| H & H Engineering .....                             | 80                |
| H & L Associates .....                              | 92                |
| HAL Devices .....                                   | 69, 84            |
| Ham Radio Magazine .....                            | 84                |
| Heath Co. ....                                      | 2                 |
| Henry Radio .....                                   | 5                 |
| International Crystal Manufacturing Co. ....        | 31                |
| James Research .....                                | 88, 89            |
| Jan Crystals .....                                  | 74                |
| Justin, Inc. ....                                   | 68                |
| LA Amateur Radio Sales .....                        | 82                |
| Madison Electronics .....                           | 88                |
| Meshna, John, Jr. ....                              | 89                |
| Micro-Z Co. ....                                    | 85                |
| Mosley Electronics, Inc. ....                       | 78, 79            |
| National Radio Co., Inc. ....                       | 23                |
| Pickering Radio Co. ....                            | 84                |
| R & R Electronics .....                             | 64, 80            |
| RP Electronics .....                                | 86                |
| Radiation Devices Co. ....                          | 92                |
| Radio Amateur Callbook, Inc. ....                   | 76, 85, 88        |
| Radio Constructor .....                             | 76                |
| Radio Shop, Lab 1 .....                             | 71                |
| Ross & White .....                                  | 73                |
| Sentry Manufacturing Co. ....                       | 1                 |
| Siliconix, Inc. ....                                | 77                |
| Spectronics .....                                   | 95, 96, Cover III |
| Spectrum International .....                        | 82                |
| Structural Glass Ltd. ....                          | 87                |
| Swan Electronics .....                              | Cover IV          |
| Telrex Communication Engineering Laboratories ..... | 53                |
| Ten-Tec, Inc. ....                                  | 81                |
| Tri-Ex Tower Corp. ....                             | 47                |
| Tri-Rio Electronics .....                           | 86                |
| Triangle Antennas .....                             | 90                |
| VHF Communication .....                             | 90                |
| Vanguard Labs .....                                 | 76                |
| Weinschenker, M. ....                               | 75                |
| World QSL Bureau .....                              | 86                |



# The reason the Yaesu FT-101 is the world's best portable rig is really an inside story.



Mill-spec gear? That's the way it looks. And that's the way it works. It's the solid-state FT-101 portable Yaesu.

Except for the final tubes, the FT-101 uses 10 FET's, 3 IC's, 31 silicon transistors and 38 silicon diodes. And most of them are found on plug-in computer-type modules. Modules that you mail to us for factory-new replacements, should they ever give you trouble. And the whole rig is guaranteed for one year.

But ruggedness is only a footnote to the FT-

supplies. You supply the 12 or 117 volts plus an antenna and you're ready to work the world — on the 80 meter band right through 10 meters. And you'll work it with 260 W PEP, 180 W CW or 80 W AM maximum input power. Receiving sensitivity is 0.3 microvolts for a 10 db signal-to-noise ratio.

For in-car operation, there's a built-in noise blanker. It picks out noise spikes and leaves clean signal copy behind.

Another important part of the FT-101 story is the price: only \$499.95.



101 story. The real story is found in features. Features like a built-in VOX, 25 KHz and 100 KHz calibrators, the WWV 10 MHz band, a high Q permeability tuned RF stage and a  $\pm 5$  KHz clarifier. That means home-base type operation, whether you're cruising near Pawtucket or working portable somewhere on the outskirts of Pago-Pago.

It's all in a thirty-pound package that even includes built-in 12 VDC and 117 VAC power

## SPECTRONICS WEST

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

## SPECTRONICS EAST

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ \_\_\_\_\_

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All prices F.O.B. Signal Hill, Ca.
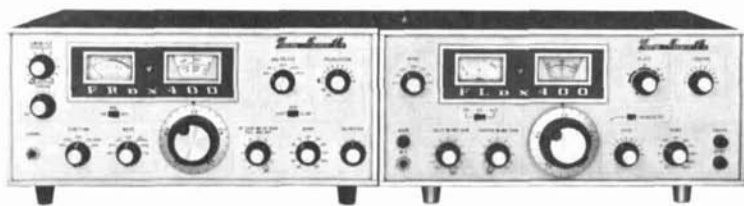
# Now you don't have to pay twice the price to get twice the rig.

Picture this pair in your shack. The Yaesu FLdx 400 transmitter and the FRdx 400 receiver. Loaded with power. Loaded with sensitivity. Loaded with features. Loaded with value. Read on, and discover how you can have the most up-to-date receiver-transmitter rig in the world... and at an unbelievably low price.



meters—with an optional provision for certain other bands that you can personally specify. For all that, you pay just \$299.95.

## The FRdx 400 Receiver

Get a big ear on the world with complete amateur band coverage from 160 meters through 2 meters, including WWV and CB reception. Four mechanical filters do it—they provide CW, SSB, AM and FM selectivity. Separate AM-SSB-FM detectors are included, along with squelch and transmit monitor controls. Plus a noise limiter and a variable delay AGC. And a built-in notch filter with front panel adjust for notch depth.

The FRdx includes calibration markers at 100 KHz and 25 KHz, with accurate calibrator checks verified by WWV. A solid-state FET VFO for unshakable stability. And a direct-reading 1 KHz dial affords frequency read-out to less than 200 Hertz.

The FRdx 400 sells for \$359.95.



## FL2000 B Linear Amplifier.

Ideal companion to the Series 400, this hand-crafted linear is another example of Yaesu's unbeatable combination of high quality and low cost. Designed to operate at 1500 watts PEP SSB and 1000 watts CW, this unit provides superb regulation—achieved by a filter system with 28 UF effective capacity.

Other features include dual cooling fans (one for each tube), individual tuned input coils on each band for maximum efficiency and low distortion, and a final amplifier of the grounded grid type using two rugged carbon-plate 572 B tubes. Ready to operate at only \$299.95.

## The FLdx 400 Transmitter

Here's how to set yourself up with dual receive, transceive or split VFO operation. The FLdx 400 with its companion receiver brings you the ultimate in operational flexibility. Flexibility like frequency spotting, VOX, break-in CW, SSB, AM and even an optional FSK circuit.

The completely self-contained FLdx 400 features a built-in power supply, fully adjustable VOX, a mechanical SSB filter, metered ALC, IC and PO. A completely solid-state FET VFO provides rock-solid frequency stability.

We rate the FLdx 400 very conservatively. That rating guarantees you 240 W PEP input SSB, 120 W CW and 75 W AM. The FSK option will go all day at a continuous 75 W. And you get full frequency coverage on all amateur bands—80 meters through 10

## SPECTRONICS WEST

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

## SPECTRONICS EAST

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ \_\_\_\_\_

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All prices F.O.B. Signal Hill, Ca.

# For \$450, you just can't beat the Yaesu FTdx 560.

## You can't even beat it for \$800.


How come the Yaesu is such a good deal?

First of all, it's made in Japan, where people do painstaking electronic assembly work for a lot less money than they do in the U.S. Secondly, it's probably the highest quality transceiver made anywhere in the world, regardless of cost.

Also we import the Yaesu and sell it direct to you, eliminating the usual dealer profit.

The Yaesu FTdx 560 is a fully assembled, fully guaranteed transceiver with 560 watts PEP of SSB power, 500 CW. Included in the selling price are many of the things you usually have to pay extra for. Like power supply, WWV, calibrators, VOX and the one-year warranty. And a lot more.

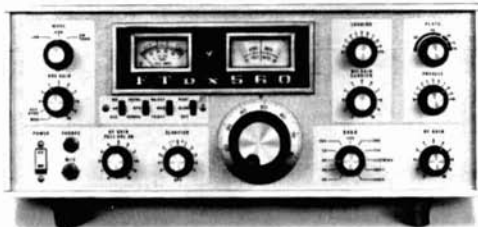To see how much more you get with Yaesu, send for our new information packet. It includes things like a chart and photos that compare Yaesu and Yaesu workmanship with other transceivers, plus a complete schematic. Study this packet and you'll see right away how much more value there is in a Yaesu.



### **SPECTRONICS WEST**

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

### **SPECTRONICS EAST**

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ \_\_\_\_\_

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All prices F.O.B. Signal Hill, Ca.

**WORLD  
TRAVELER**



## SWAN *Cygnet* 270B

### SSB TRANSCEIVER

The 5 band deluxe 270-B, with a power rating of 260 Watts P.E.P., is a complete self contained radio station with built-in AC power supply and speaker in one compact, portable package. You can take it with you on vacation or business trips, operate from your motel room, your boat, car, or hide-away cabin. All you do is connect to an AC power source and antenna, plug in your mike and you're on the air, with enough power to work the world.

The Swan Cygnet 270B is a world traveler. And the price is a world beater! **\$499**




**ELECTRONICS**

305 Airport Road

Oceanside, California 92054

A Subsidiary of Cubic Corporation

**1200 WATTS  
\$295**

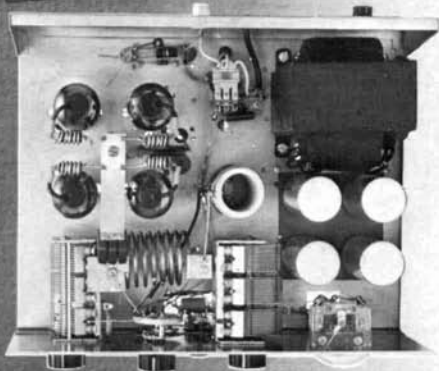

## SWAN 1200W 1200 WATT LINEAR AMPLIFIER WITH SELF CONTAINED AC POWER SUPPLY

We built this little gem to go with our Cygnet 270B. But when word got around that Swan had a 1200 Watt amp with a built-in AC power supply, for just two hundred and ninety-five bucks, all h---broke loose. Production has finally caught up with sales again, so see your dealer soon.



**ELECTRONICS**

305 Airport Road

Oceanside, California 92054

A Subsidiary of Cubic Corporation